



OPERATIONAL AMPLIFIER

INTRODUCTION

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Op-Amp Abstraction


Ideal Op-Amp

Non-inverting Op-Amp



LUMPED CIRCUIT ABSTRACTION

Physics Law

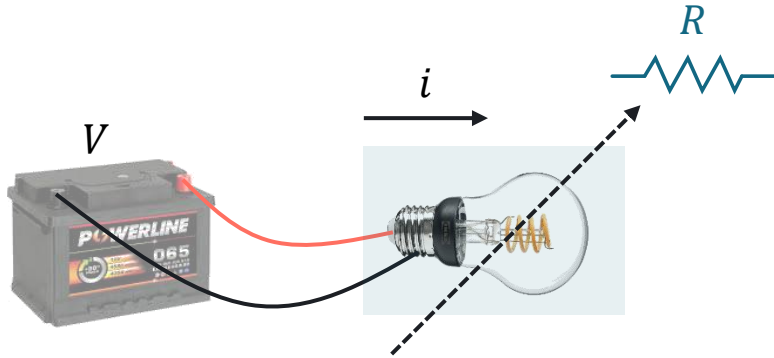


Maxwell's Equation

$$\nabla \cdot E = -\frac{\partial B}{\partial t} \xrightarrow{0}$$



$$\nabla \cdot J = -\frac{\partial \rho}{\partial t} \xrightarrow{0}$$

$$\nabla \cdot E = \frac{\rho}{\epsilon_0} \xrightarrow{0}$$

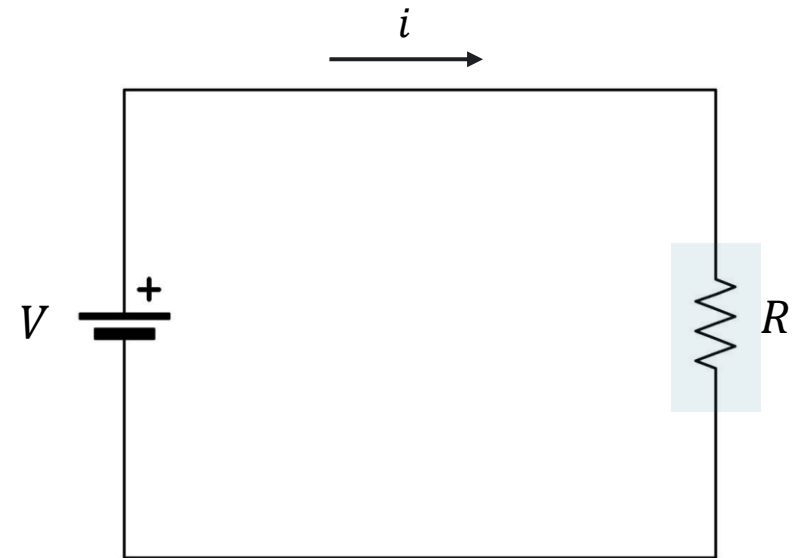R is a lumped element abstraction for the bulb



DIGITAL ABSTRACTION

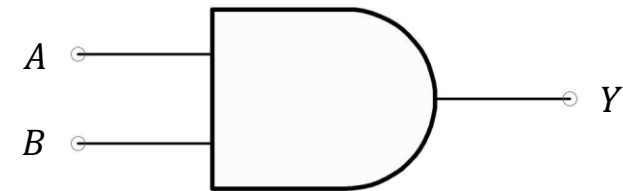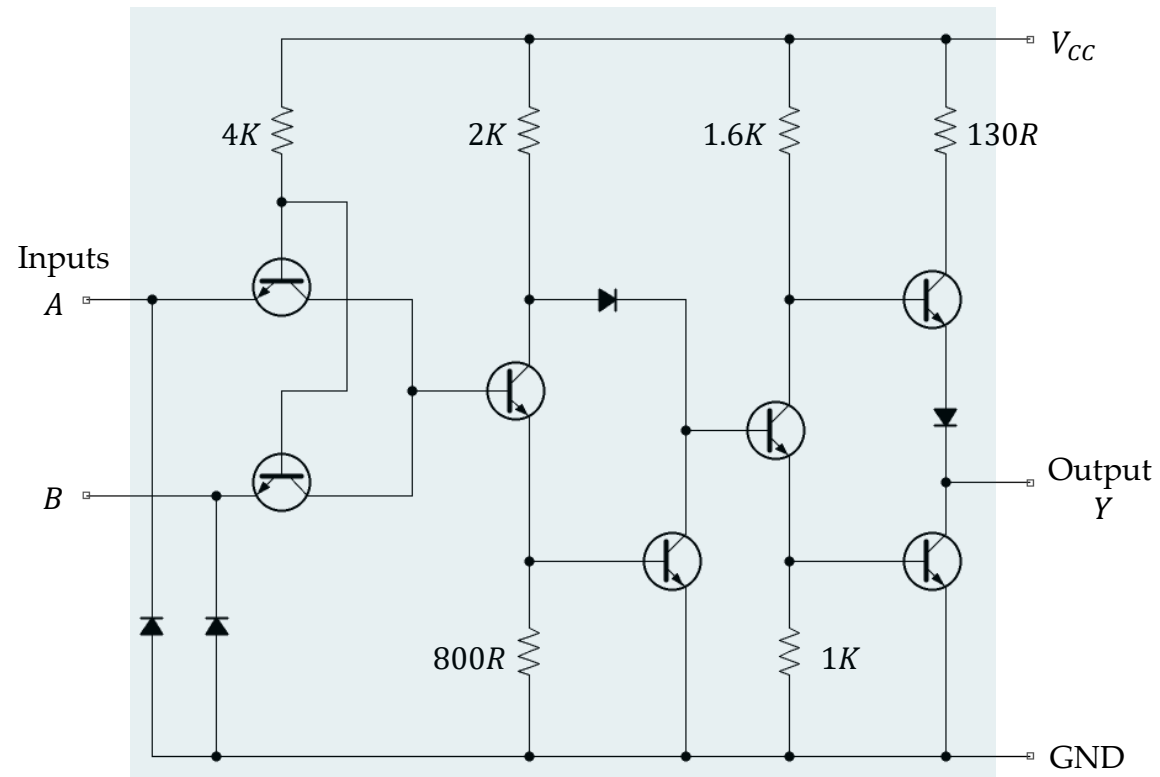

LANGUAGE ABSTRACTION

```
#include <libioP.h>
#include <stdarg.h>
#include <stdio.h>

#undef printf

/* Write formatted output to stdout from the format string
FORMAT.  */
/* VARARGS1 */
int
__printf (const char *format, ...)
{
    va_list arg;
    int done;

    va_start (arg, format);
    done = vfprintf (stdout, format, arg);
    va_end (arg);

    return done;
}



#undef _IO_printf
ldbl_strong_alias (__printf, printf);
/* This is for libg++.  */
ldbl_strong_alias (__printf, _IO_printf);
```



printf()



OP-AMP ABSTRACTION

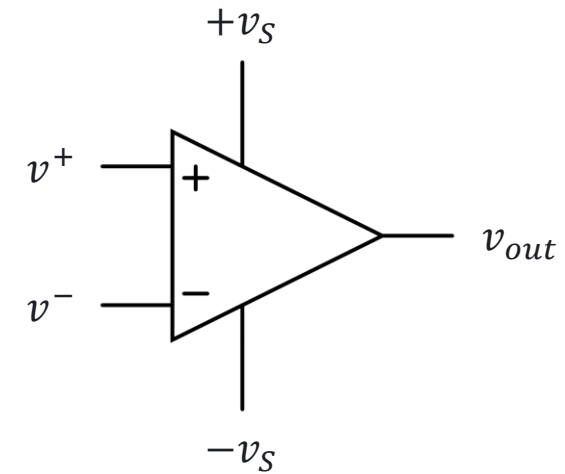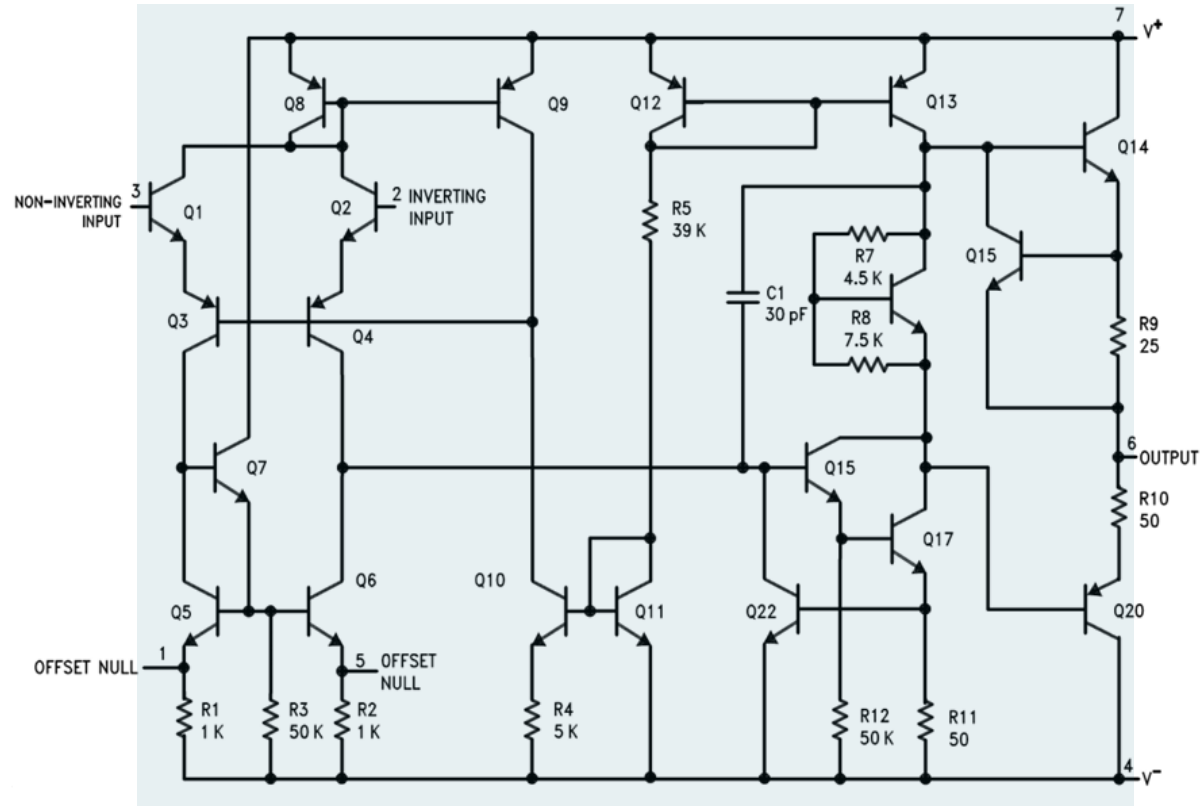


IDEAL OP-AMP




IDEAL OP-AMP

Abstract representation

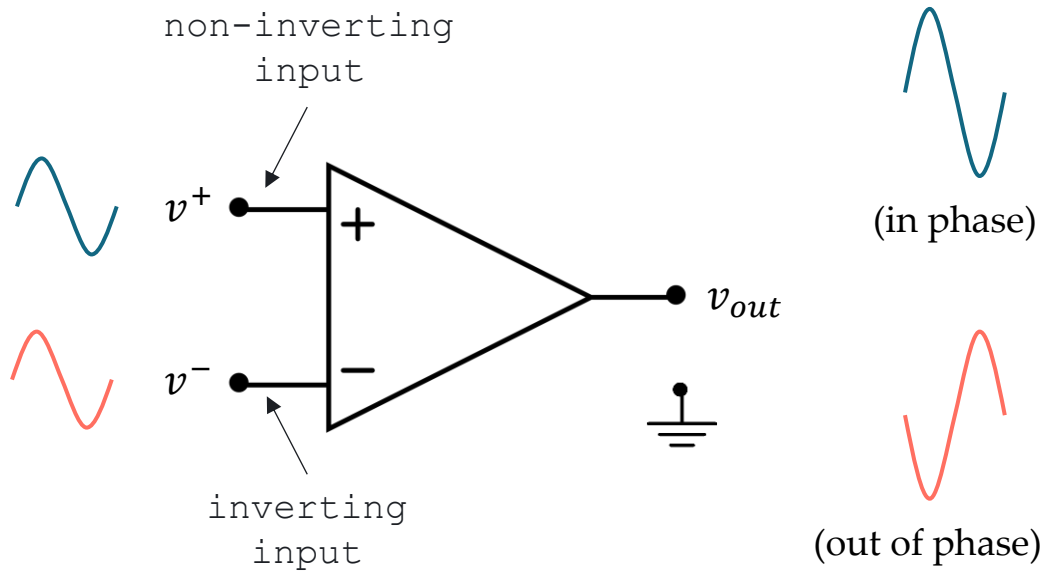

Circuit model

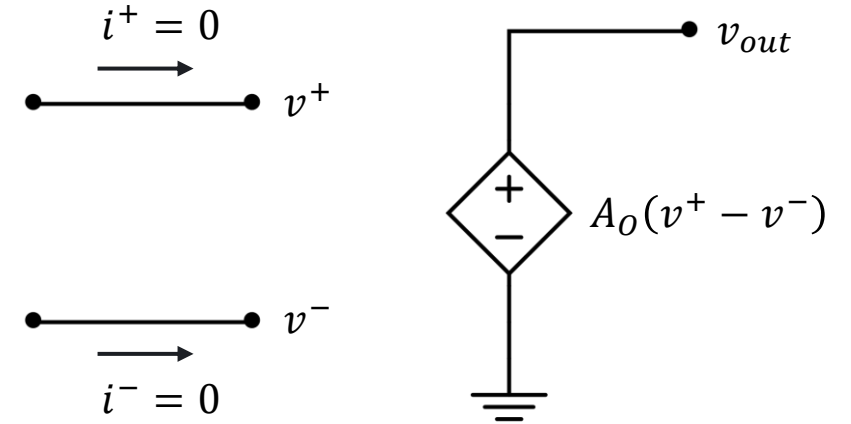


IDEAL OP-AMP

Properties of an ideal op-amp


- ($R_{in} \rightarrow \infty$) Infinite input resistance
- (R_{out}) Zero output resistance
- ($A_o \rightarrow \infty$) Infinite open-loop gain
- ($v_{out} \rightarrow \infty$) No saturation

Circuit model

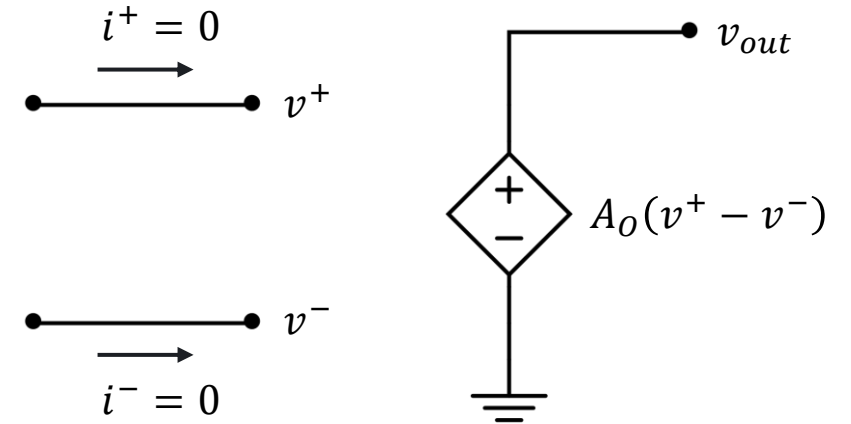


SATURATION REGION

Abstract representation

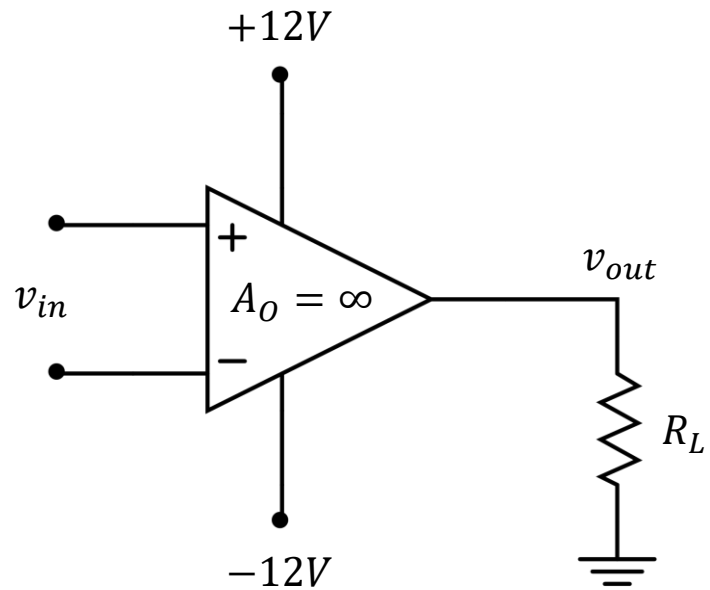

Transfer characteristic

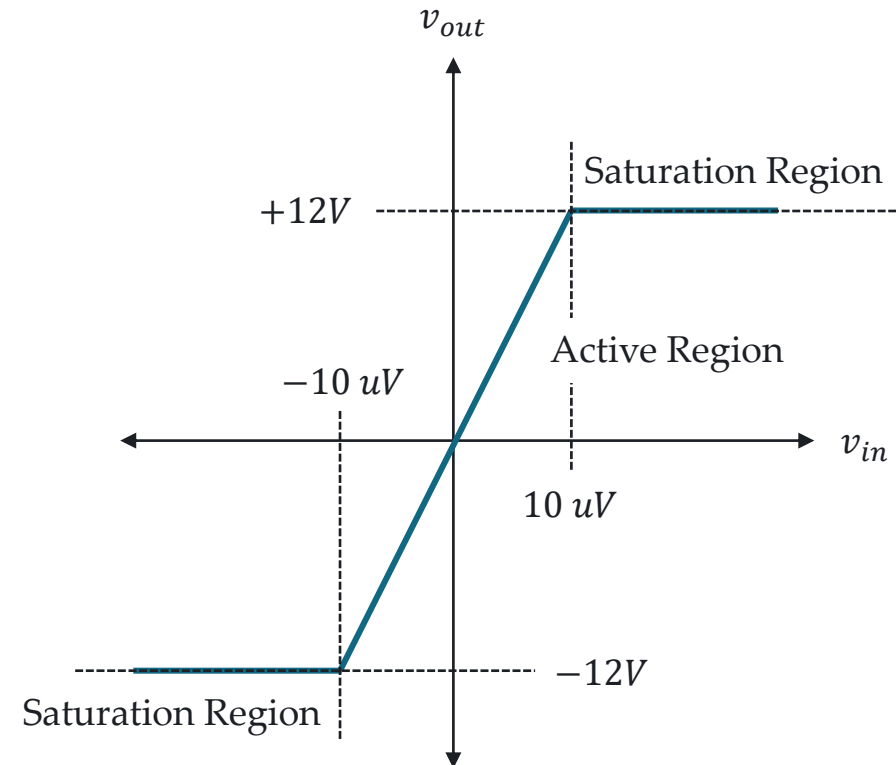


NON-INVERTING OP-AMP



NON-INVERTING OP-AMP

Abstract representation

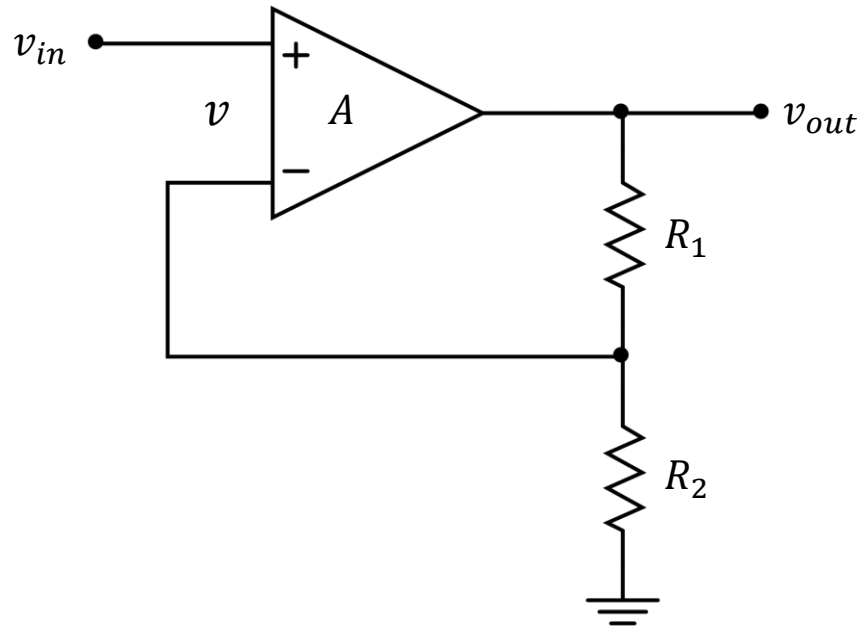


note

A = closed-loop gain


A_o = open-loop gain (∞)

Circuit model

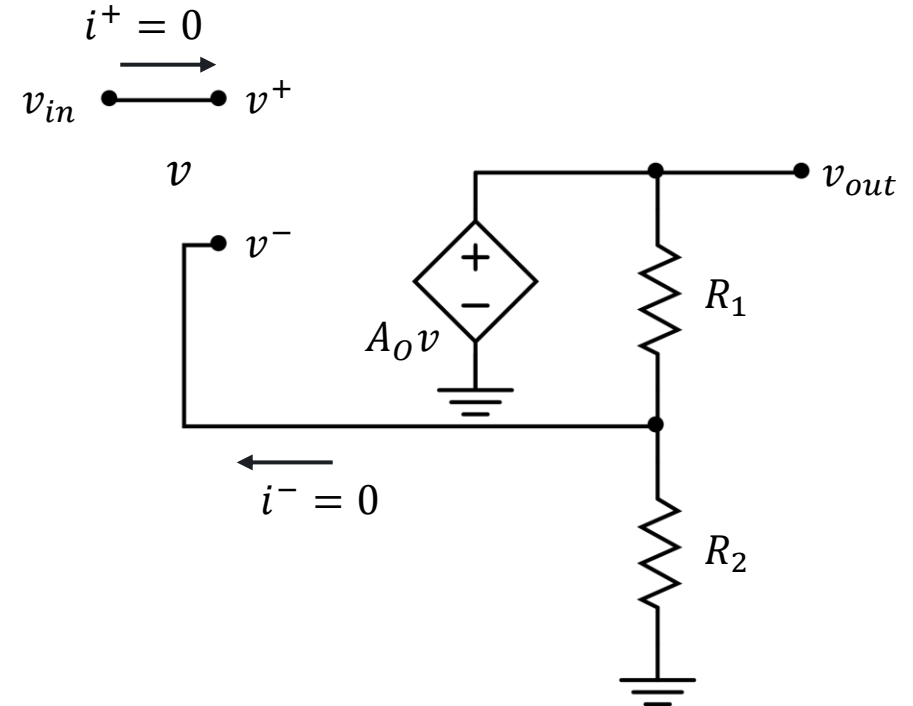

NON-INVERTING OP-AMP

Circuit model

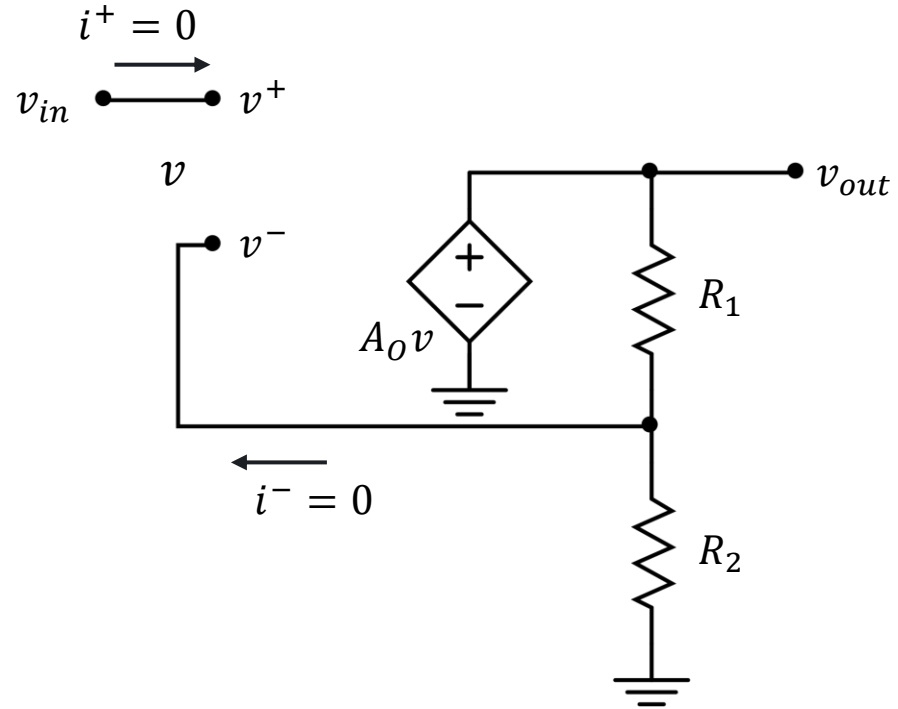

Closed-loop gain

note

A = closed-loop gain


A_O = open-loop gain (∞)



NON-INVERTING OP-AMP

Abstract representation

Closed-loop gain

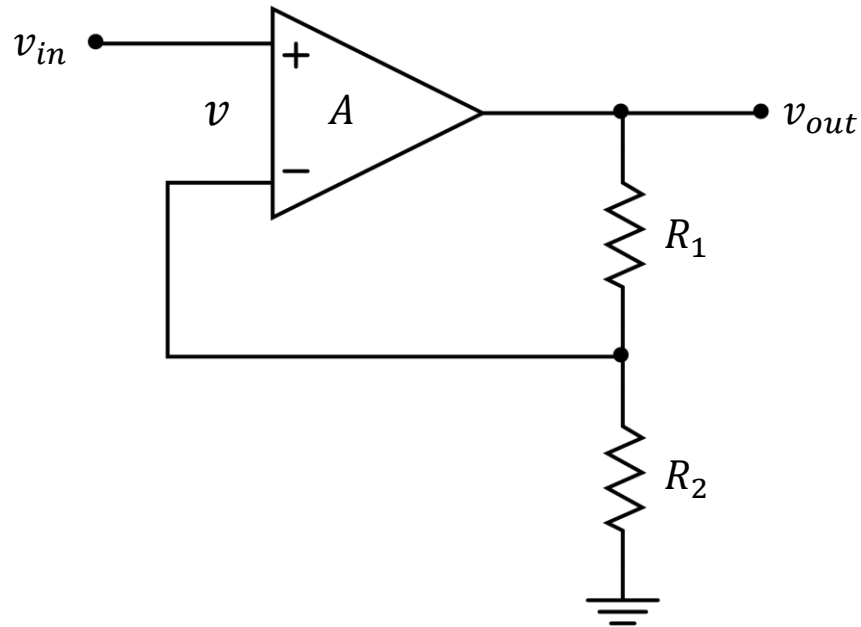

note

A = closed-loop gain


A_o = open-loop gain (∞)



NEGATIVE FEEDBACK


Abstract representation

Differential inputs

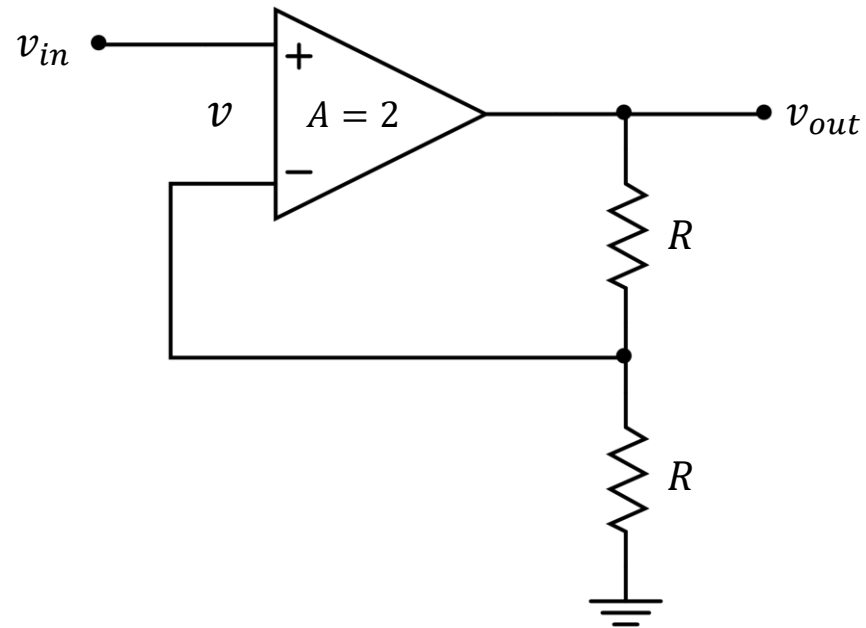

NEGATIVE FEEDBACK

Abstract representation

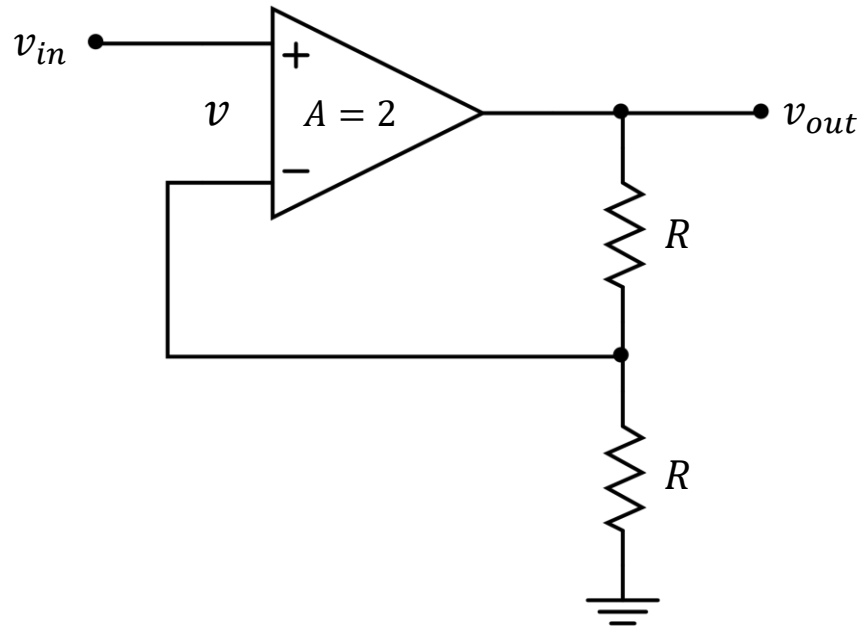

Insightful analysis

- $v^+ \approx v^-$
- $i^+ = 0$
- $i^- = 0$



LABORATORY

