



FIXED-BIAS

JFET DC BIASING

prepared by:

Gyro A. Madrona

Electronics Engineer

TOPIC OUTLINE

Fixed-Bias

- Gate-to-Source Loop
- Drain-to-Source Loop
- Transconductance Curve



FIXED-BIAS



GENERAL RELATIONSHIPS

Gate Current

$$i_G \cong 0$$

Drain Current


$$i_D = I_{DSS} \left(1 - \frac{v_{GS}}{V_P} \right)^2$$

Source Current


$$i_D = i_S$$



FIXED-BIAS CONFIGURATION

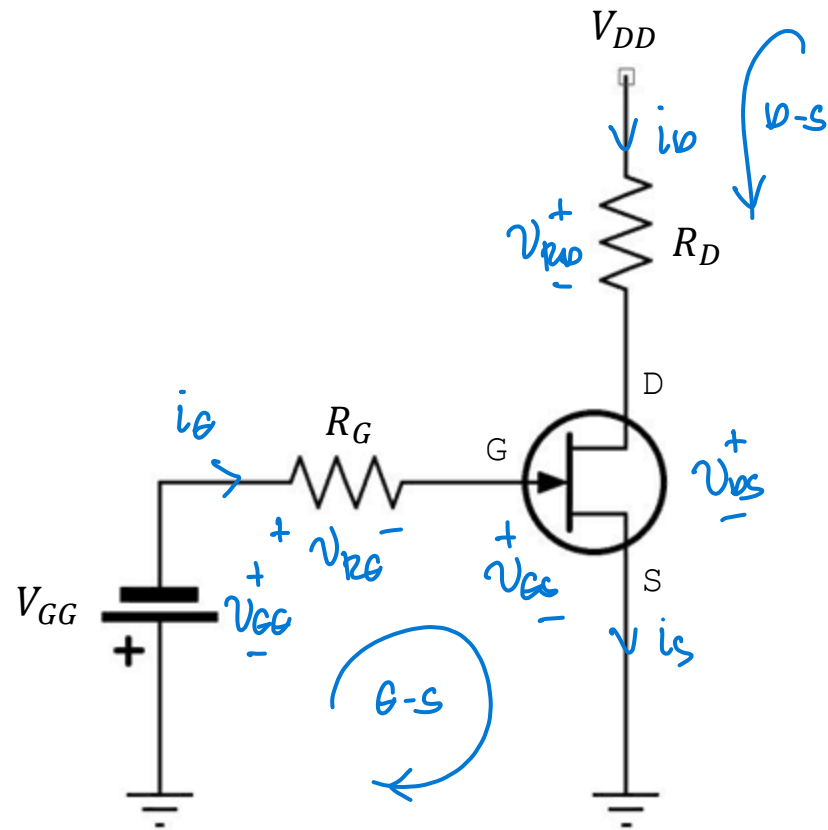

GATE-TO-SOURCE

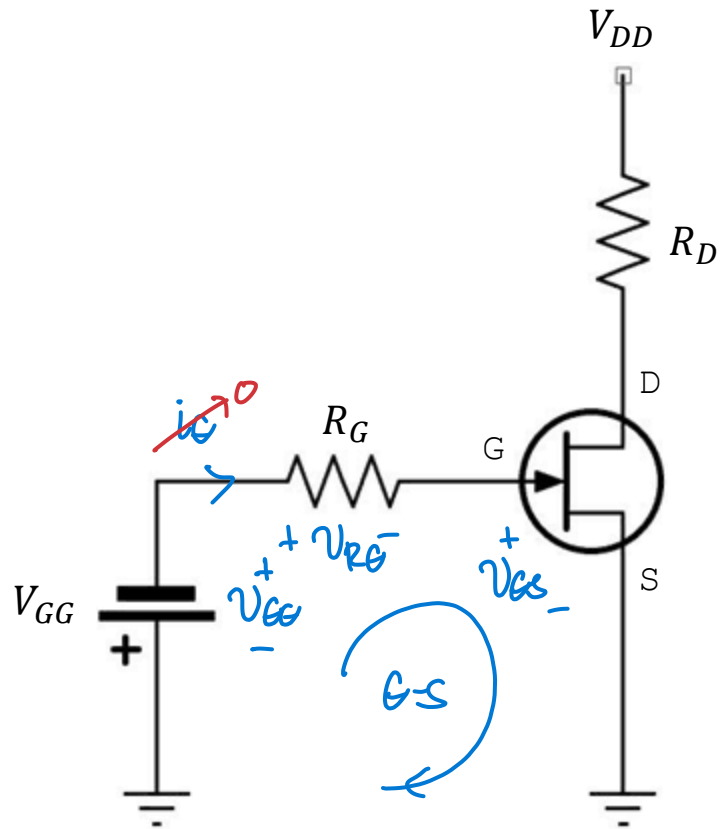

KVL @ G-S

$$-V_{GG} + V_{RG} + \underline{V_{GS}} = 0$$


$$V_{GS} = V_{GG} - V_{RG}$$

$$V_{GS} = -V_{GG} - \cancel{i_G R_G}$$

$$\boxed{V_{GS} = -V_{GG}}$$



DRAIN-TO-SOURCE

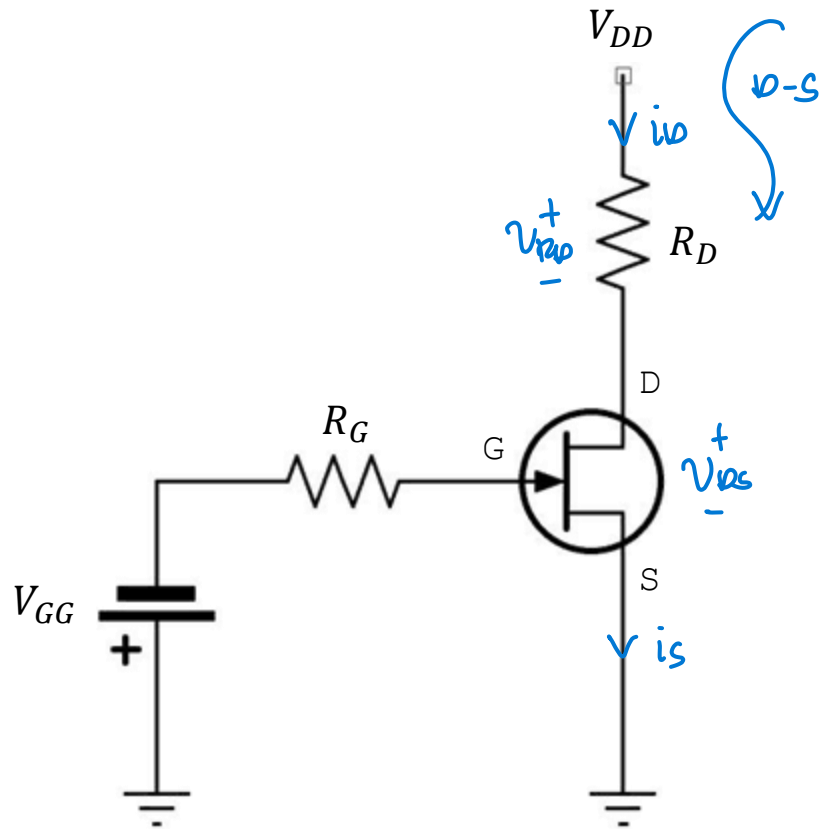

KVL @ D-S


$$-V_{DD} + V_{RD} + \underline{V_{DS}} = 0$$

$$V_{DS} = -V_{DD} - V_{RD}$$

$$V_{DS} = -V_{DD} - i_D R_D$$



EXERCISE

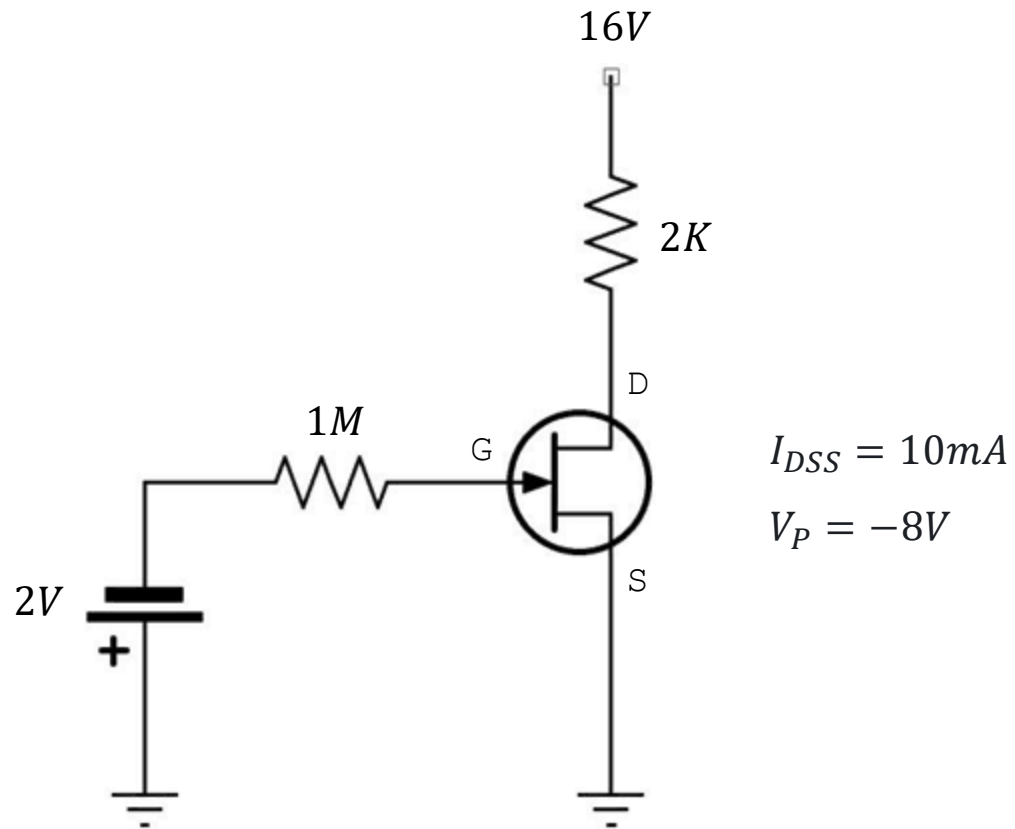


For the given network, determine the following :

- Gate-source voltage (v_{GSQ})
- Source voltage (v_S)
- Gate voltage (v_G)
- Drain current (i_{DQ})
- Drain-source voltage (v_{DS})
- Drain voltage (v_D)

and sketch the transconductance curve.



EXERCISE

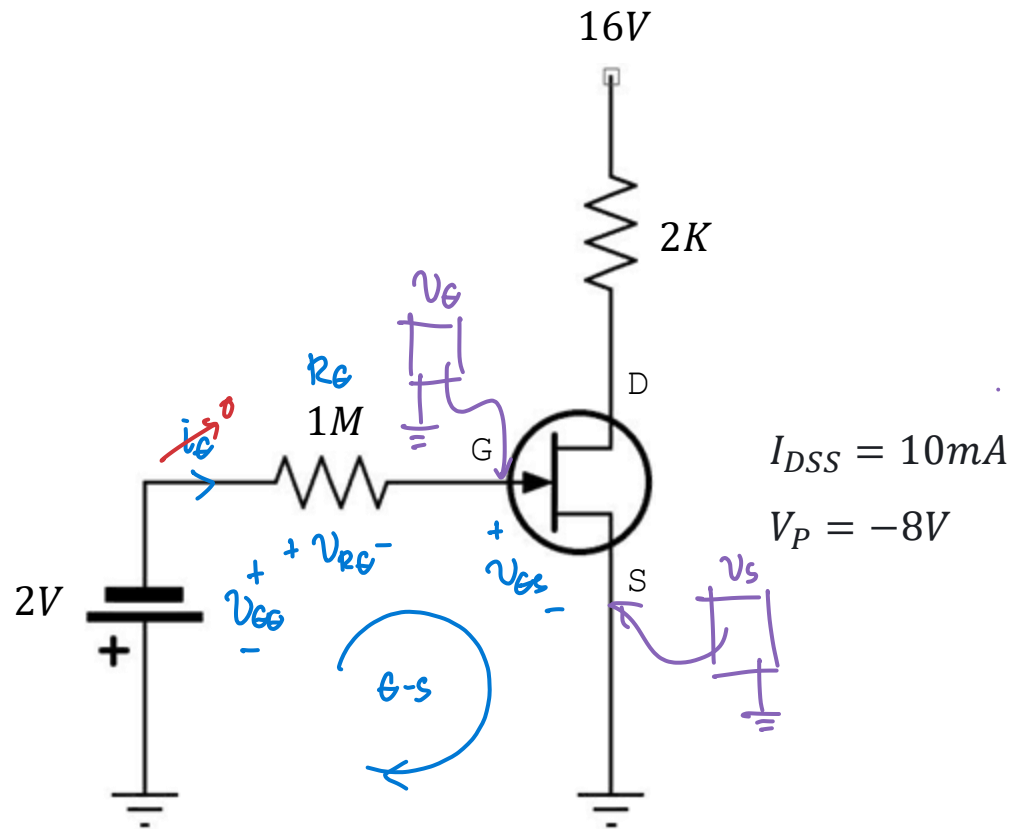

Solution

KVL @ G-S

$$-V_{GG} + V_{RG} + \underline{V_{GS}} = 0$$

$$V_{GS} = V_{GG} - \cancel{V_{RG}}^0$$

$$V_{GS} = -V_{GG}$$

$$\boxed{V_{GS} = -2\text{V}}$$

ans

$$\boxed{V_G = 0}$$

ans


Node Method

$$V_{GS} = V_G - \cancel{V_S}^0$$

$$\boxed{V_G = -2\text{V}}$$

ans

EXERCISE

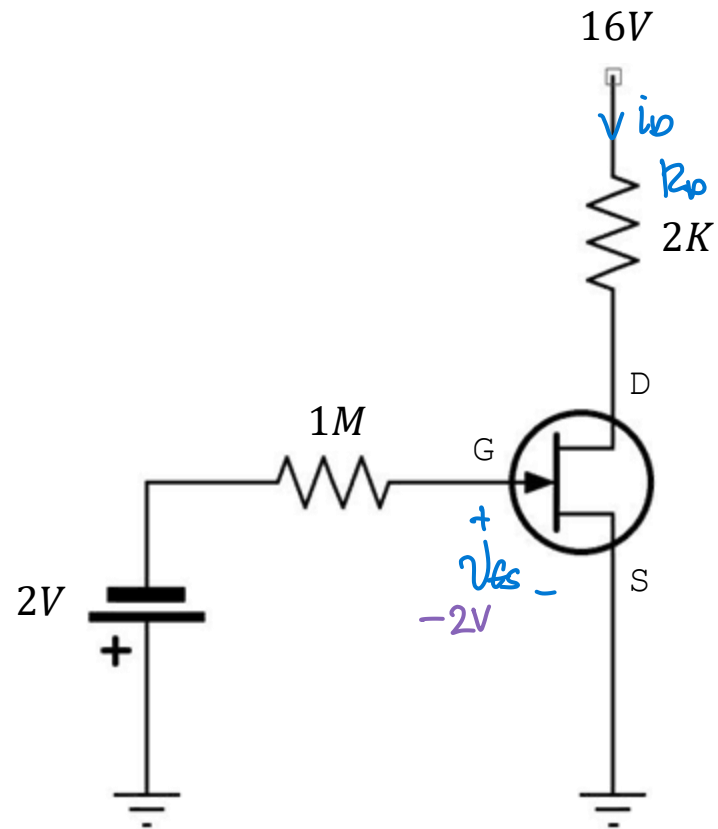

$$I_{DSS} = 10mA$$

$$V_P = -8V$$

Solution

Shockley's Equation


$$i_o = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$i_o = 10m \left(1 - \frac{-2}{-8}\right)^2$$

$$i_o = 5.63mA$$

Ans

EXERCISE

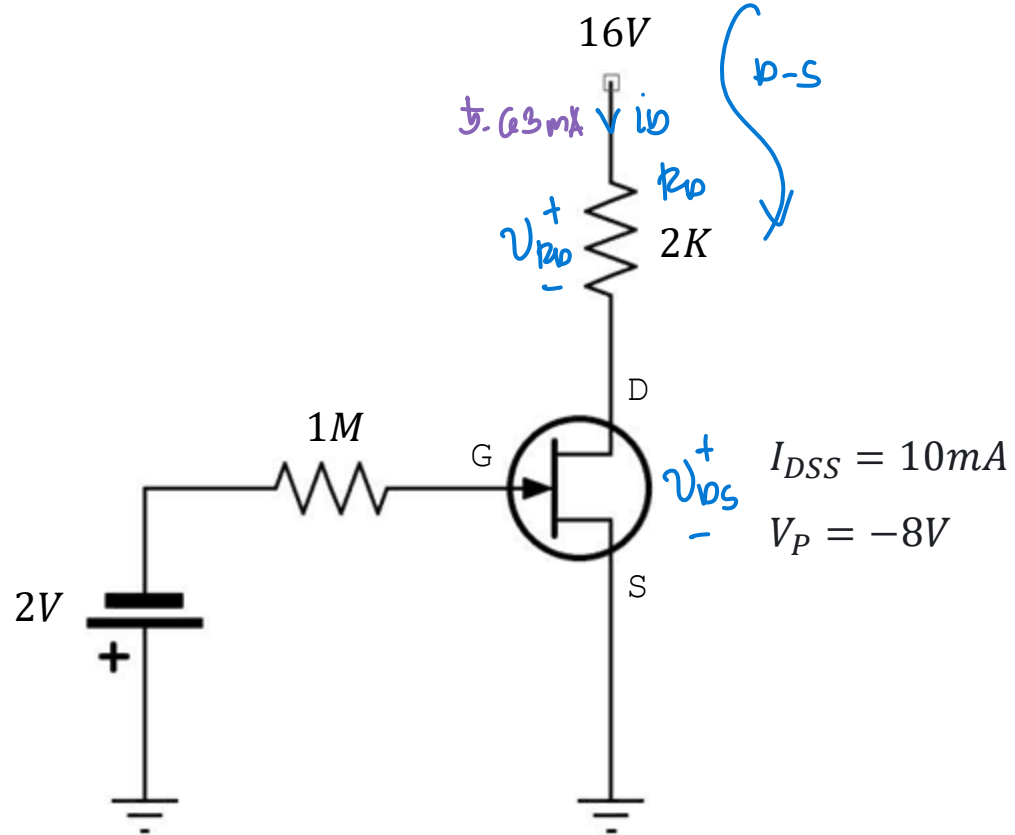

Solution

KVL @ D-S

$$-V_{DD} + V_{RD} + \underline{V_{DS}} = 0$$

$$V_{DS} = V_{DD} - V_{RD}$$


$$V_{DS} = V_{DD} - i_D R_D$$

$$V_{DS} = 16 - 5.63m(2k)$$

$$V_{DS} = 4.74 V$$

ans

EXERCISE

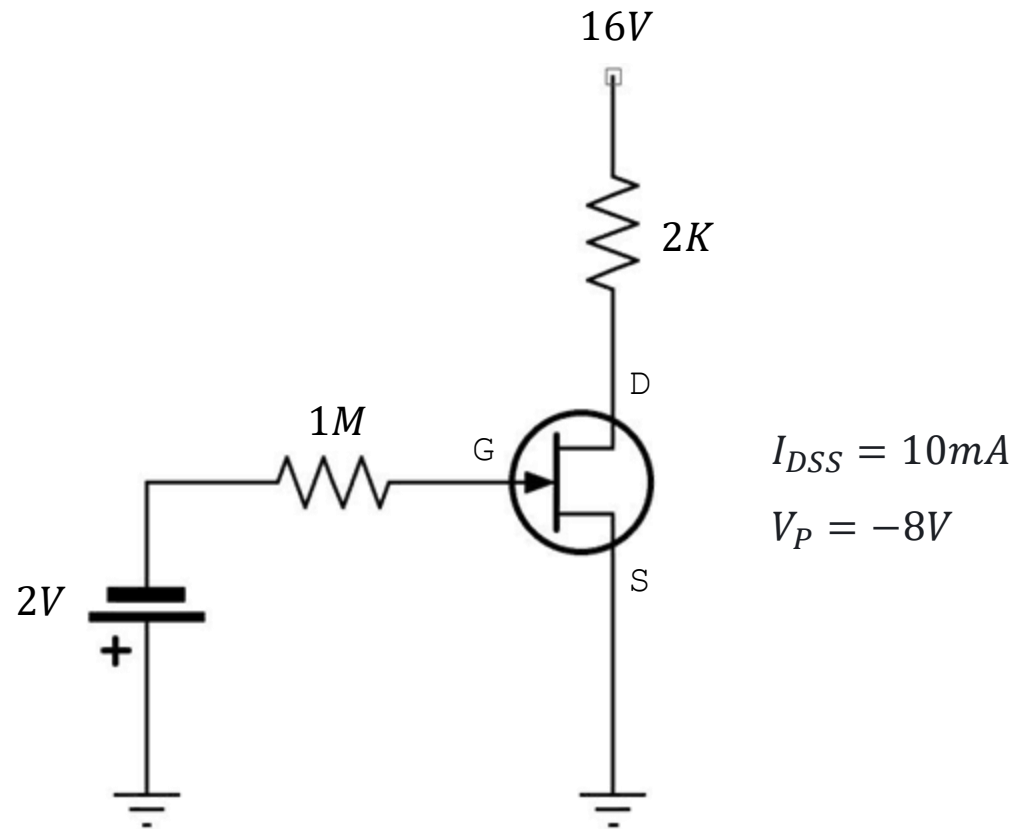

Solution

Transconductance Curve


$$i_D = \frac{1}{4} I_{DSS} \quad \left| \quad v_{GS} = \frac{1}{2} V_P \right.$$

$$i_D = \frac{1}{4} (10\text{mA}) \quad \left| \quad v_{GS} = -4\text{V} \right.$$

$$i_D = 2.5\text{mA} \quad \left| \quad v_{GS} = -4\text{V} \right.$$



EXERCISE

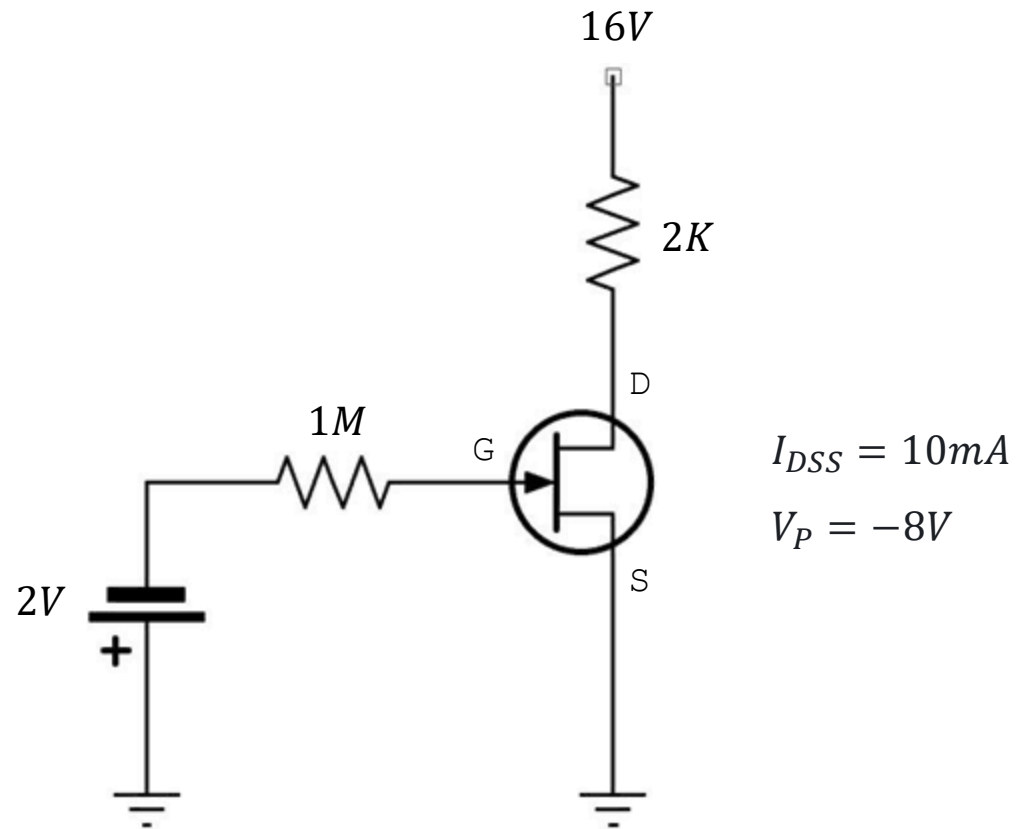

Solution

Transconductance Curve


$$v_{gs} = 0.3V_p \mid i_D = \frac{1}{2} I_{DSS}$$

$$v_{gs} = 0.3(-8) \mid i_D = 5\text{mA}$$

$$v_{gs} = -2.4\text{V} \mid i_D = 5\text{mA}$$



TRANSCONDUCTANCE CURVE

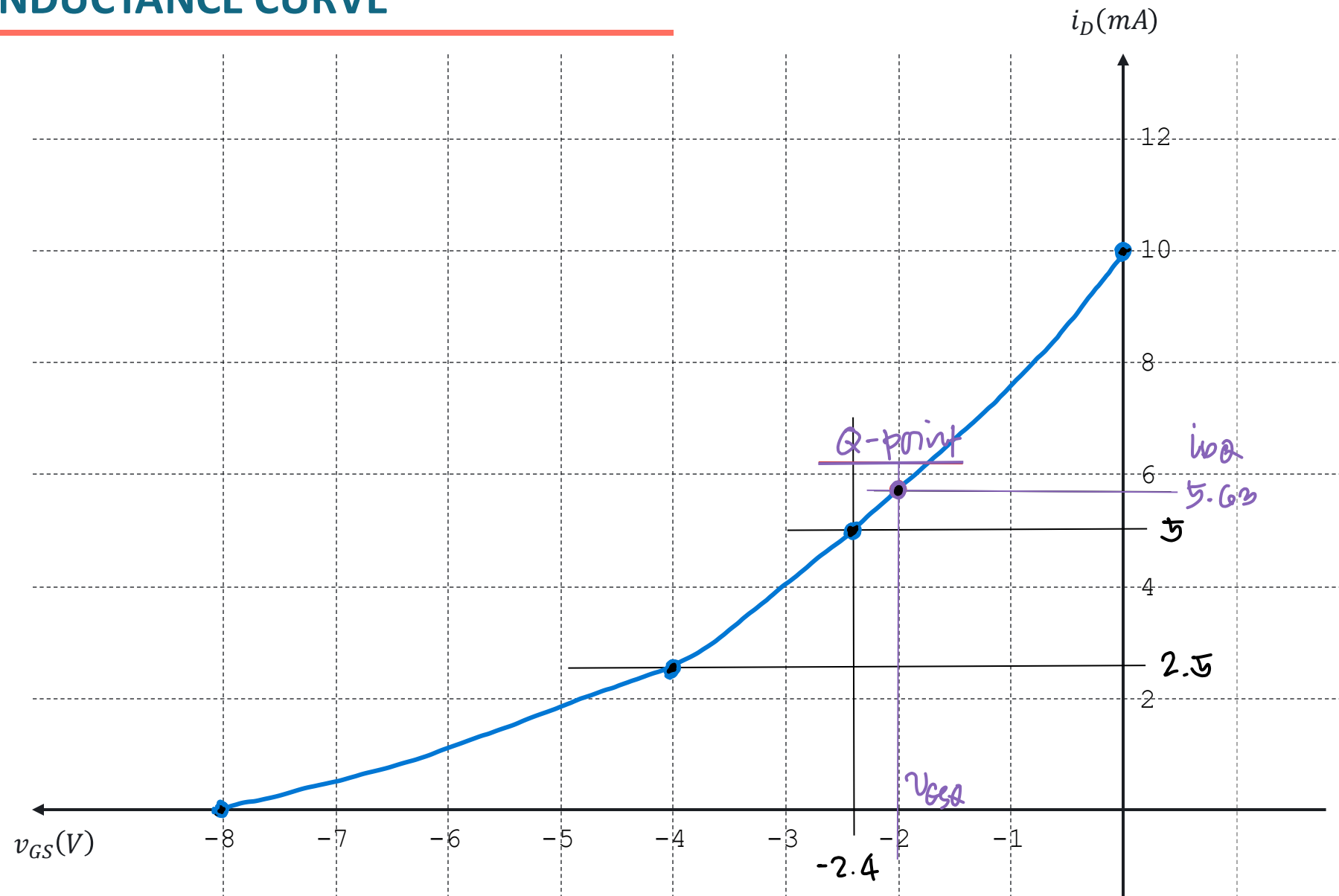

LABORATORY

