



DATAFLOW MODELING

VERILOG DESIGN STYLE

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Bitwise Operator

Dataflow Modeling



BITWISE OPERATORS



BITWISE NOT

```
wire a,b;
```






```
wire [3:0] x,y;
```

not (\sim)

```
a = ~b;
```

```
x = ~y;
```

implementation

 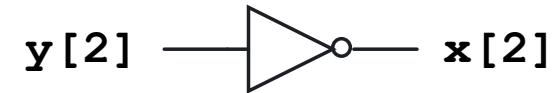  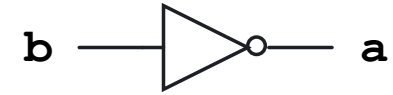

BITWISE OR

```
wire a,b,c;
```

```
wire [3:0] w,x,y;
```

or (|)



```
a = b | c;
```

```
x = w | y;
```

Set bits

	w	0	0	1	0	
(mask)	y	0	1	0	1	1-set
	x	0	1	1	1	

implementation

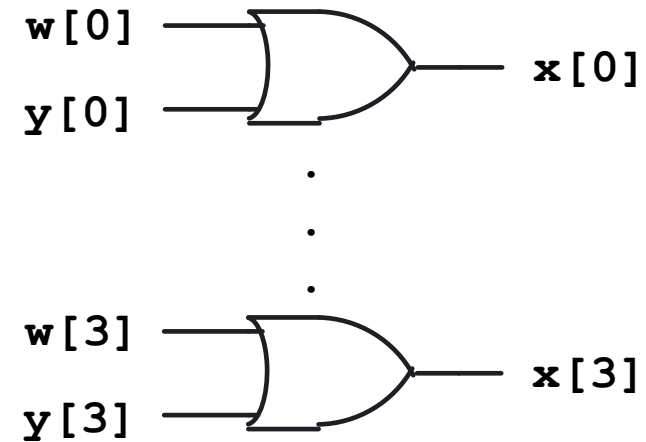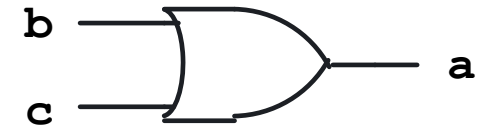

BITWISE AND

```
wire a,b,c;
```

```
wire [3:0] w,x,y;
```

and (&)


```
a = b & c;
```

```
x = w & y;
```


Reset bits

	w	1101	
(mask)	y	0110	0-reset
	x	0100	

implementation

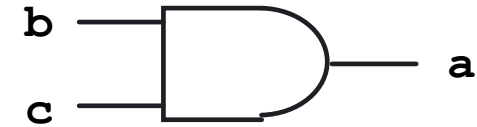

⋮

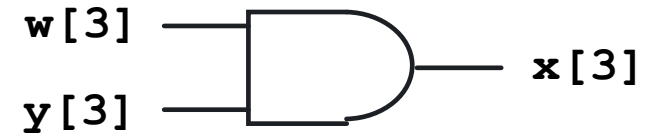

BITWISE XOR

```
wire a,b,c;
```

```
wire [3:0] w,x,y;
```

xor (^)



```
a = b ^ c;
```

```
x = w ^ y;
```

Flip bits

	w	0	1	0	1	
(mask)	y	0	1	1	0	1-flip
	x	0	0	1	1	

implementation

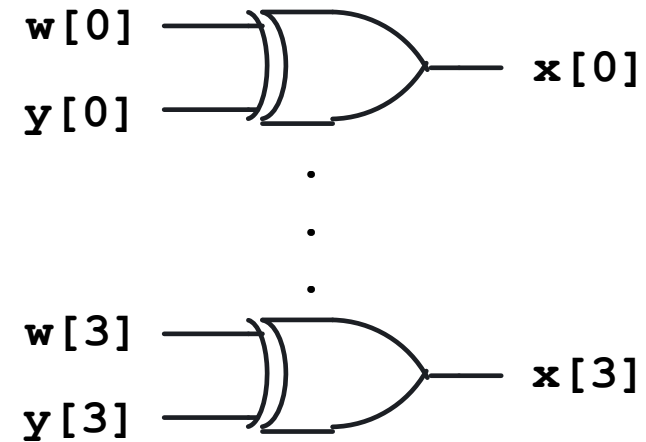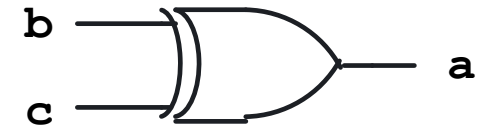

BITWISE NOR

```
wire a,b,c;
```

```
wire [3:0] w,x,y;
```

nor (~|)



```
a = b ~| c;
```

```
x = w ~| y;
```

Reset and flip bits

	w	0101	<i>0-flip</i>
(mask)	y	0110	<i>1-reset</i>
	x	1001	

implementation

  

BITWISE NAND

```
wire a,b,c;
```

```
wire [3:0] w,x,y;
```

nand (~&)



```
a = b ~& c;
```

```
x = w ~& y;
```

Set and flip bits

	w	0101	<i>0-set</i>
<i>(mask)</i>	y	1001	<i>1-flip</i>
	<hr/>		
	x	1110	

implementation

  

BITWISE XNOR

```
wire a,b,c;
```

```
wire [3:0] w,x,y;
```

xnor (\sim^{\wedge})



```
a = b ~^ c;
```

```
x = w ~^ y;
```

Equality check

	w	0101
(mask)	y	0100
	<hr/>	
	x	1110
		1-equal

implementation

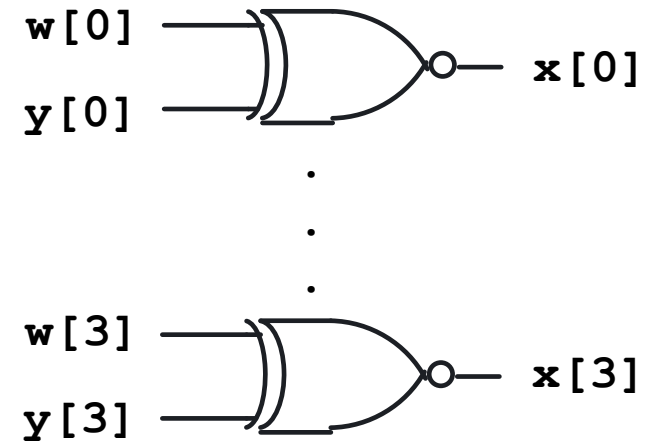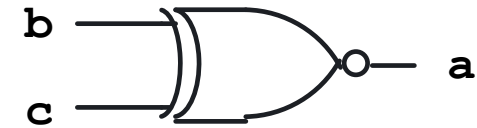


DATAFLOW MODELING



XOR MODULE

module name

xor_gate

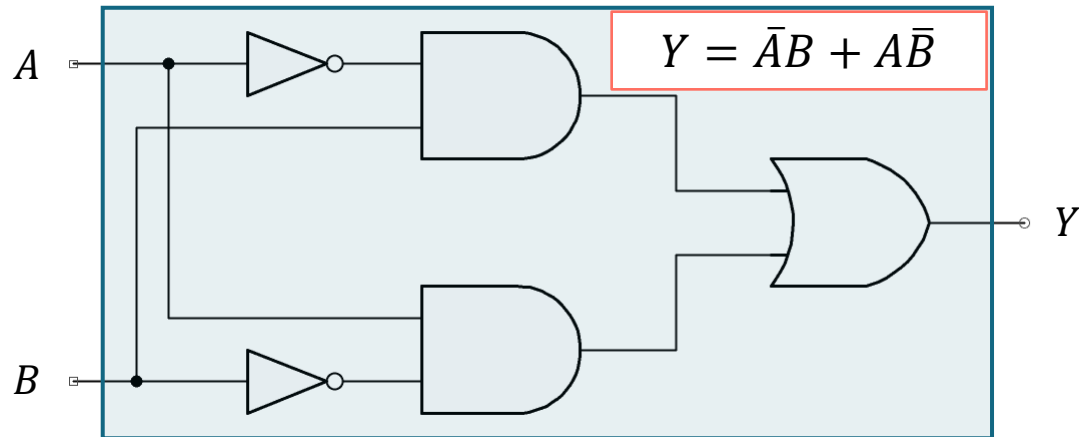

```
module xor_gate(Y,A,B) ;
```

```
    input A,B;
```

```
    output Y;
```

```
    assign Y = (~A & B) | (A & ~B) ;
```

```
endmodule
```

The assign keyword is used for continuous assignments – it continuously drives a value onto a net based on an expression.


Dataflow modeling describes a circuit using continuous assignments and requires knowing the logic expression of the design.



XNOR MODULE

module name

xnor_gate

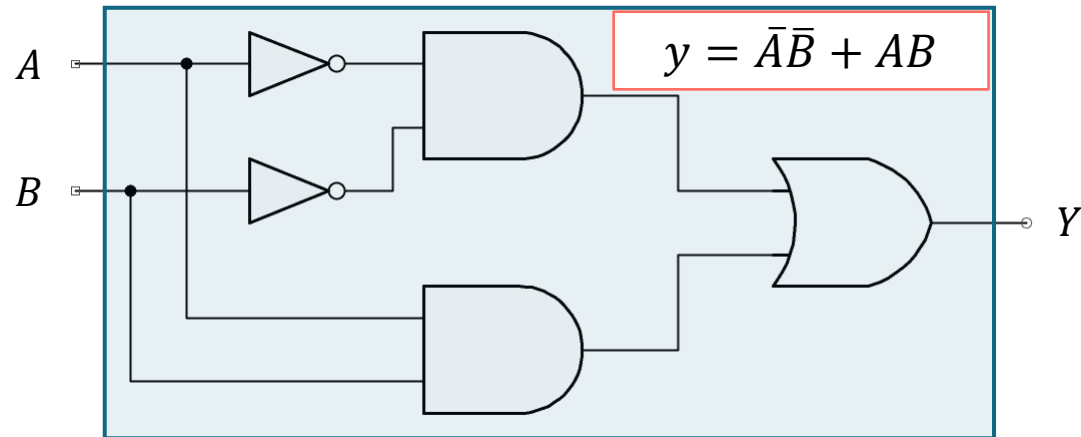

```
module xnor_gate(Y,A,B) ;
```

```
    input A,B;
```

```
    output Y;
```

```
    assign Y = (~A & ~B) | (A & B) ;  
endmodule
```

Dataflow modeling describes a circuit using continuous assignments and requires knowing the logic expression of the design.




HALF-ADDER MODULE

module name

// Verilog code

half_adder

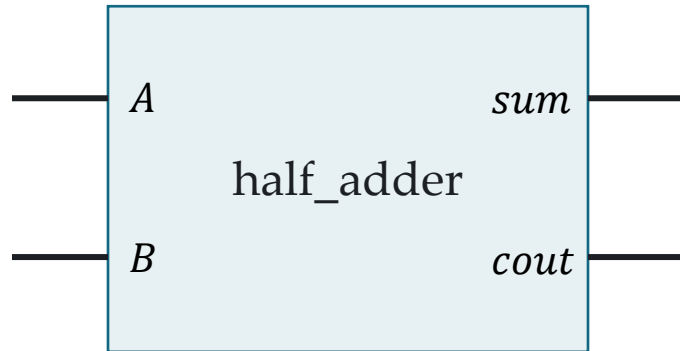

$$cout = AB$$

$$sum = A \oplus B$$




FULL-ADDER MODULE

module name

// Verilog code

half_adder

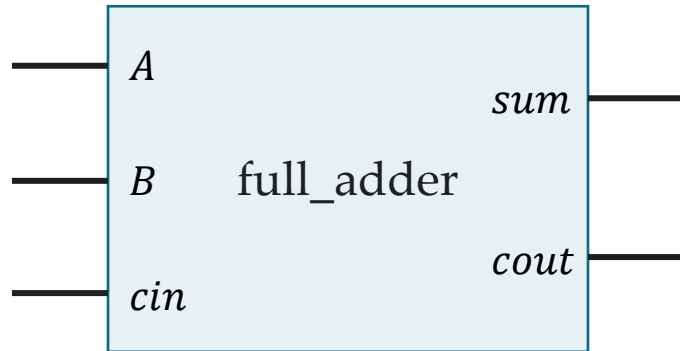

$$cout = cin(A \oplus B) + AB$$

$$sum = cin \oplus A \oplus B$$



LABORATORY

