



SELF-BIAS

JFET DC BIASING

prepared by:

Gyro A. Madrona

Electronics Engineer

TOPIC OUTLINE

Self-Bias

- Gate-to-Source Loop
- Drain-to-Source Loop
- Transconductance Curve



SELF-BIAS



GENERAL RELATIONSHIPS

Gate Current

$$i_G \cong 0$$

Drain Current


$$i_D = I_{DSS} \left(1 - \frac{v_{GS}}{V_P} \right)^2$$

Source Current


$$i_D = i_S$$



SELF-BIAS CONFIGURATION

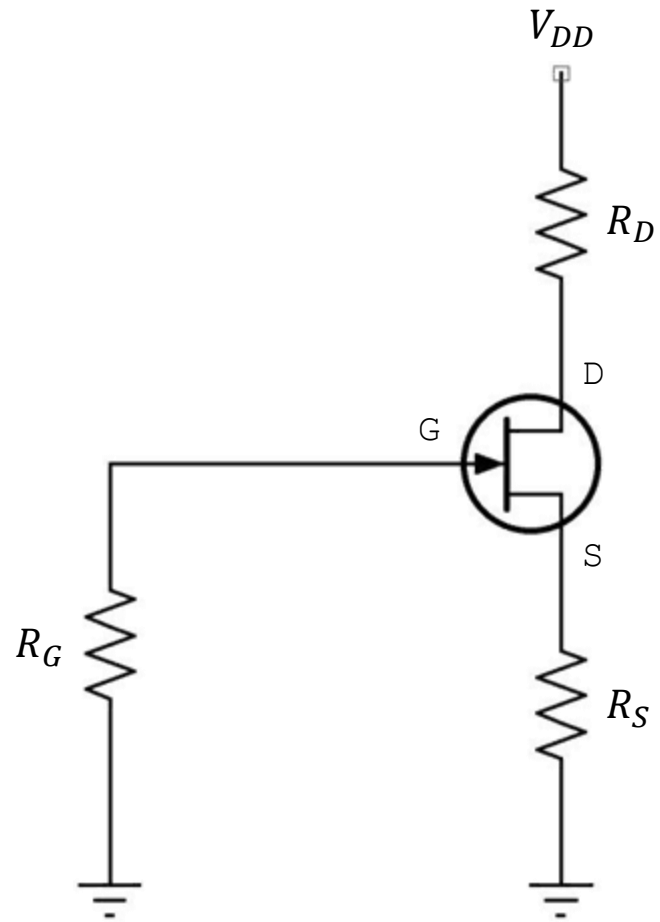

GATE-TO-SOURCE

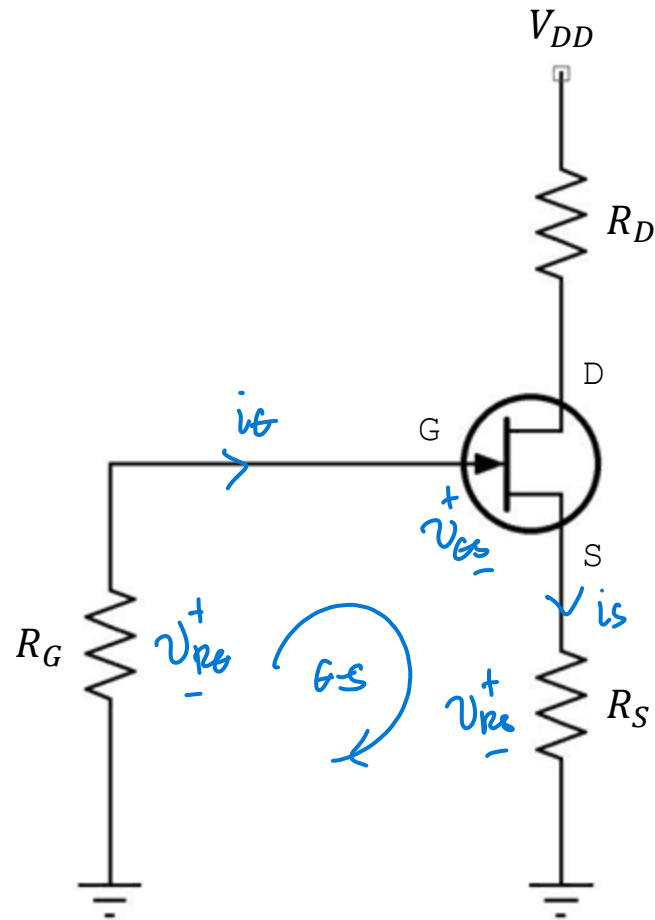KVL @ G-S

$$-V_{RG} + \underline{V_{GS}} + V_{PS} = 0$$

$$V_{GS} = V_{RG} - V_{RS}$$

$$V_{GS} = i_G R_G - i_S R_S$$


$$V_{GS} = -i\omega R_S$$

Shockley's equation

$$i_b = I_{BSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$



DRAIN-TO-SOURCE

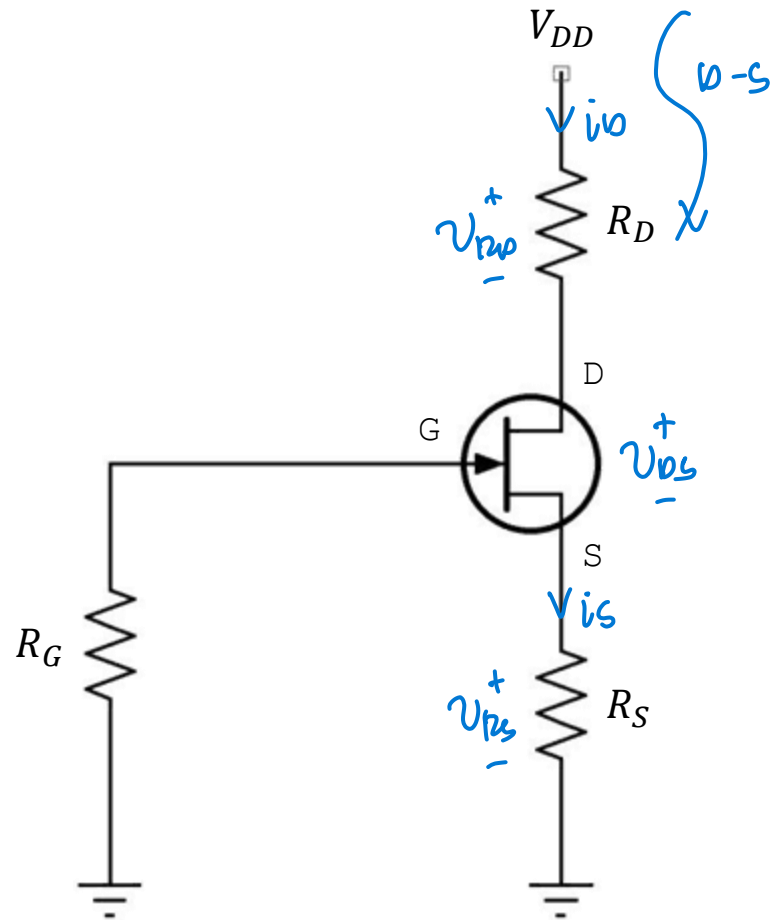

KVL @ D-S

$$-V_{DD} + V_{RD} + \underline{V_{DS}} + V_{RS} = 0$$


$$V_{DS} = V_{DD} - V_{RD} - V_{RS}$$

$$V_{DS} = V_{DD} - i_D R_D - i_S R_S$$

$$V_{DS} = V_{DD} - i_D (R_D + R_S)$$



EXERCISE

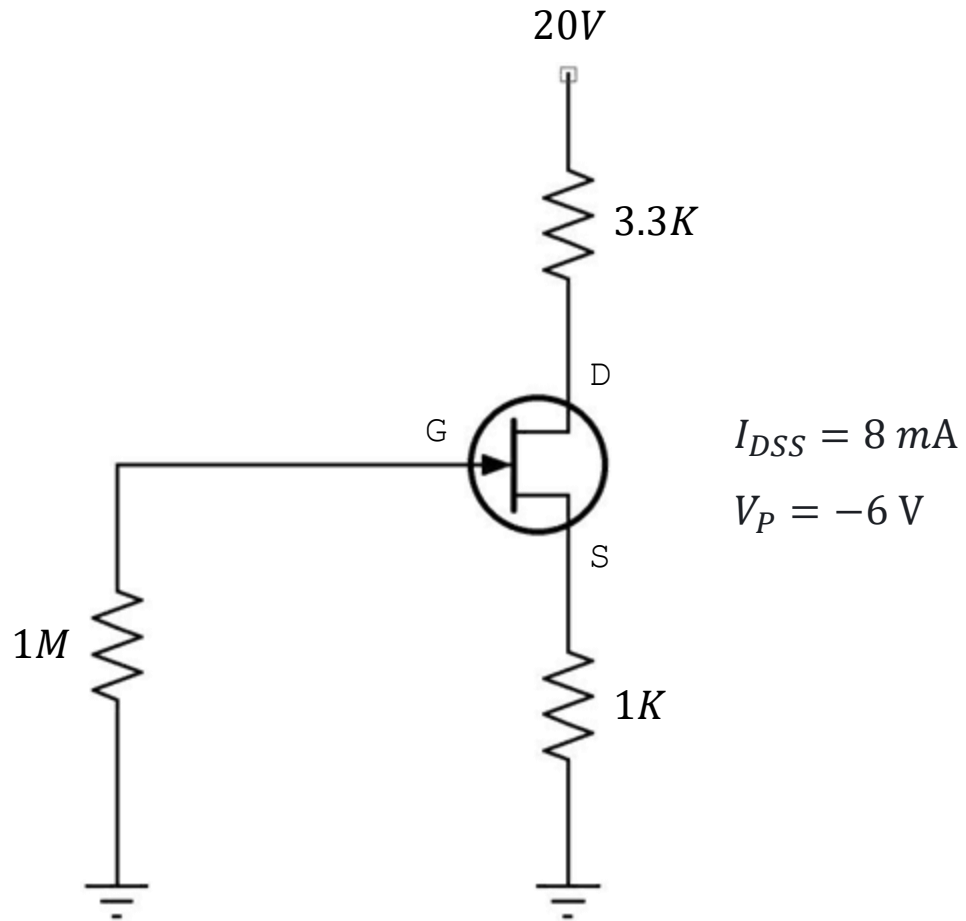


For the given network, determine the following :

- Gate-source voltage (v_{GSQ})
- Drain current (i_{DQ})
- Drain-source voltage (v_{DS})
- Source voltage (v_S)

and sketch the transconductance curve.



EXERCISE

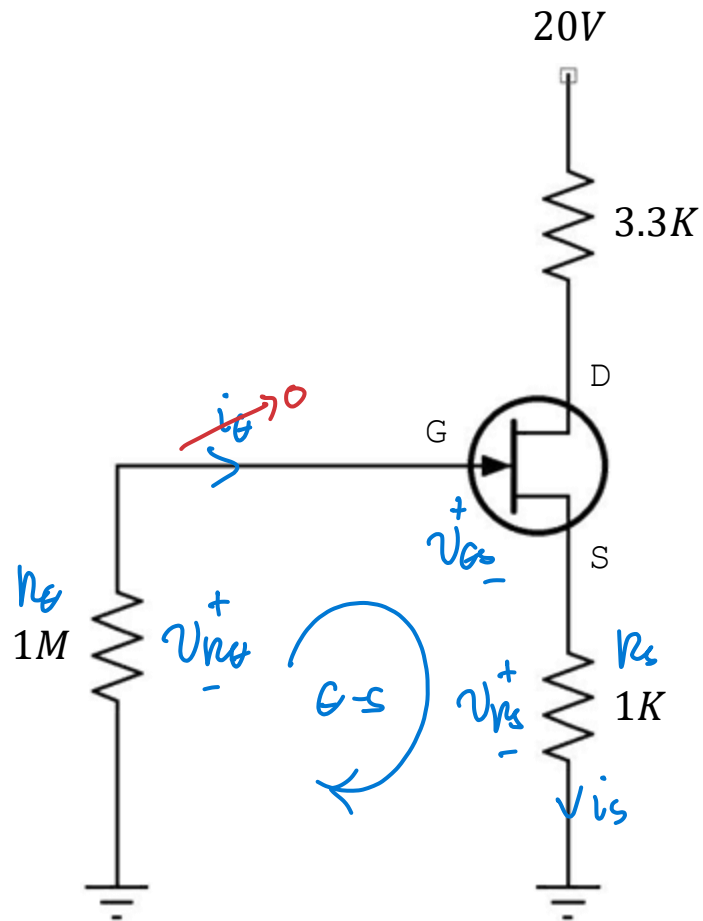

$$I_{DSS} = 8 \text{ mA}$$

$$V_P = -6 \text{ V}$$

Solution

KVL @ G-S

$$-\cancel{V_{DG}}^0 + V_{GS} + \cancel{V_{RS}}^{i_D R_S} = 0$$

$$V_{GS} = -\cancel{i_D R_S}$$

$$V_{GS} = -I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 R_S$$


$$V_{GS} = -I_{DSS} R_S \left(1 - 2 \frac{V_{GS}}{V_P} + \frac{V_{GS}^2}{V_P^2}\right)$$

$$V_{GS} = -I_{DSS} R_S + 2 I_{DSS} R_S \frac{V_{GS}}{V_P} - I_{DSS} R_S \frac{V_{GS}^2}{V_P^2}$$

$$V_{GS} = -(8\text{m} \cdot 1\text{k}) + 2(8\text{m} \cdot 1\text{k}) \frac{V_{GS}}{-6} - (8\text{m} \cdot 1\text{k}) \frac{V_{GS}^2}{(-6)^2}$$

$$\cancel{V_{GS}}^0 = -8 - 2.67 \cancel{V_{GS}} - 0.22 \cancel{V_{GS}}^2$$

EXERCISE

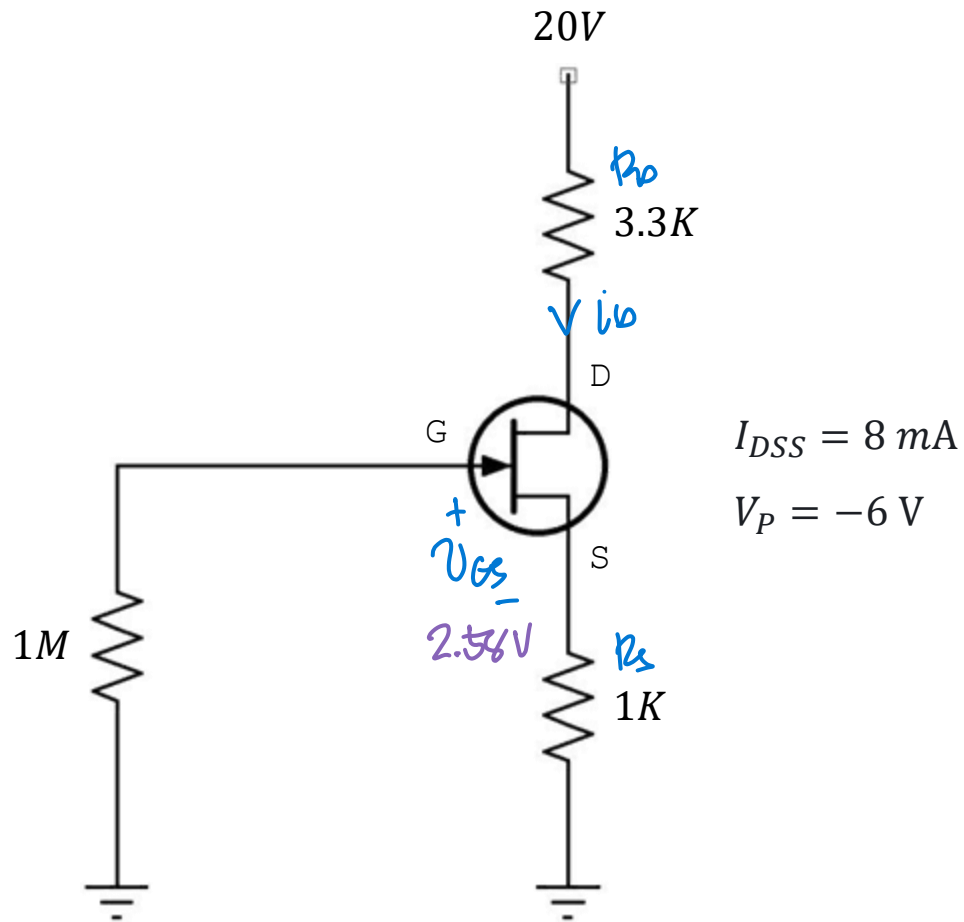

Solution

$$0 = -8 - 3.67 V_{GS} - 0.22 V_{GS}^2$$

$$V_{GS} = -14.10 \text{ V}$$

$$V_{GSQ} = -2.58 \text{ V}$$

ans

Shockley's equation

$$i_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$


$$i_D = 8 \text{ mA} \left(1 - \frac{-2.58}{-6} \right)^2$$

$$i_{DQ} = 2.60 \text{ mA}$$

ans



EXERCISE

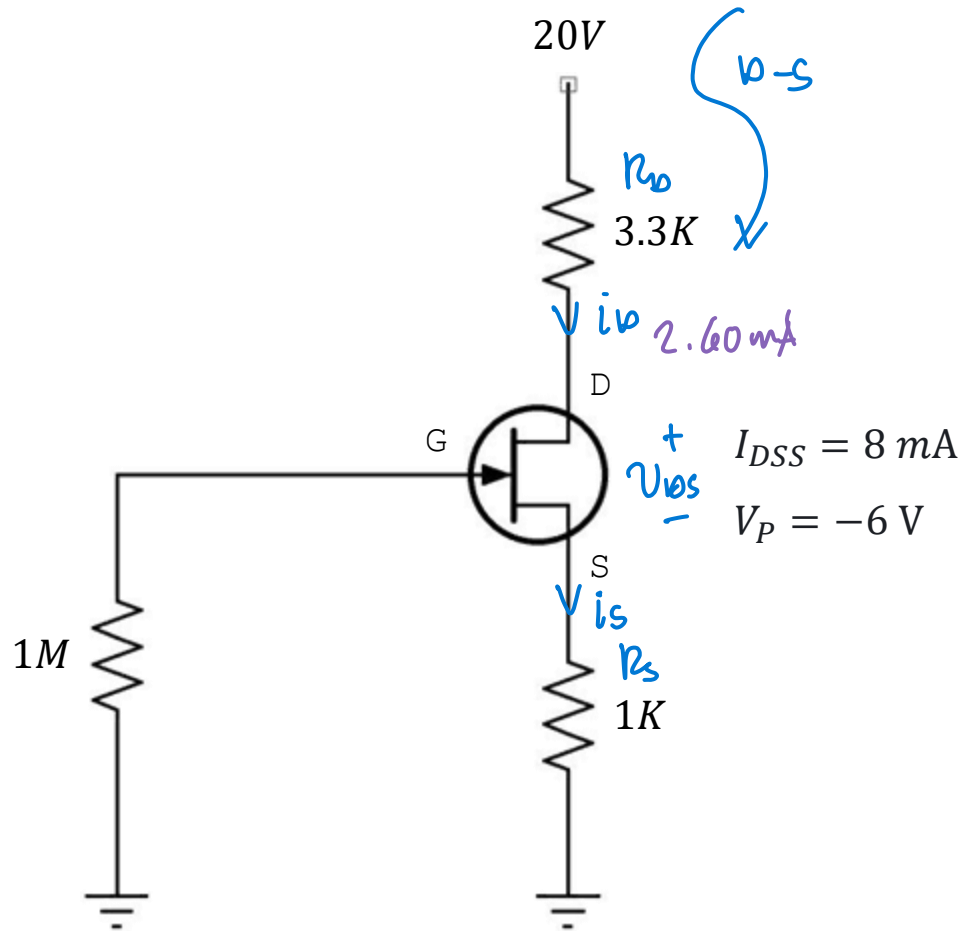

Solution

KVL @ D-S

$$-V_{DD} + V_{RD} + \underline{V_{DS}} + V_{RS} = 0$$

$$V_{DS} = V_{DD} - V_{RD} - V_{RS} = 0$$

$$V_{DS} = V_{DD} - i_D R_D - \overset{i_D}{i_S} R_S$$


$$V_{DS} = V_{DD} - i_D (R_D + R_S)$$

$$V_{DS} = 20 - 2.60\text{m}(3.3\text{k} + 1\text{k})$$

$$V_{DS} = 8.82\text{V}$$

ans

EXERCISE

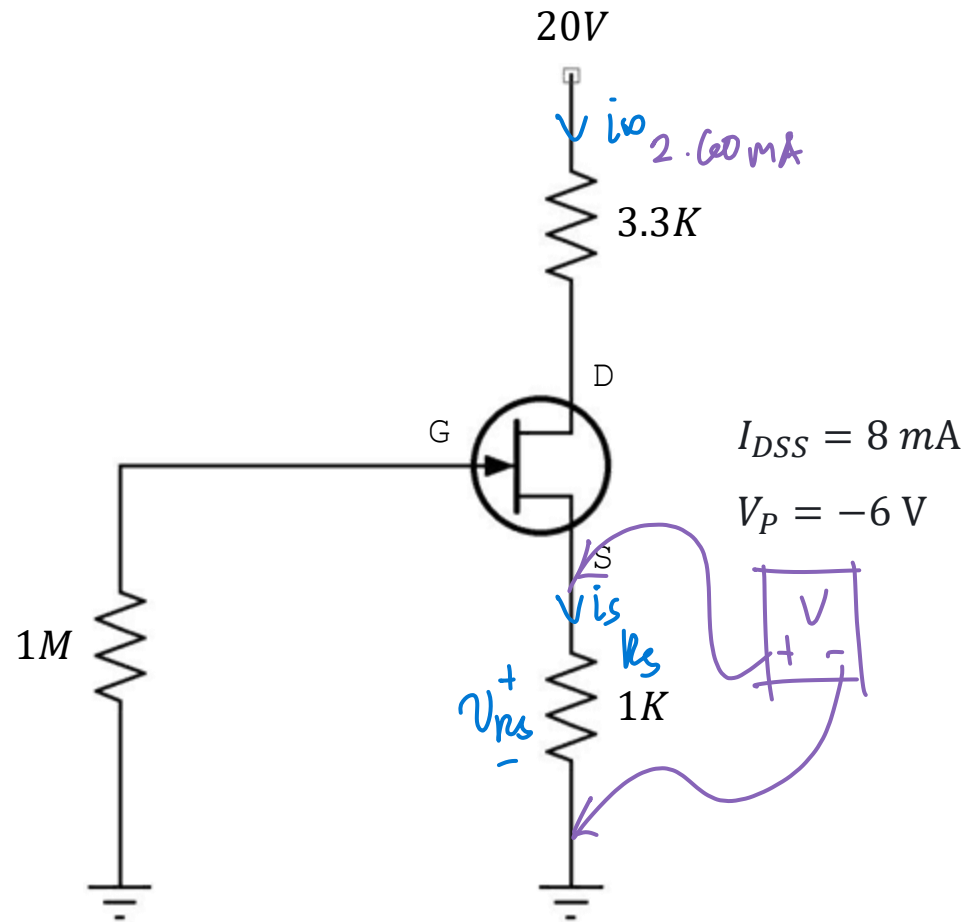

Solution


$$V_{rs} = i_{s} R_s$$

$$V_{rs} = 2.60m(1K)$$

$$V_s = 2.6V$$

Ans

EXERCISE

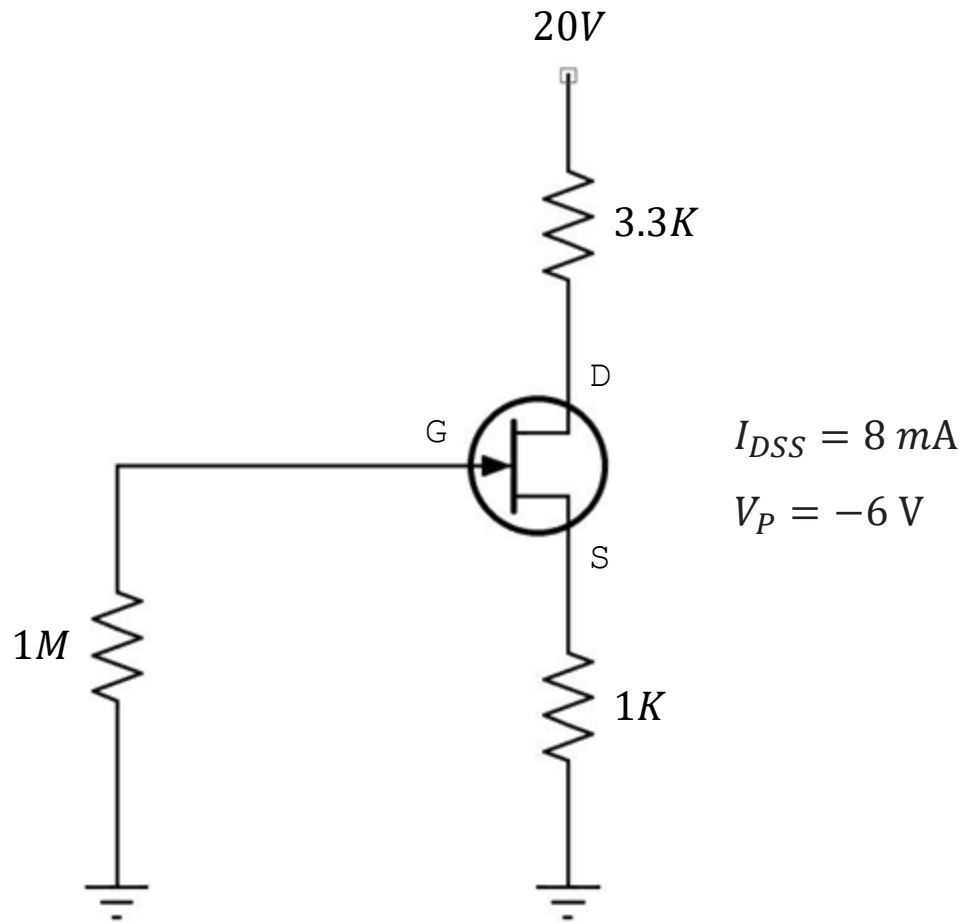

Solution

Transconductance Curve


$$i_D = \frac{1}{4} I_{DSS} \quad \left| \quad v_{GS} = \frac{1}{2} V_P \right.$$

$$i_D = \frac{1}{4} (8\text{ mA}) \quad \left| \quad v_{GS} = \frac{1}{2} (-6\text{ V}) \right.$$

$$\underline{i_D = 2\text{ mA} \quad \left| \quad v_{GS} = -3\text{ V} \right.}$$



EXERCISE

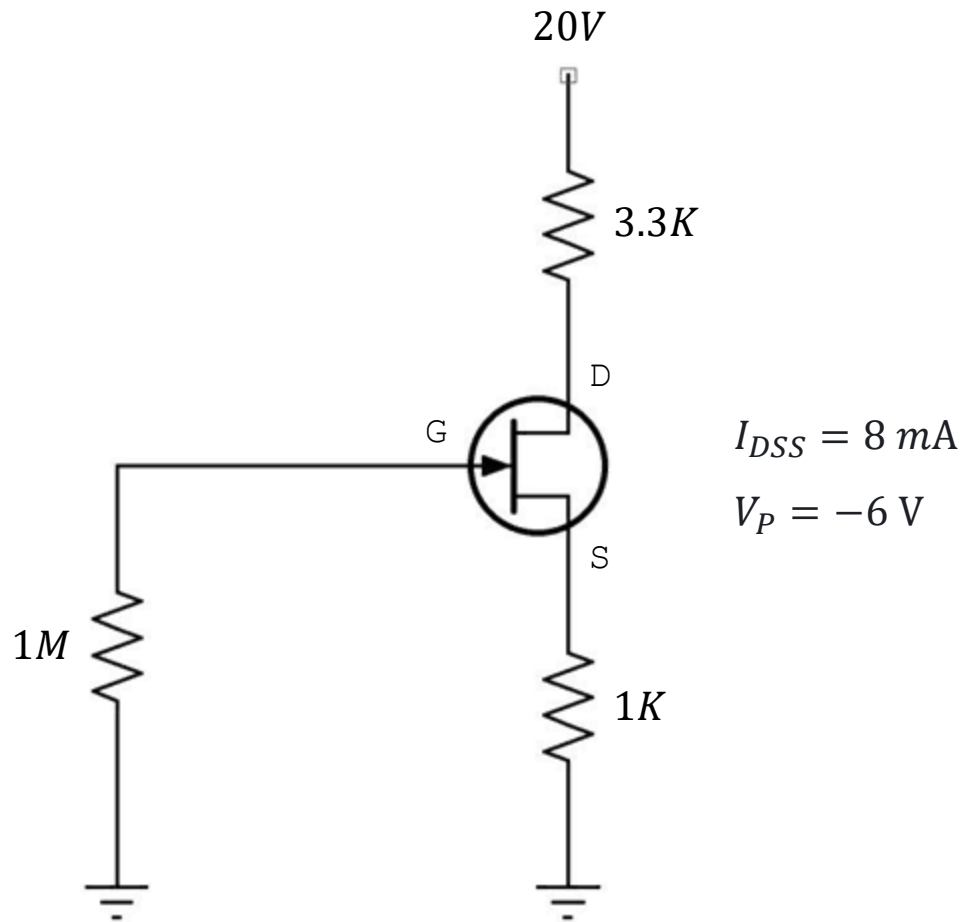

Solution

Transconductance Curve

$$V_{GS} = 0.3 V_P \mid i_D = \frac{1}{2} I_{DSS}$$


$$V_{GS} = 0.3 (-6\text{ V}) \mid i_D = \frac{1}{2} (8\text{ mA})$$

$$\underline{V_{GS} = -1.8\text{ V} \mid i_D = 4\text{ mA}}$$




EXERCISE

Solution

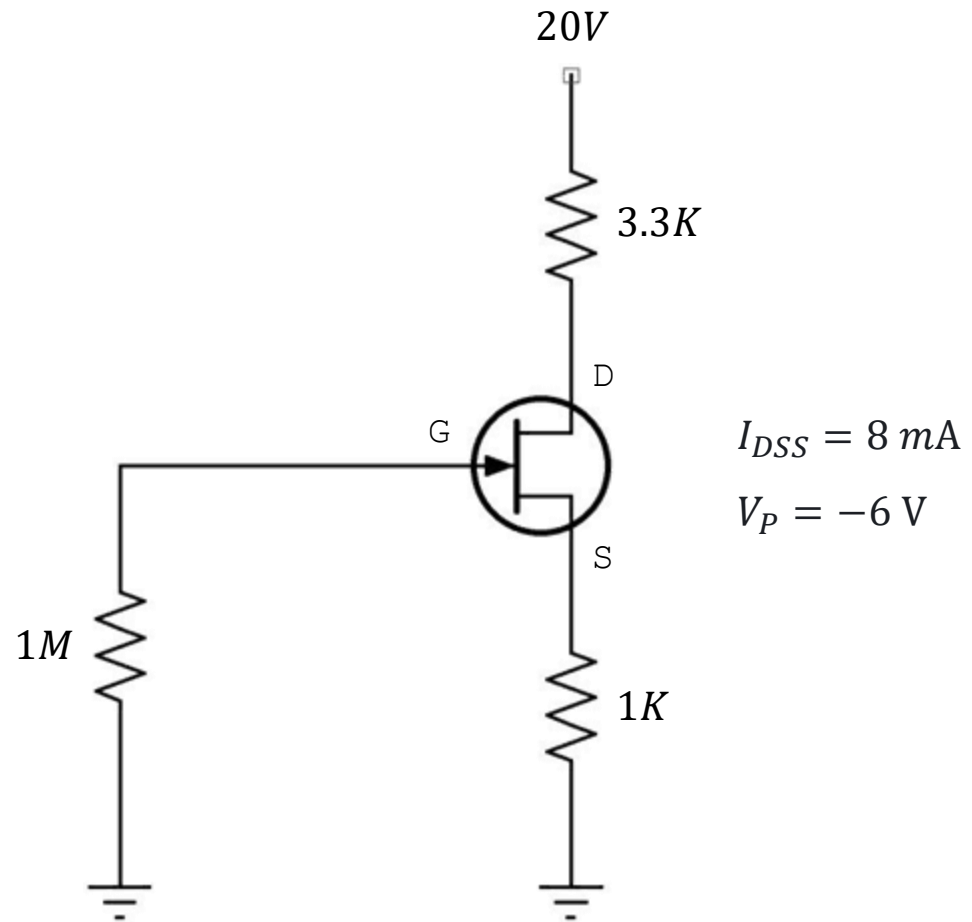

TRANSCONDUCTANCE CURVE
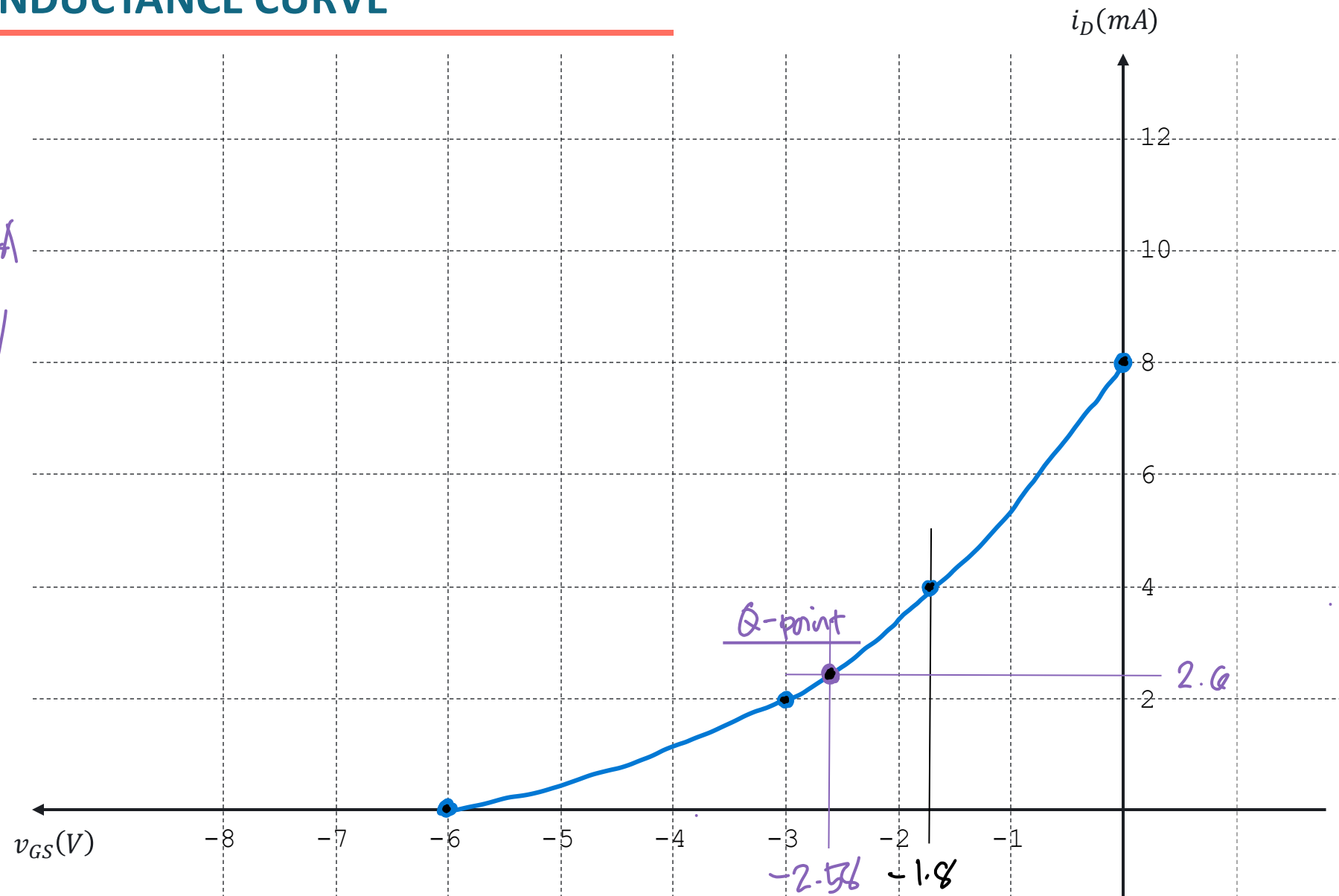
$$I_{DQ} = 2.6 \text{ mA}$$
$$V_{GS} = -2.58 \text{ V}$$



LABORATORY

