

# E-MOSFET AS A DIGITAL SWITCH

## E-MOSFET APPLICATION

---

*prepared by:*

**Gyro A. Madrona**

Electronics Engineer

# TOPIC OUTLINE


The Ohmic Region

Active-load Switching



# OHMIC REGION

Measuring  $R_{DS(on)}$

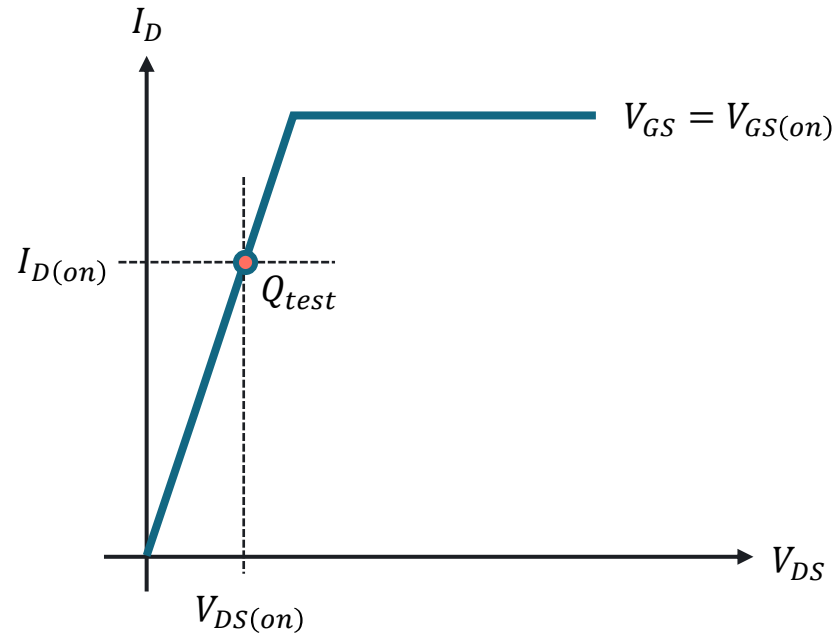

Drain-Source ON Resistance

$$R_{DS(on)} = \frac{V_{DS(on)}}{I_{D(on)}}$$

For instance, at the test point, a VN2406L has  $V_{DS(on)} = 1V$  and  $I_{D(on)} = 100mA$ .

$$R_{DS(on)} = \frac{1V}{100\text{ mA}}$$

$$R_{DS(on)} = 10\Omega$$




## SMALL-SIGNAL E-MOSFETs

Device	$V_{GS(th)}$	$V_{GS(on)}$	$I_{D(on)}$	$R_{DS(on)}$	$I_{D(max)}$	$P_{D(max)}$
VN2406L	1.5V	2.5V	100 mA	10 $\Omega$	200mA	350mW
BS107	1.75V	2.6V	20 mA	28 $\Omega$	250mA	350mW
2N7000	2V	4.5V	75 mA	6 $\Omega$	200mA	350mW
VN10LM	2.5V	5V	200 mA	7.5 $\Omega$	300mA	1W
MPF930	2.5V	10V	1 A	0.9 $\Omega$	2A	1W
IRFD120	3V	10V	600 mA	0.3 $\Omega$	1.3A	1W




# BIASING IN OHMIC REGION

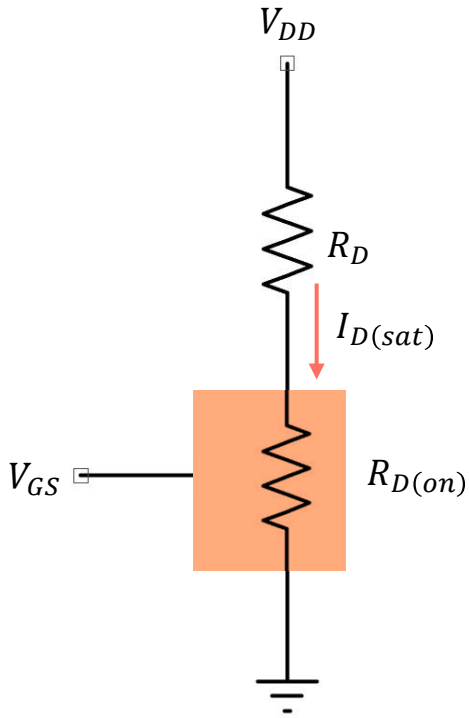

Drain saturation current

$$i_{D(sat)} = \frac{V_{DD}}{R_D}$$

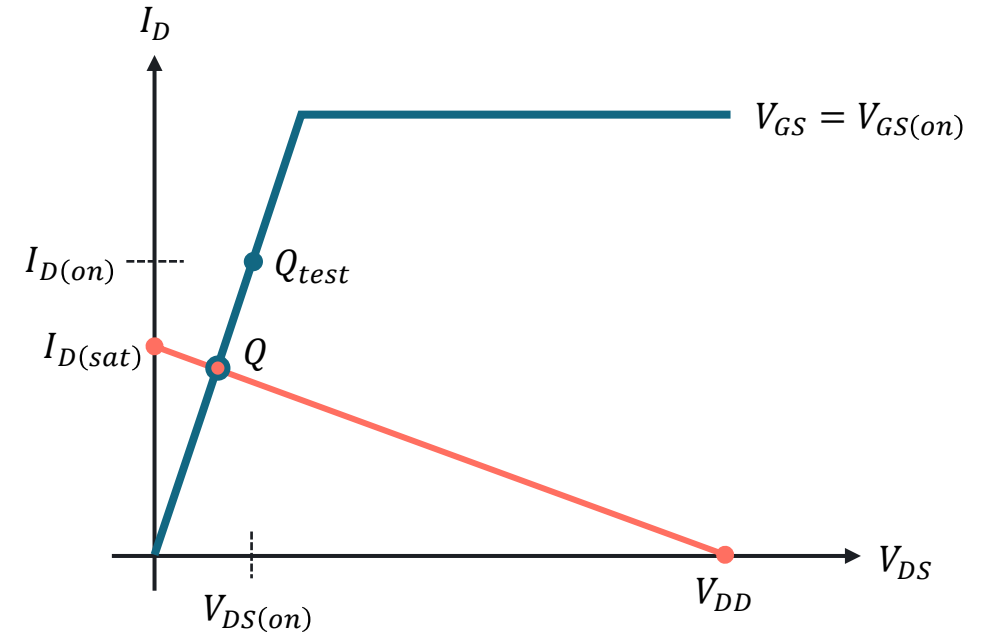


$I_{D(sat)}$  less than  $I_{D(on)}$  with  $V_{GS} = V_{GS(on)}$  ensures saturation.



## EXERCISE

What is the output voltage in the given circuit?


Solution

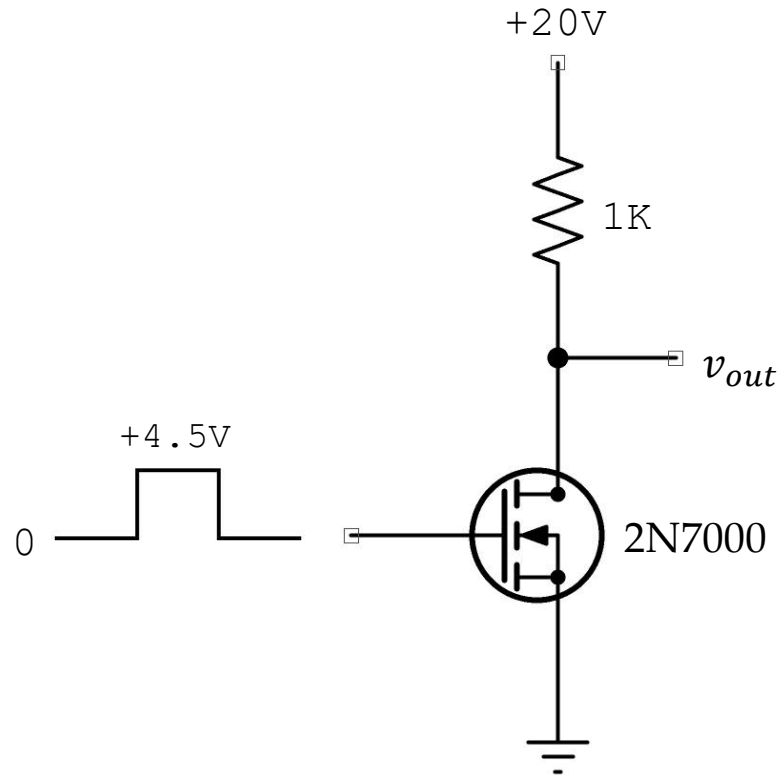

## EXERCISE

Calculate the LED current in the given circuit.


Solution

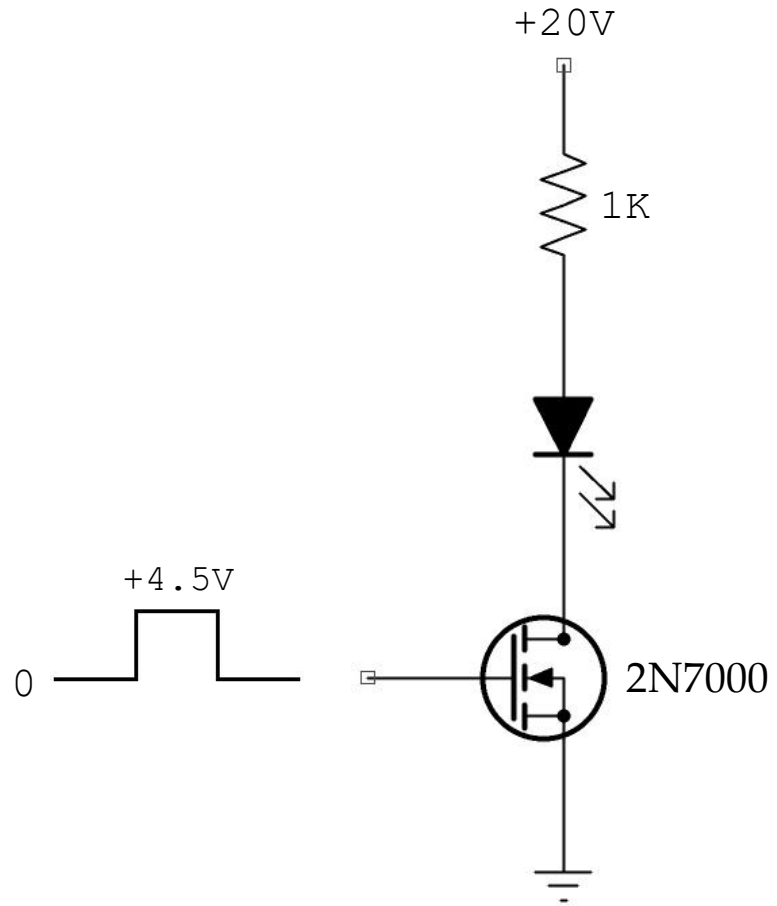

## EXERCISE

What does the given circuit do if a coil current of 30mA or more closes the relay contact?

Solution

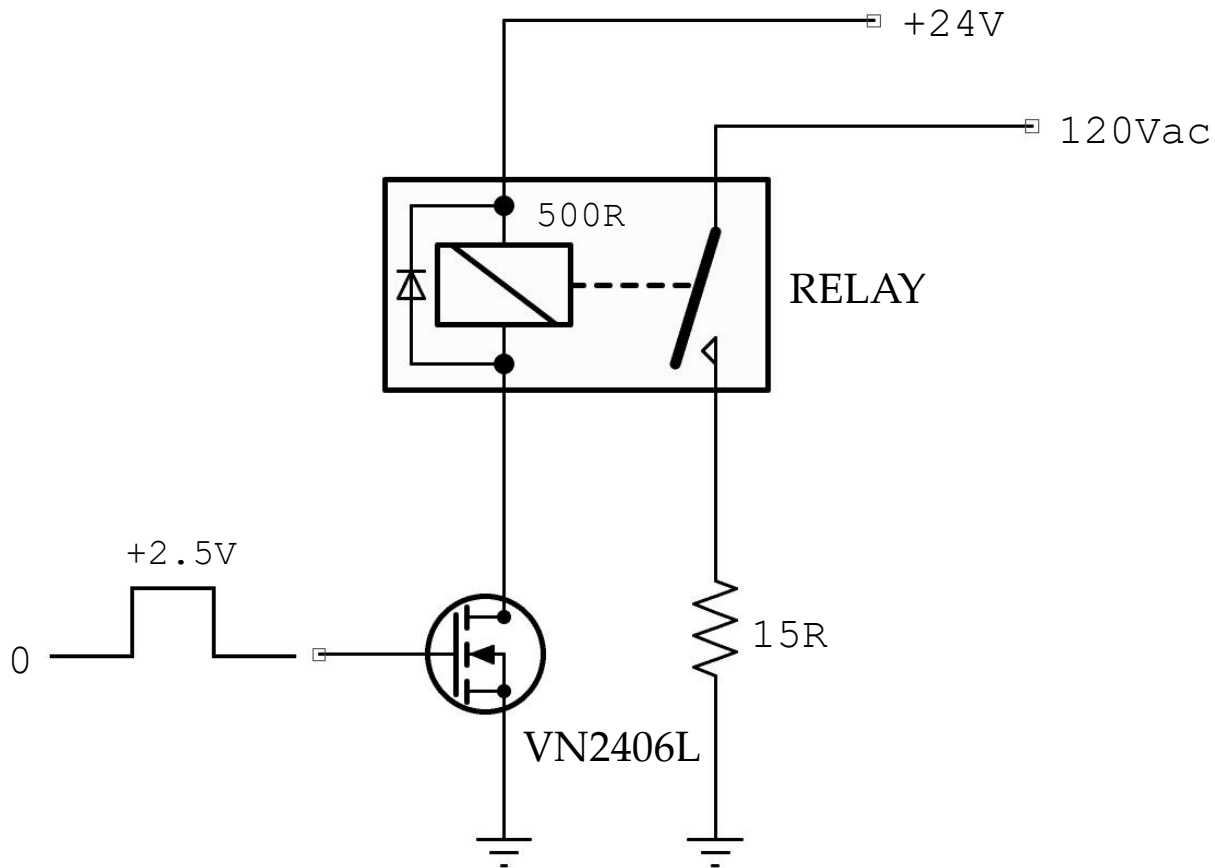




## EXERCISE

What is the current through the motor winding? For an MTP4N80E:  $V_{GS(on)} = 10\text{ V}$ ,  $I_{D(on)} = 2\text{ A}$ , and  $R_{DS(on)} = 1.95\Omega$ .


Solution

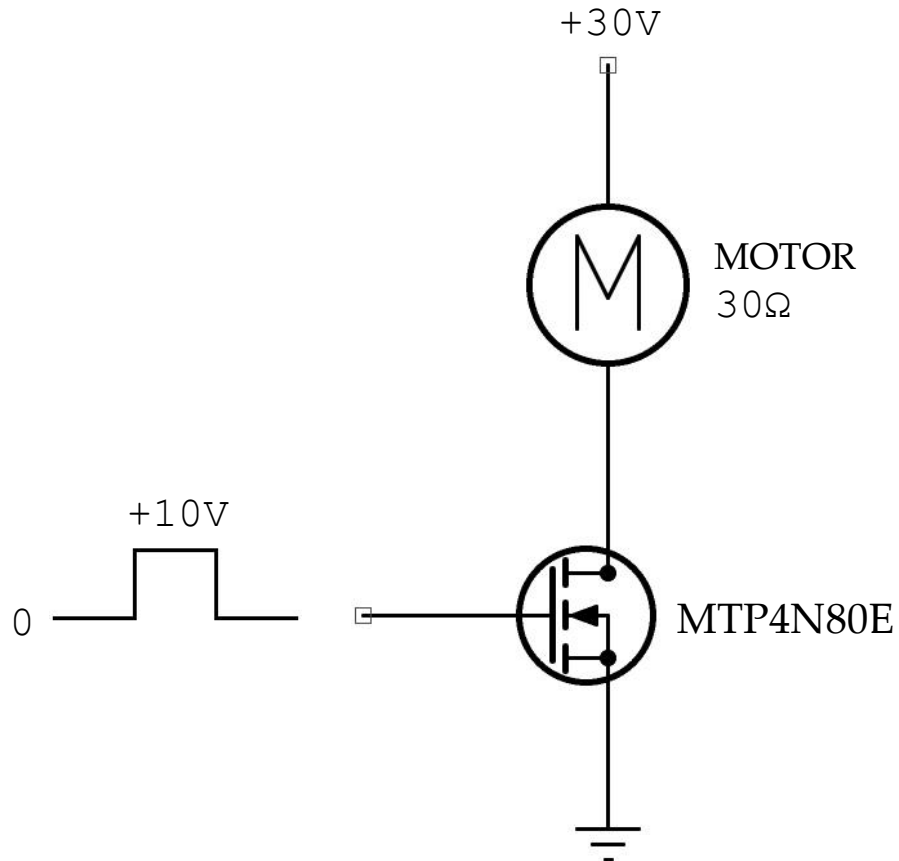


# ACTIVE-LOAD SWITCHING



# ACTIVE-LOAD SWITCHING

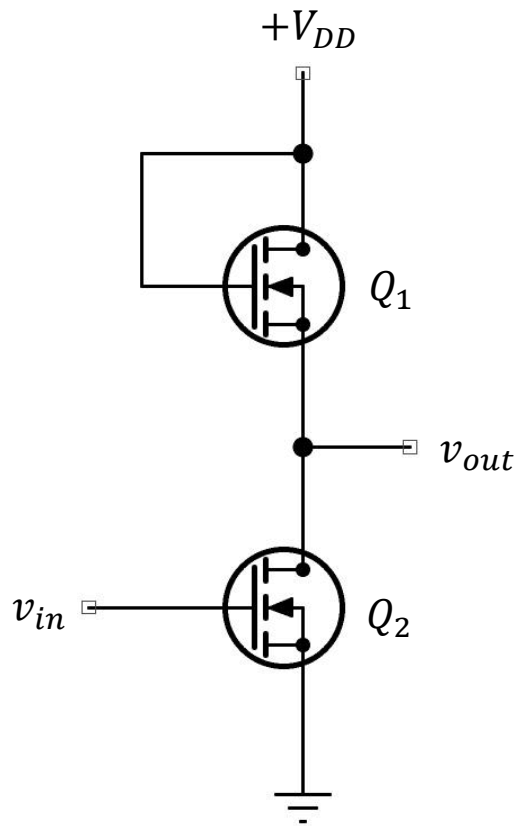


Active Load

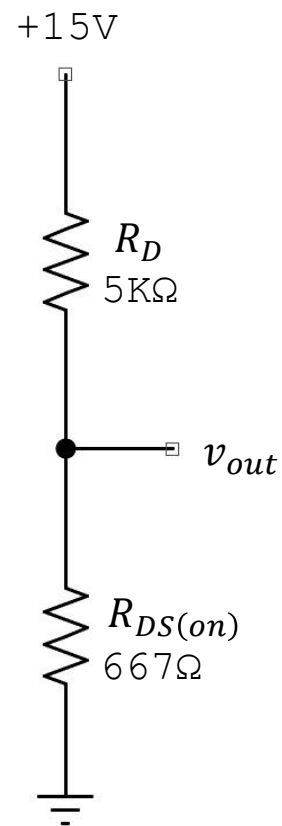

Equivalent Circuit

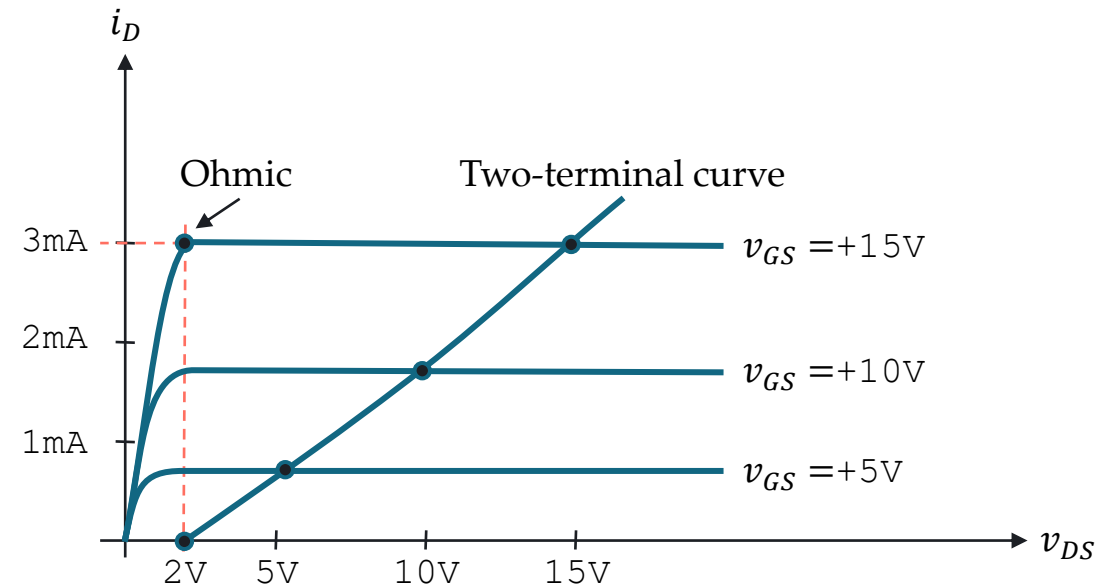$V_{GS} = V_{DS}$  produces a two-terminal curve




## EXERCISE

What is the output voltage when the input is low?

When the it is high?

Solution

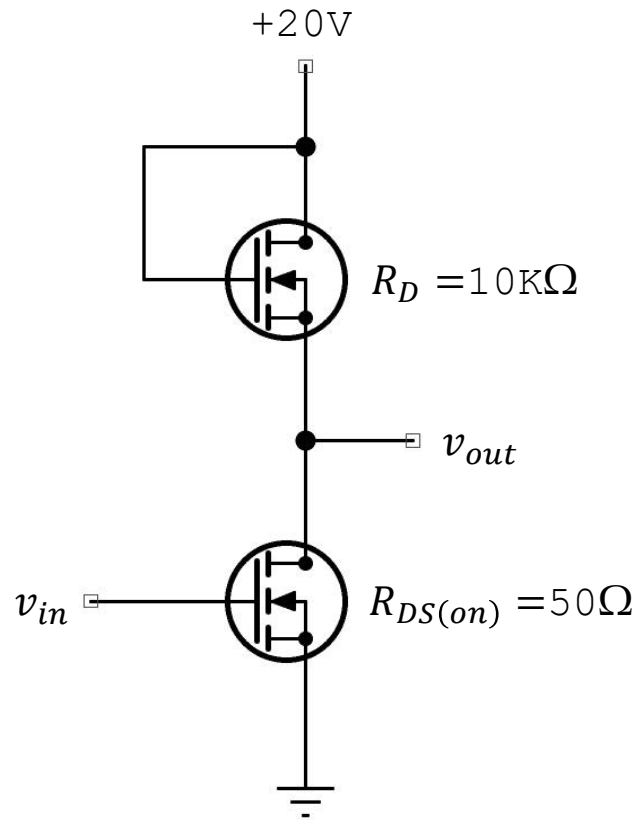


## EXERCISE

What is the output voltage when the input is low?

When the it is high?

Solution

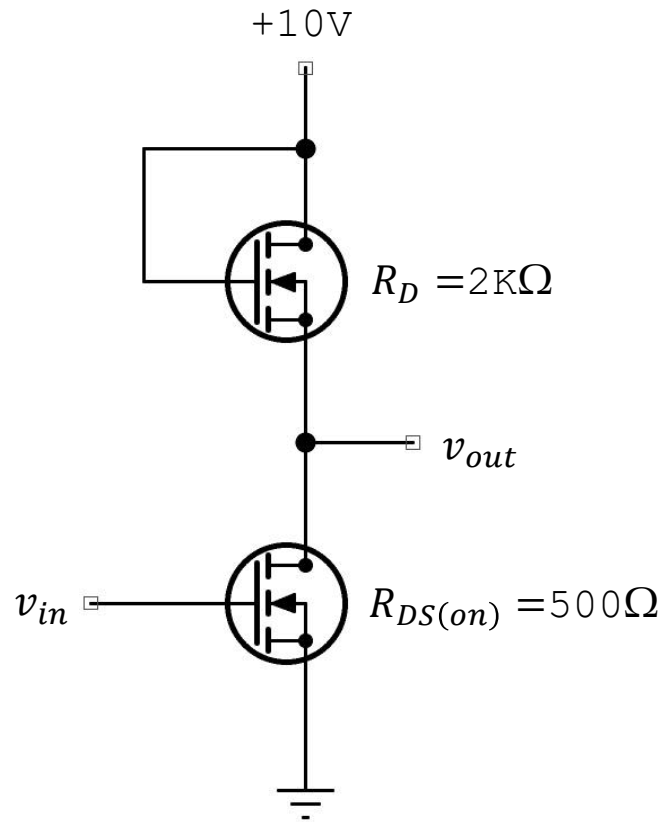

# LABORATORY

