

ELEMENT COMBINATION RULE

CIRCUIT ANALYSIS METHOD

prepared by:

Gyro A. Madrona

Electronics Engineer

TOPIC OUTLINE

Ohm's Law

Series Network

Parallel Network

Series-Parallel Network



OHM'S LAW



OHM'S LAW

Ohm's Law states that the ratio of voltage (V) to current (I) is **constant** (R).

Mathematical Representation

$$R = \frac{V}{I}$$

Basic Electrical Quantities

1. **Voltage (V)**

The measure of electrical potential energy per unit charge. It is the "**push**" or "force" that drives electric current through a circuit.

Formula

$$V = IR$$

unit

Volt (V)



OHM'S LAW

Ohm's Law states that the ratio of voltage (V) to current (I) is **constant** (R).

Mathematical Representation

$$R = \frac{V}{I}$$

Basic Electrical Quantities

2. **Current (I):**

The **flow of electric charge**, typically carried by electrons in a conductor. It represents the rate at which charge flows through a point in a circuit.

Formula

$$I = \frac{V}{R}$$

unit

Ampere (A)



OHM'S LAW

Ohm's Law states that the ratio of voltage (V) to current (I) is **constant** (R).

Mathematical Representation

$$R = \frac{V}{I}$$

Basic Electrical Quantities

3. **Resistance (R)**

The **opposition** to the flow of electric current in a material or component. It determines how much current will flow for a given voltage.

Formula

$$R = \frac{V}{I}$$

unit


Ohm (Ω)



EXERCISE

Determine the current flowing through a circuit with 4 ohms resistance when a voltage of 12 volts is applied.


Solution

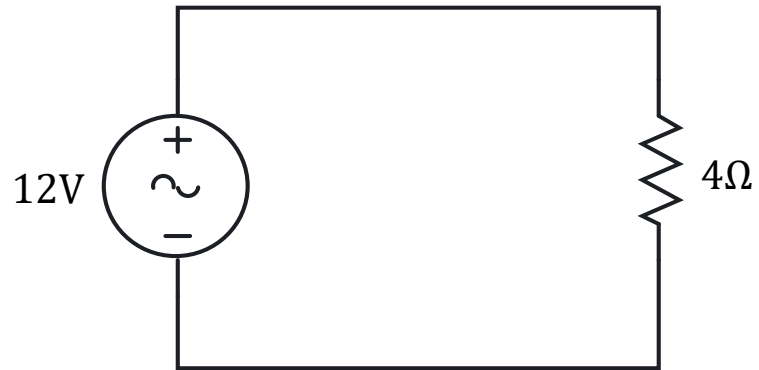

EXERCISE

Determine the voltage drop across a circuit with a resistance of 5 ohms when a current of 2 amps flows through it.


Solution

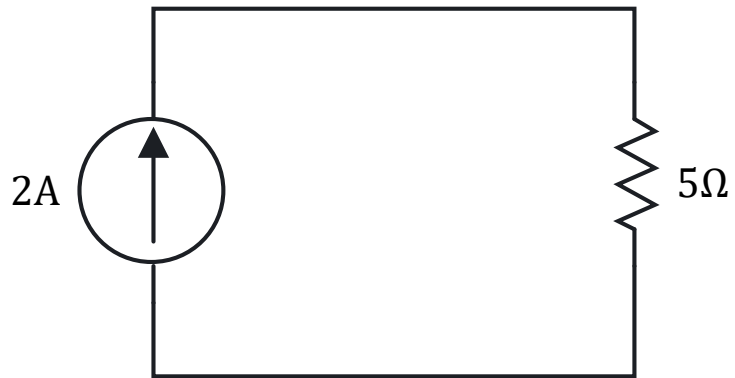

EXERCISE

Determine the resistance of a circuit if a 9-volt applied voltage results in a current flow of 1-ampere.

Solution

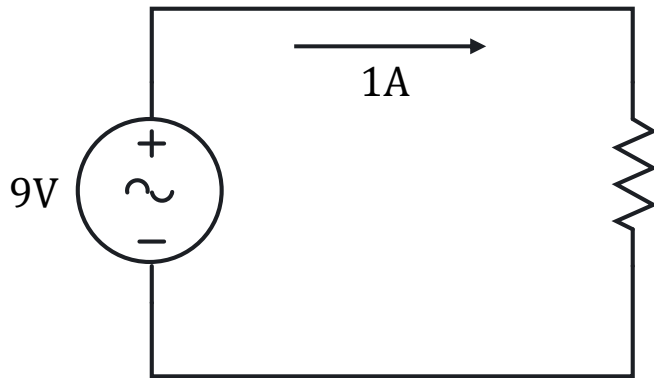


SERIES NETWORK



SERIES NETWORK

A series network refers to a configuration where components are connected end-to-end, forming a single path for current to flow.

Series Network

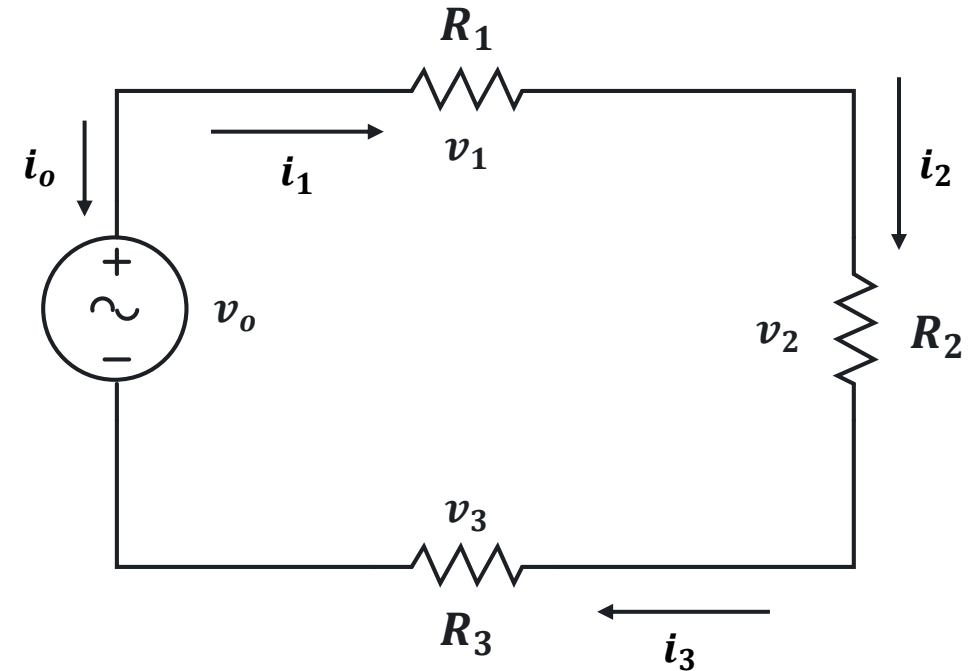


CURRENT

In a series network, the same current flows through all components.

Mathematical Representation

$$i_o = i_1 = i_2 = i_3 = \cdots i_n$$

Series Network

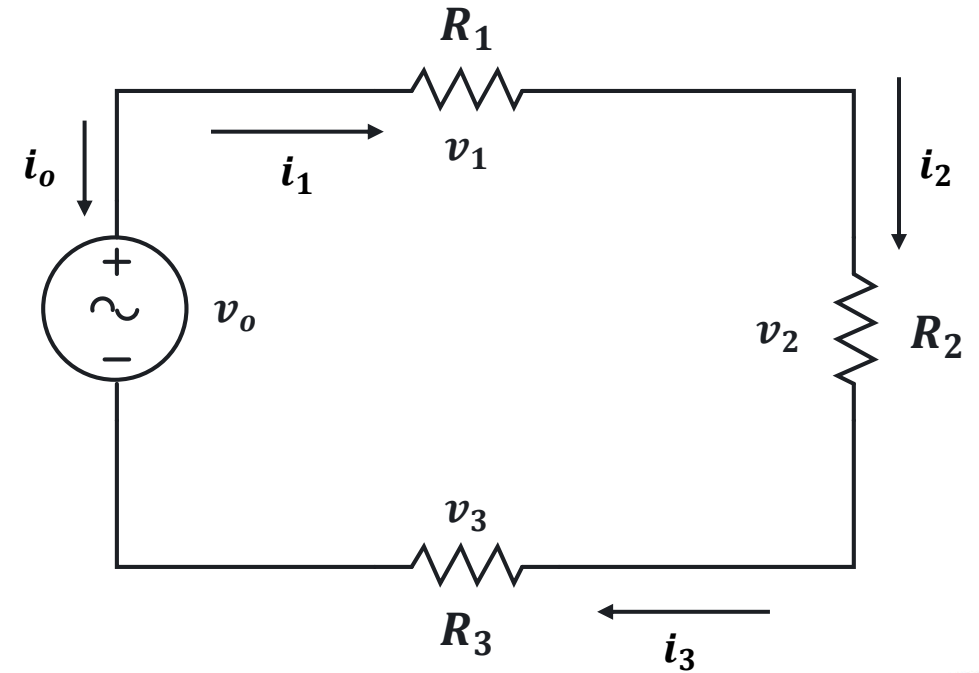


RESISTANCE

In a series network, the total resistance is the sum of the individual resistances.

Mathematical Representation

$$R_o = R_1 + R_2 + R_3 + \cdots R_n$$

Series Network

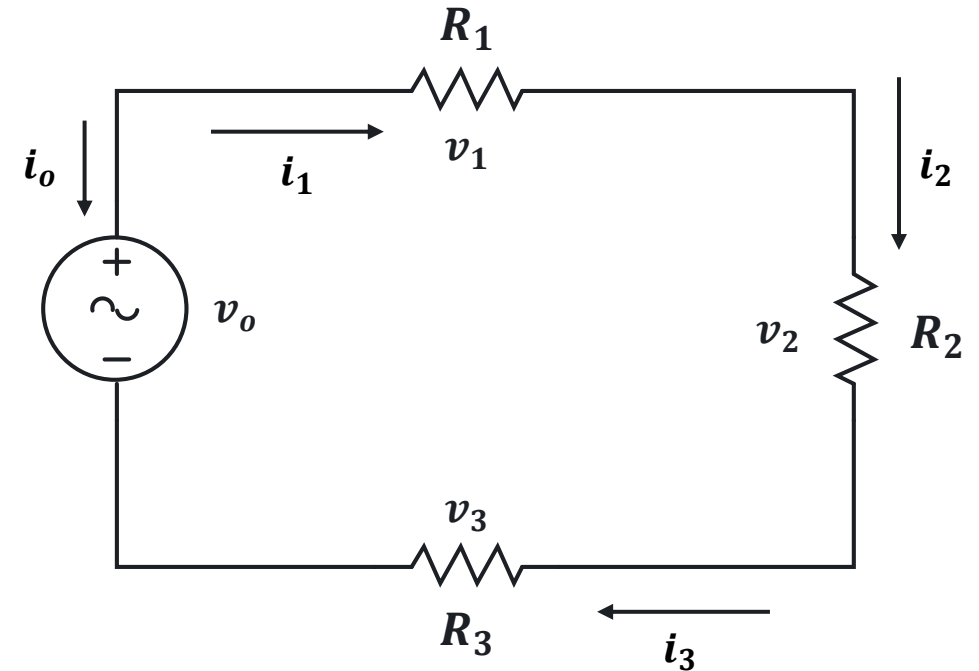


VOLTAGE

In a series network, the total voltage is the sum of the voltages across each individual component.

Mathematical Representation

$$v_o = v_1 + v_2 + v_3 + \cdots v_n$$


Series Network

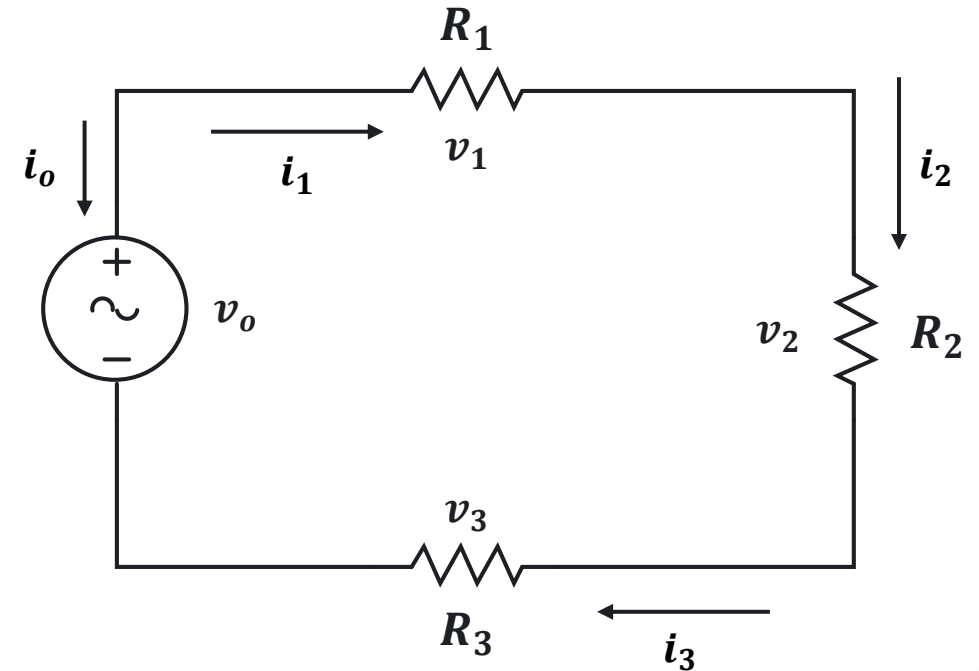

EXERCISE

Determine the voltage drop across each resistor of the given circuit.


Solution

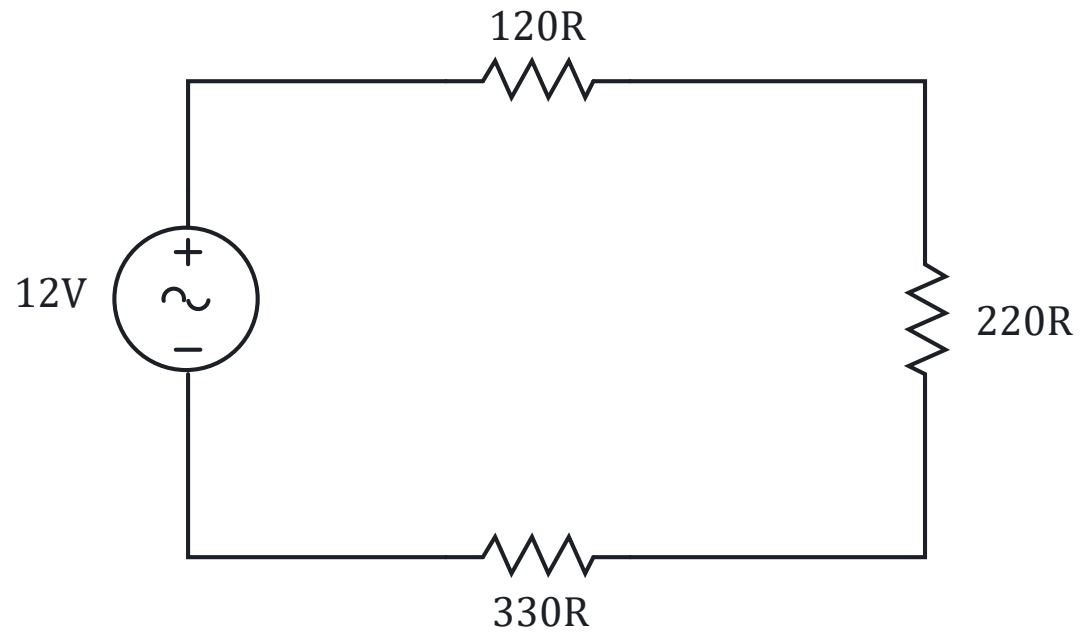

PARALLEL NETWORK

A parallel network is a configuration where components are connected across the same two points, providing multiple paths for current to flow.

Parallel Network

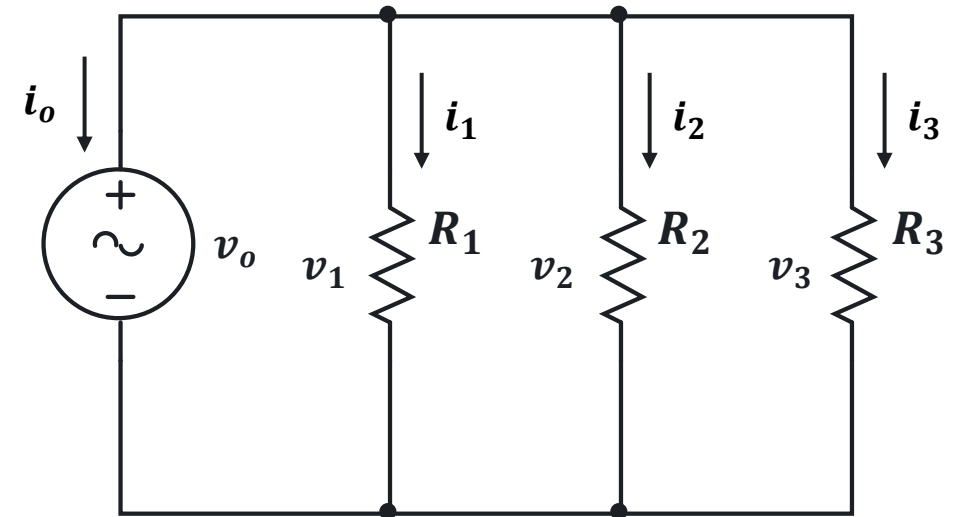


VOLTAGE

In a parallel network, the voltage across all components is the same.

Mathematical Representation

$$v_o = v_1 = v_2 = v_3 = \cdots v_n$$

Parallel Network

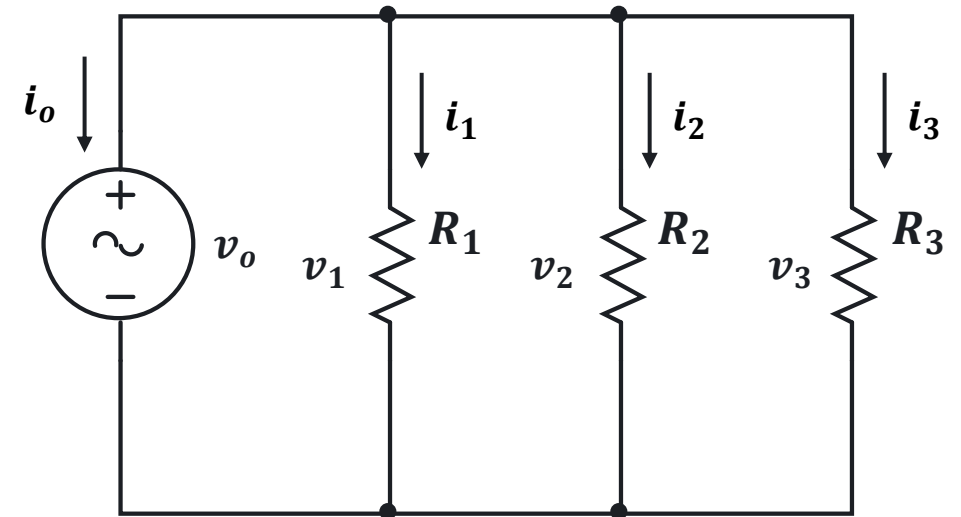


CONDUCTANCE

Conductance refers to the ability of the network to allow the flow of electric current. It is the reciprocal of resistance and is measured in siemens (S).

Mathematical Representation

$$G = \frac{1}{R}$$

Parallel Network

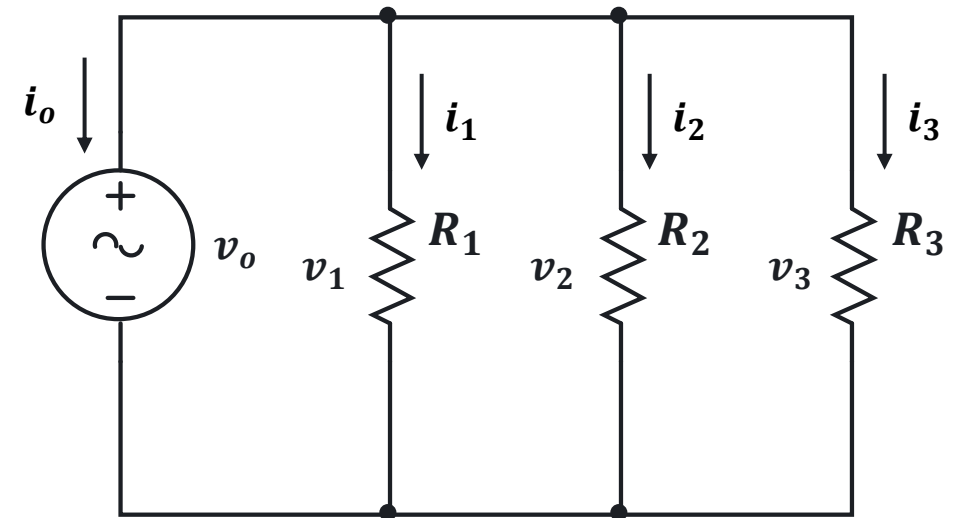


CONDUCTANCE

In a parallel network, the total conductance is the sum of the individual conductance of each resistor.

Mathematical Representation

$$G_o = G_1 + G_2 + G_3 + \cdots G_n$$

Parallel Network

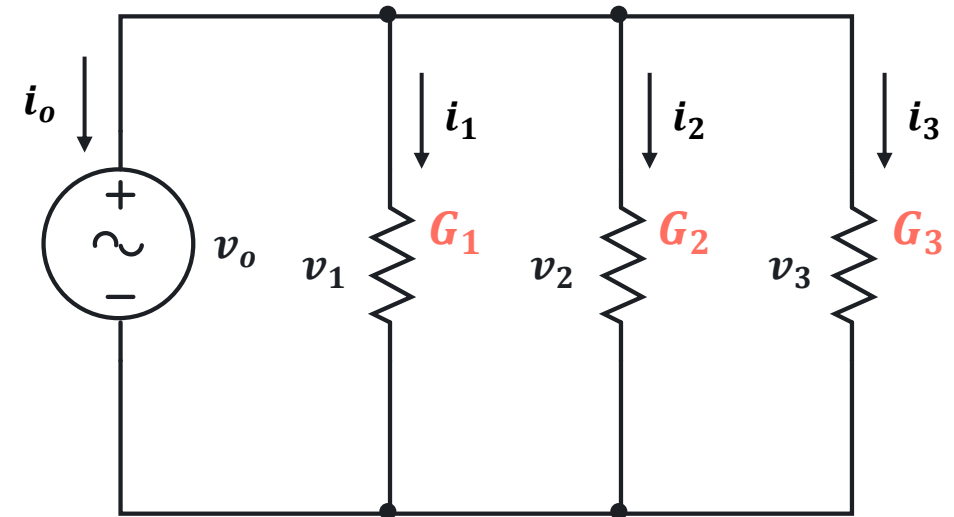


CURRENT

In a parallel network, the total current is the sum of the current flowing through each individual component.

Mathematical Representation

$$i_o = i_1 + i_2 + i_3 + \cdots i_n$$


Parallel Network

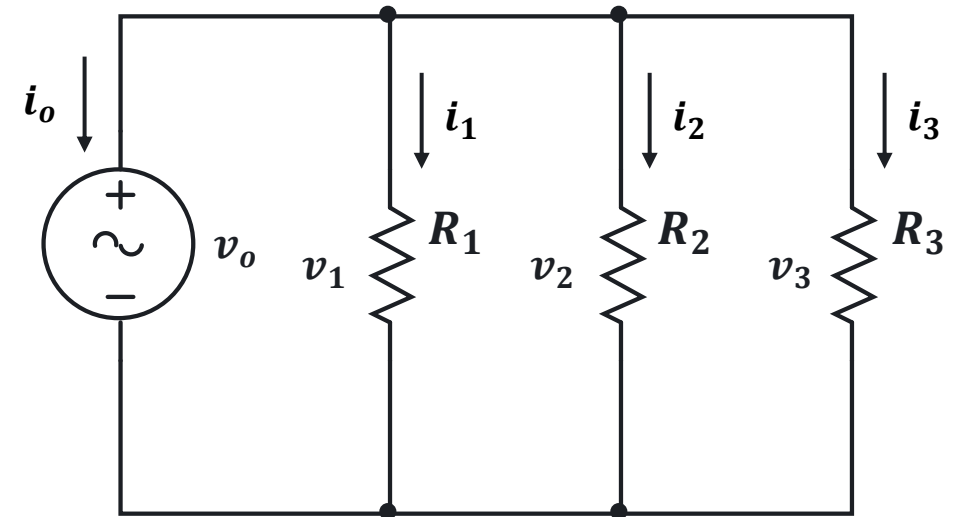

EXERCISE

Determine the current flowing through each resistor of the given circuit.

Solution

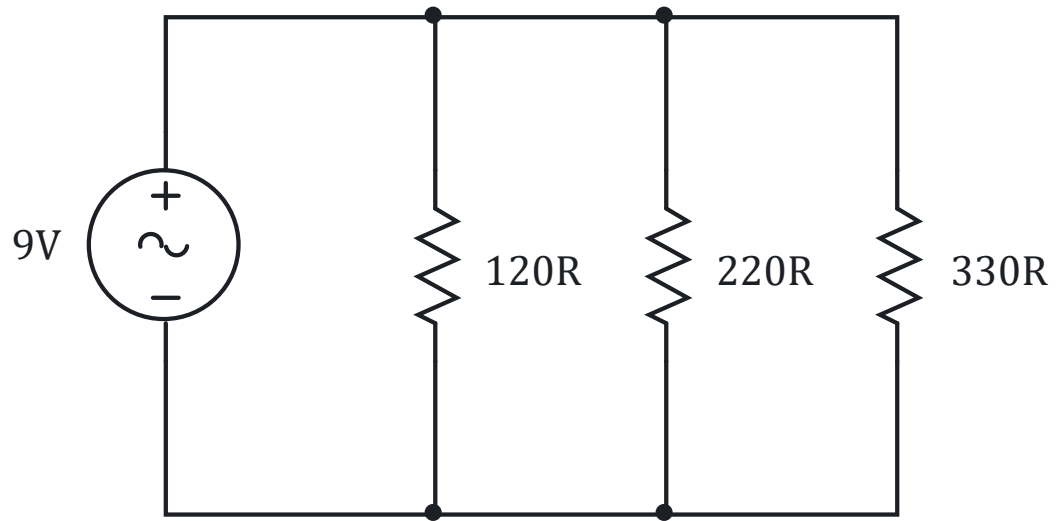

SERIES PARALLEL NETWORK



SERIEL-PARALLEL NETWORK


A series-parallel network is a type of electrical network that combines elements of both series and parallel circuits. These networks are commonly used in electrical and electronic systems to achieve desired voltage, current, and resistance characteristics.



EXERCISE

Determine the current flowing through each resistor and the voltage drop across each resistor of the given circuit.


Solution

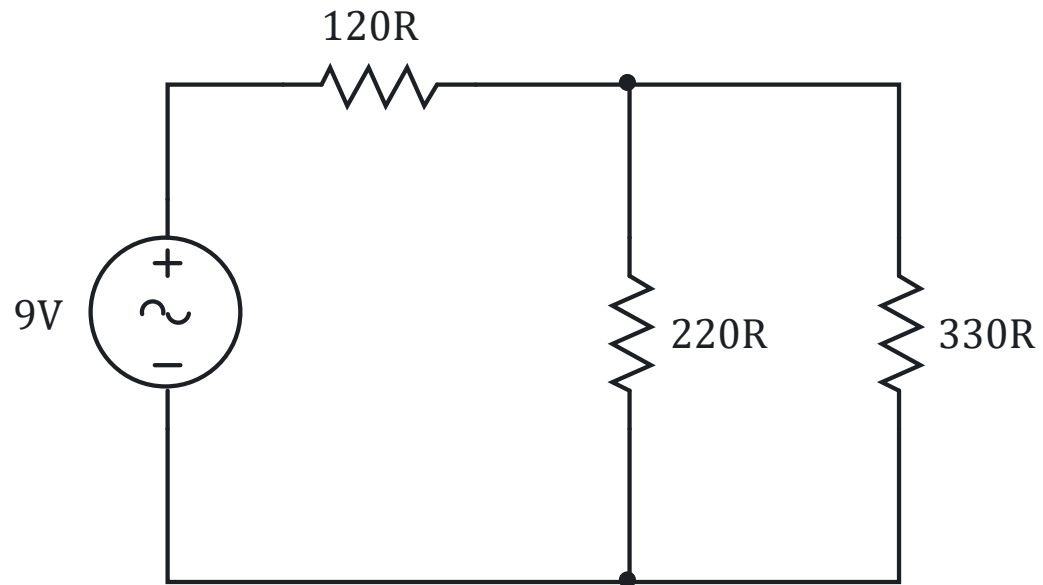

EXERCISE

Determine the current flowing through each resistor and the voltage drop across each resistor of the given circuit.


Solution

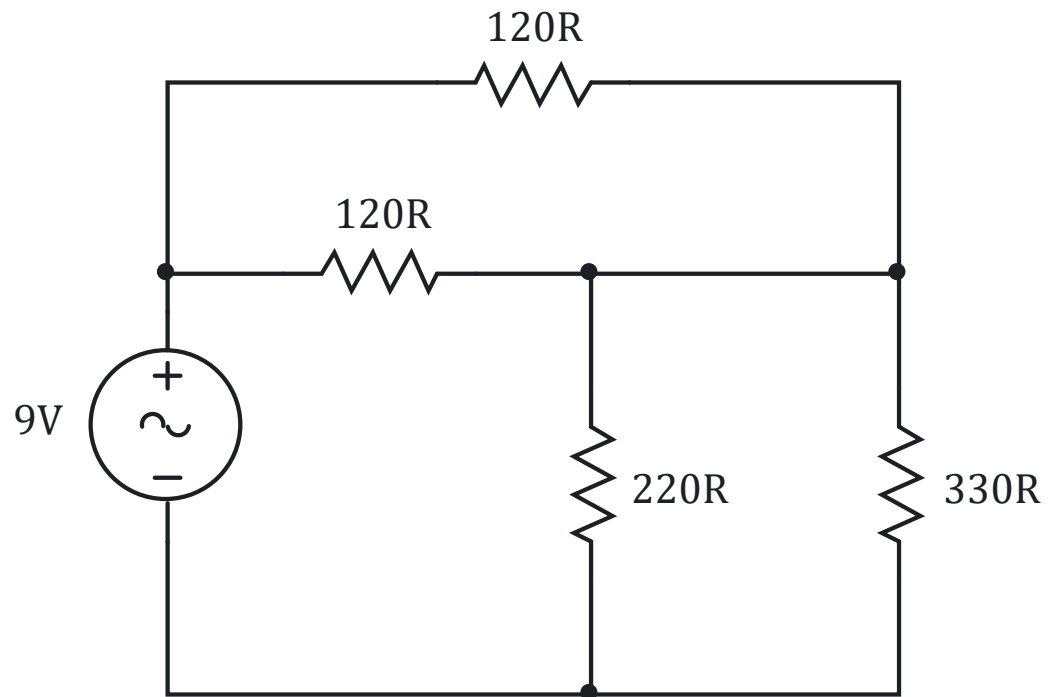

EXERCISE

Determine the current flowing through each resistor and the voltage drop across each resistor of the given circuit.

Solution

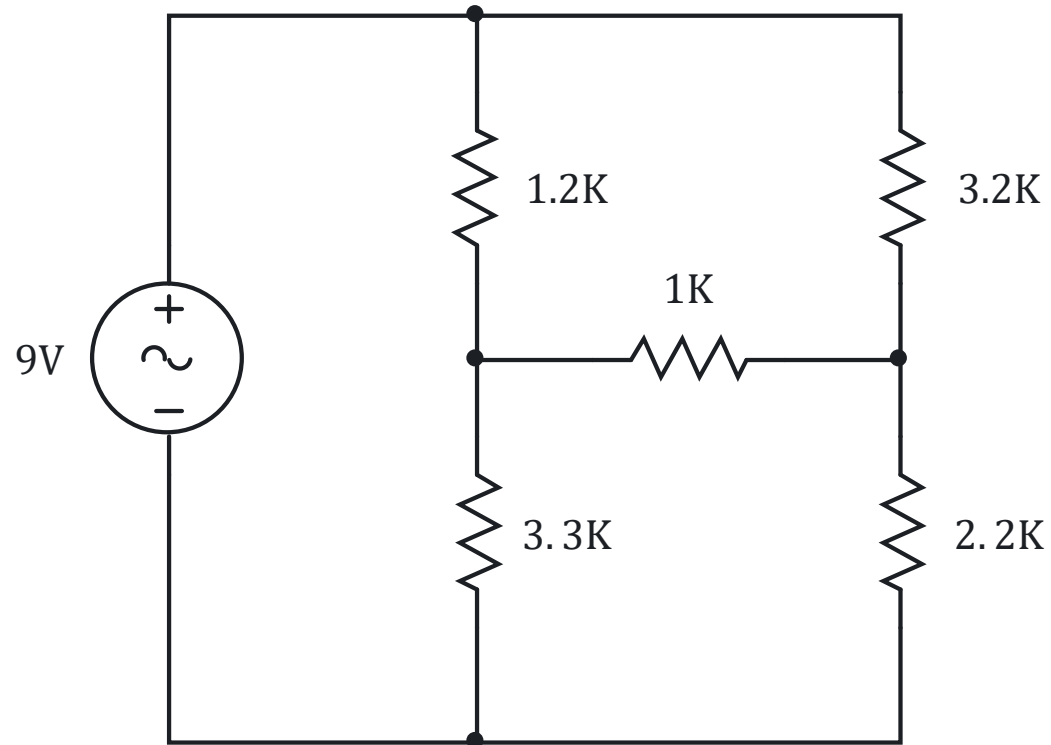

LABORATORY

