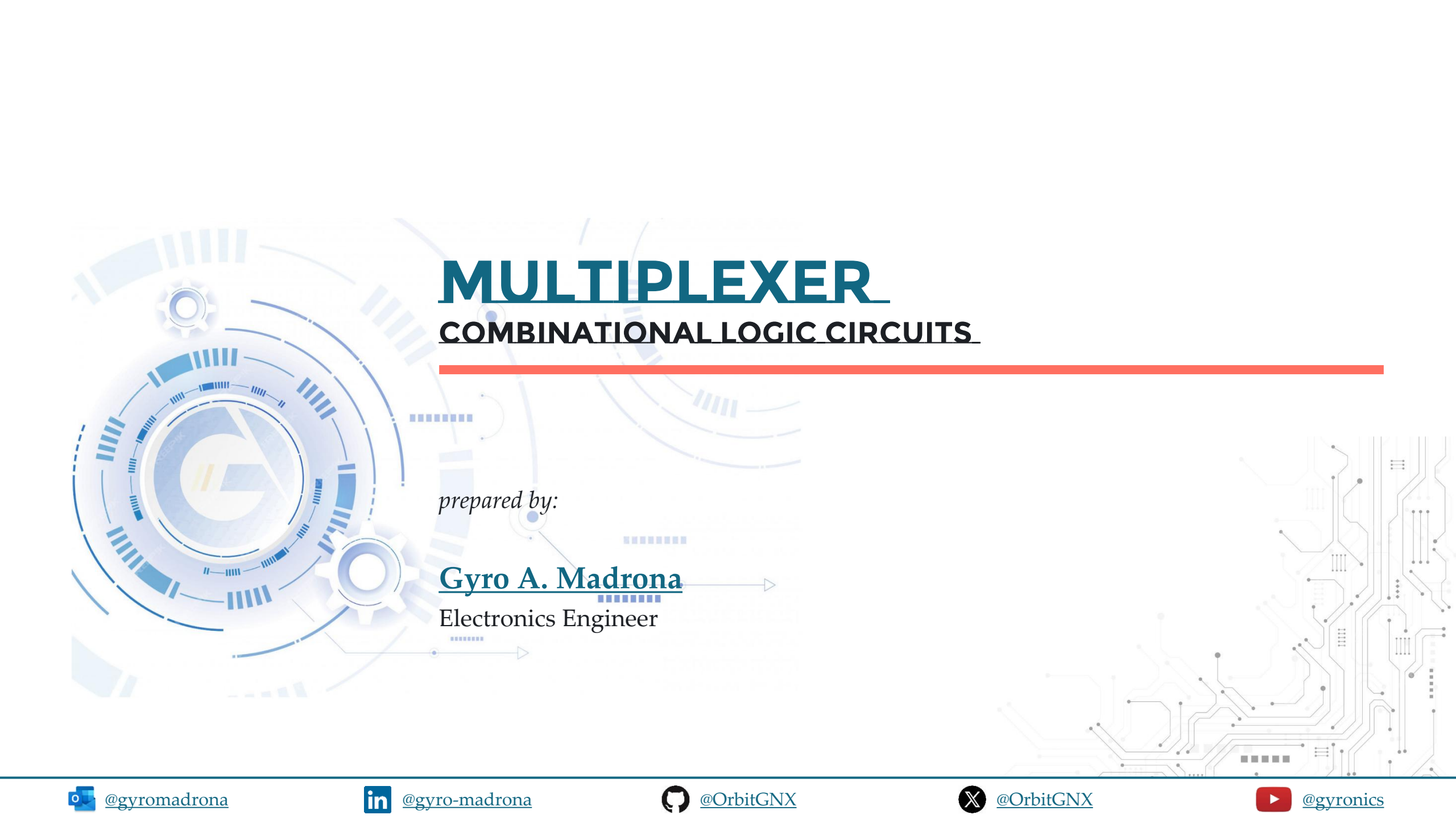




MULTIPLEXER

COMBINATIONAL LOGIC CIRCUITS

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Synthesis of Logic Functions

Shannon's Expansion Theorem



SYNTHESIS OF LOGIC FUNCTIONS




MULTIPLEXER

A multiplexer circuit has several data inputs, one or more select inputs, and **one output**. It passes the signal value on one of the data inputs to the output.

A multiplexer that has n data inputs ($D_0, D_1, \dots, D_{n-1}$), requires $\lceil \log_2 n \rceil$ select inputs.

$$\log_2(n = 2^s)$$
$$s = \log_2(n) \text{ no. of inputs}$$
$$\text{no. of selector}$$


4-to-1 Multiplexer

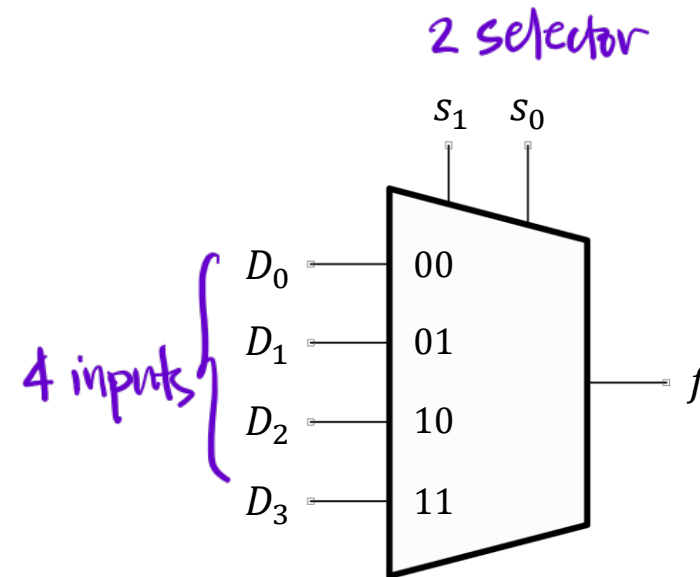

$$n = 2^s$$
$$s = \log_2 n$$
$$n = 2^2$$
$$s = \log_2 4$$
$$\underline{n = 4}$$
$$\underline{s = 2}$$

2-TO-1 MUX

Graphical Symbol

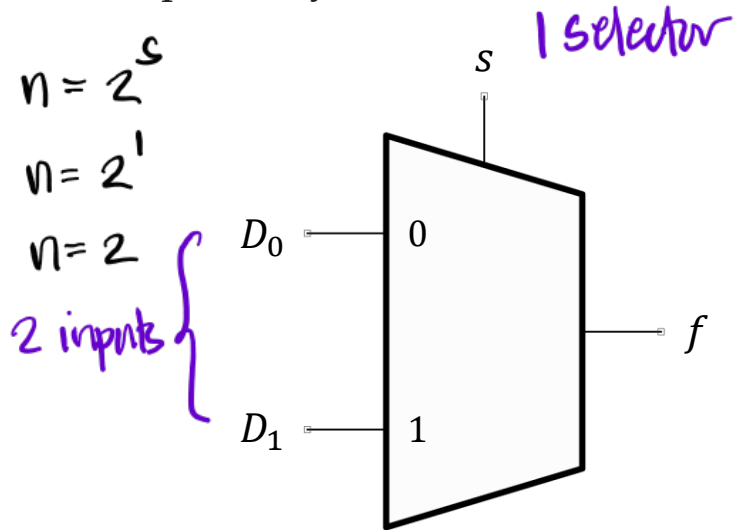

Truth Table


s	f
0	D_0
1	D_1

Minterm

$$\bar{s}D_0$$

$$sD_1$$


Sum-of-Products Implementation

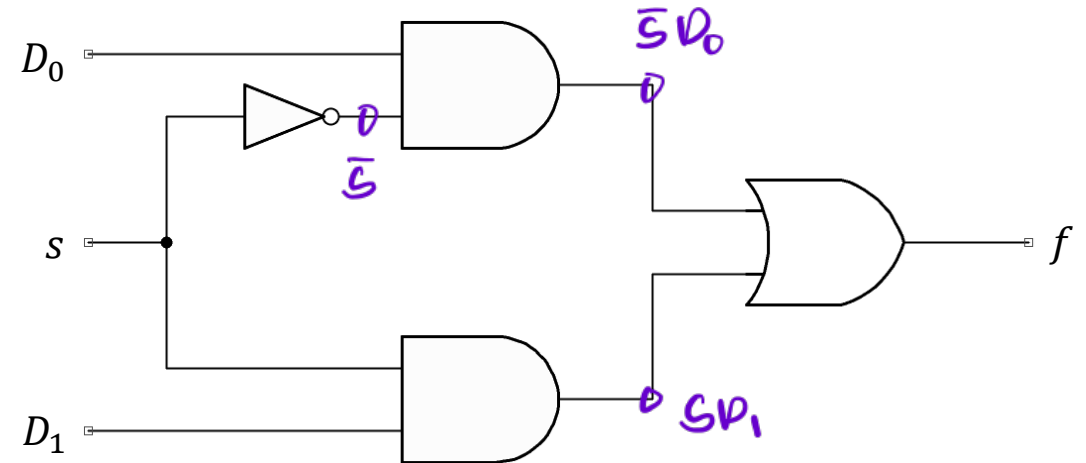

$$\underline{f = \bar{s}D_0 + sD_1}$$

4-TO-1 MUX

Graphical Symbol

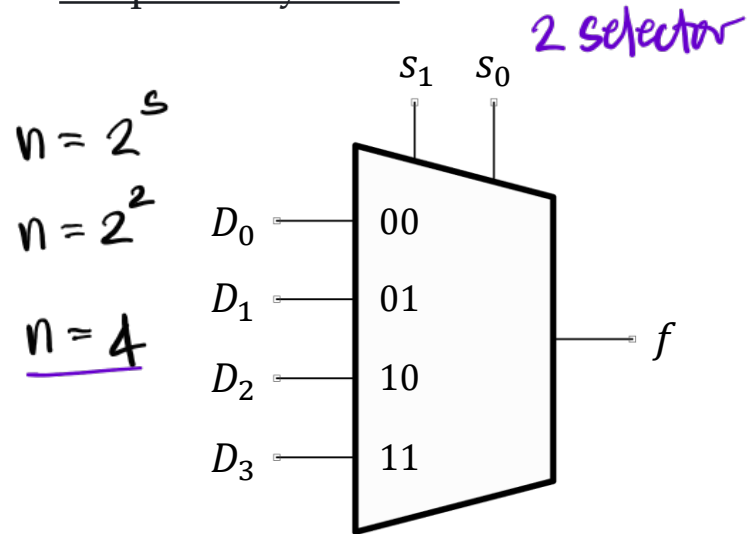

Truth Table

s_1	s_0	f
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Minterm


$\bar{s}_1 \bar{s}_0 D_0$

$\bar{s}_1 s_0 D_1$

$s_1 \bar{s}_0 D_2$


$s_1 s_0 D_3$

Sum-of-Products Implementation

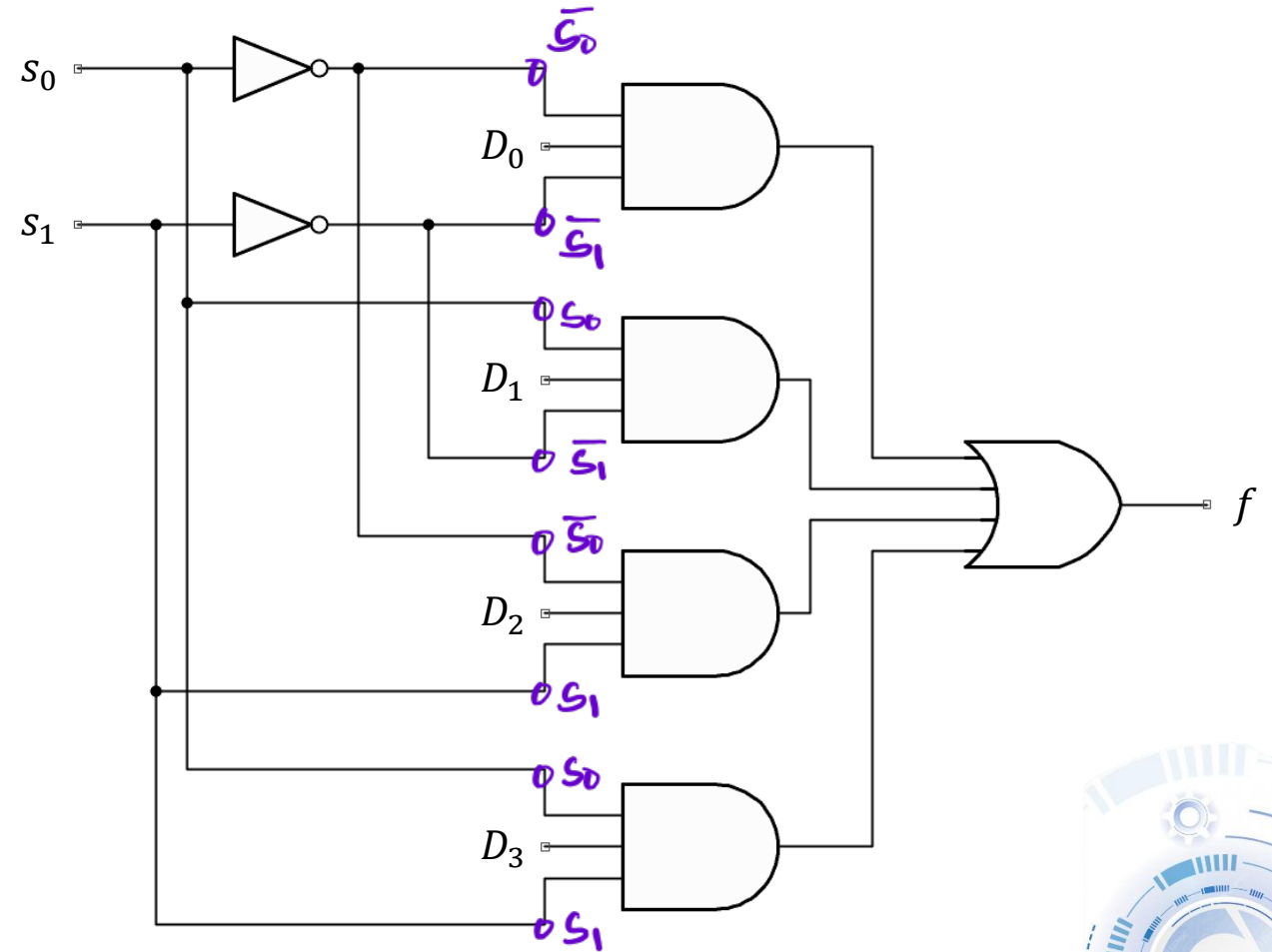


USING 2-TO-1 MUX

Using 2-to-1 MUX to build a 4-to-1 MUX

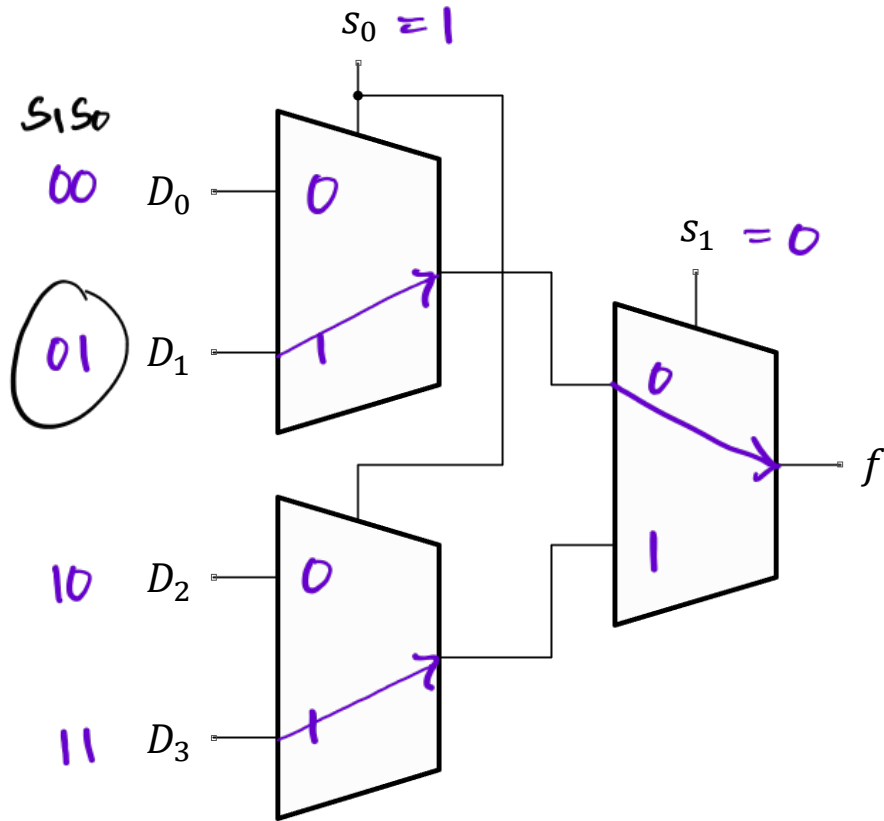

Using 2-to-1 MUX to build a 16-to-1 MUX

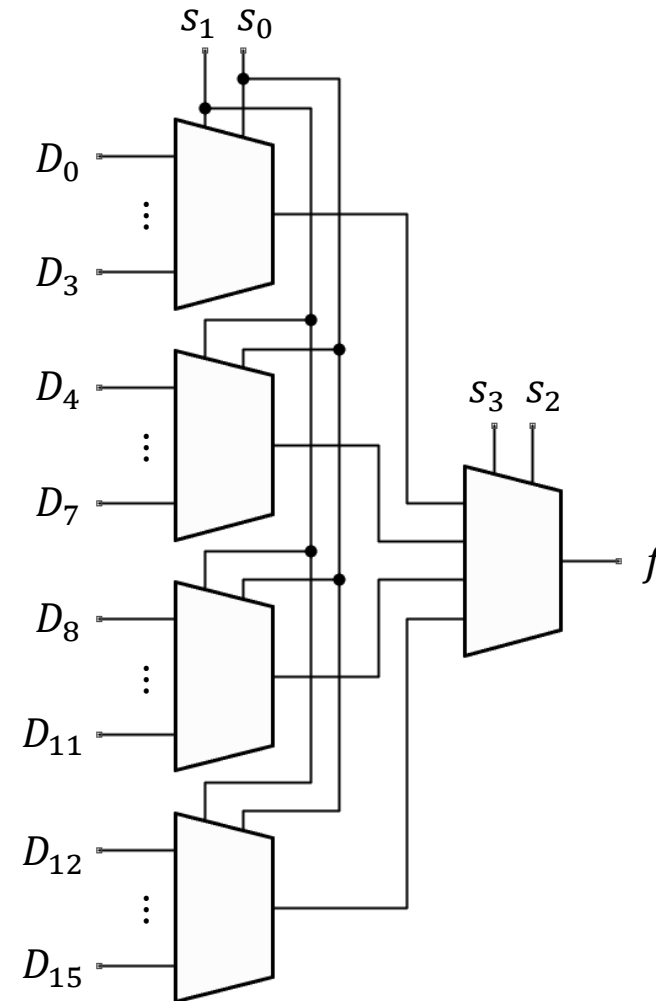

XOR LOGIC GATE

Implementation using 4-to-1 MUX

D_1 S_1	D_0 S_0	f
0 0	00	0
0 1	01	1
1 0	10	1
1 1	11	0


for 4 inputs

$$\log_2(n = 2^S)$$

$$S = \log_2 n$$

$$S = \log_2(4)$$


$$\underline{S = 2}$$

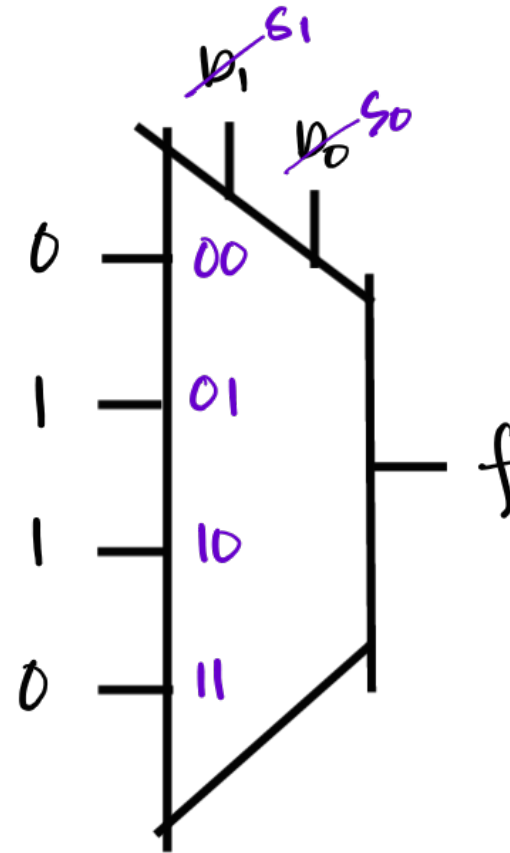

XOR LOGIC GATE

Implementation using 2-to-1 MUX


D_1 S_1	D_0 S_0	f
0	0	0
0	1	1
1	0	1
1	1	0

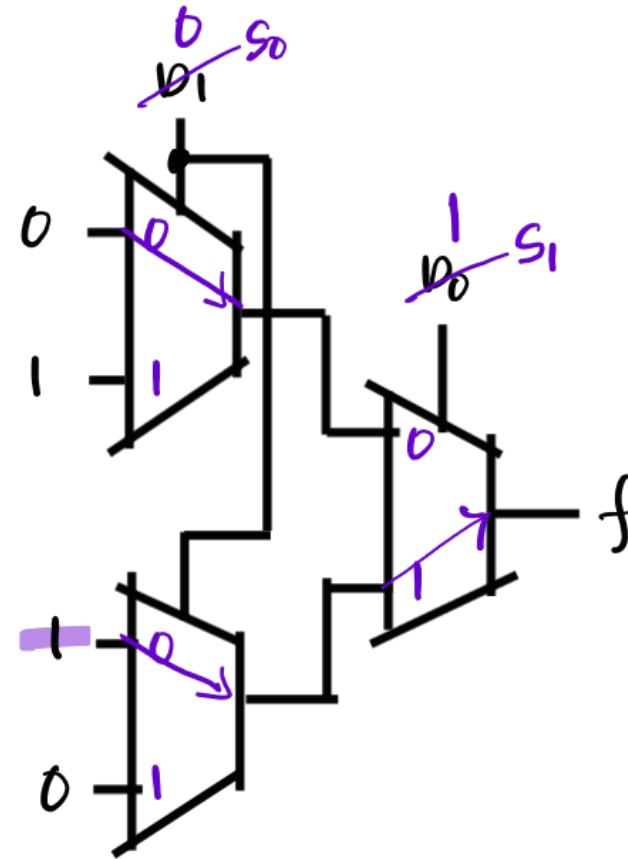

XOR LOGIC GATE

Implementation using 2-to-1 MUX

D_1 <i>5</i>	D_0 <i>input</i>	f
0 <i>0</i>	0 <i>→</i>	0
0 <i>0</i>	1 <i>→</i>	1
1 <i>1</i>	0 <i>not</i>	1
1 <i>1</i>	1 <i>not</i>	0

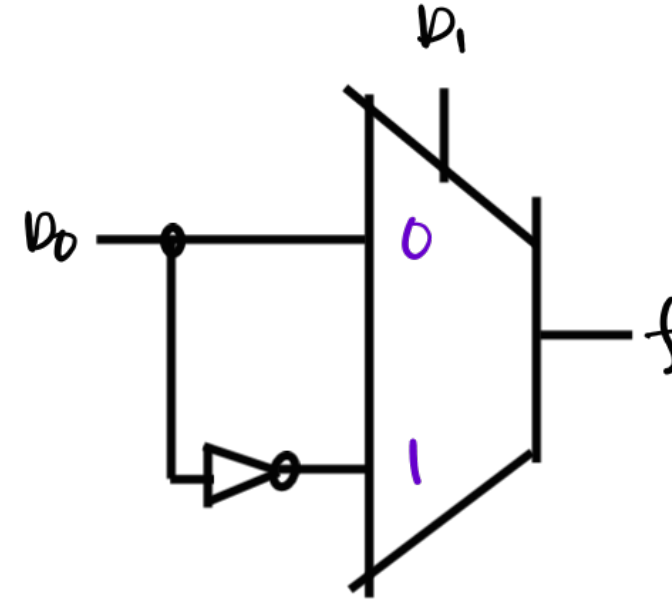


EXERCISE

Implement the logic function described by the truth table using a 4-to-1 multiplexer configuration.

$\cancel{D_2} S_1$	$\cancel{D_1} S_0$	$\cancel{D_0} \text{ input}$	f
0	0	0 x	0
0	0	1 x	0
0	1	0 →	0
0	1	1 →	1
1	0	0 →	0
1	0	1 →	1
1	1	0 x	1
1	1	1 x	1

Solution

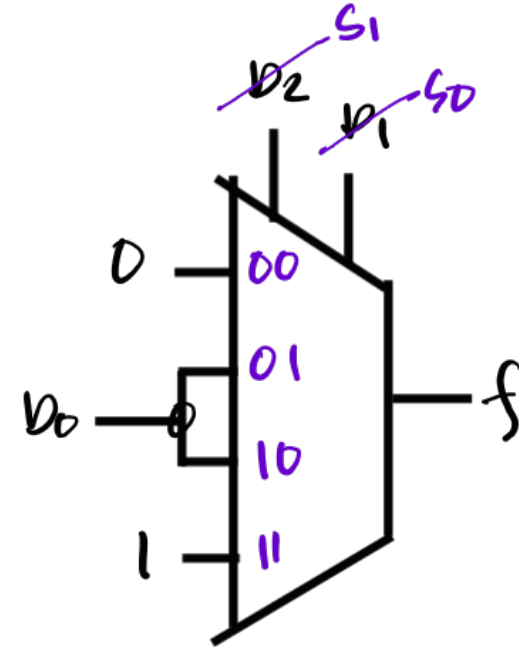


EXERCISE

Implement the three-input XOR described by the truth table using a 4-to-1 multiplexer configuration.

D_2 S_1	D_1 S_0	D_0 input	f
0	0	0 →	0
0	0	1 →	1
0	1	0 not	1
0	1	1 not	0
1	0	0 not	1
1	0	1 not	0
1	1	0 →	0
1	1	1 →	1

Solution

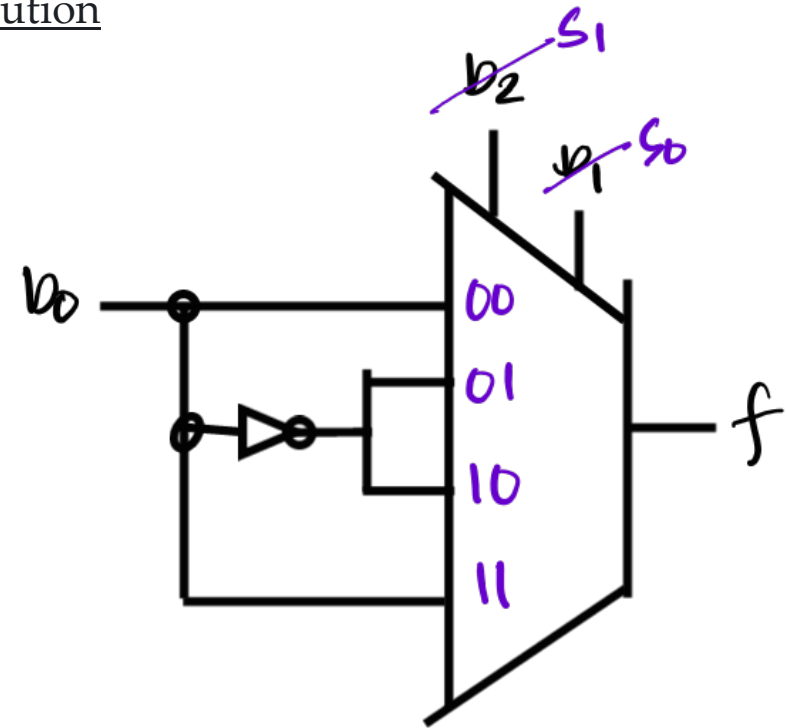

SHANNON'S EXPANSION THEOREM



SHANNON'S EXPANSION THEOREM

Shannon's expansion theorem states that any Boolean function $f(x_0, x_1, \dots, x_{n-1})$ can be written in the form:

$$f(x_0, x_1, \dots, x_{n-1}) = \bar{x}_1 f_{\bar{x}_1} + x_1 f_{x_1}$$

where

$f_{\bar{x}_1}$ = the cofactor of f with respect to $\bar{x}_1$
= $(x_0, \mathbf{0}, \dots, x_{n-1})$

f_{x_1} = the cofactor of f with respect to x_1
= $(x_0, \mathbf{1}, \dots, x_{n-1})$

Selector

Expanding the given function with respect to x_1

$$f = x_0 x_1 + x_0 x_2 + x_1 x_2$$

$$f = x_1 (x_0 \cdot 1 + x_0 x_2 + 1 \cdot x_2) + \bar{x}_1 (x_0 \cdot 0 + x_0 x_2 + 0 \cdot x_2)$$

$$f = x_1 (\underbrace{x_0 + x_0 x_2 + x_2}_{A + AB = A}) + \bar{x}_1 (x_0 x_2)$$

$$f = \cancel{x_1}^S (\underbrace{x_0 + x_2}_{\text{inputs}}) + \bar{x}_1 (x_0 x_2)$$

SHANNON'S EXPANSION THEOREM

Shannon's expansion theorem states that any

Boolean function $f(x_0, x_1, \dots, x_{n-1})$ can be written in the form:

$$f(x_0, x_1, \dots, x_{n-1}) = \bar{x}_1 f_{\bar{x}_1} + x_1 f_{x_1}$$

where


$f_{\bar{x}_1}$ = the cofactor of f with respect to $\bar{x}_1$
= $(x_0, \mathbf{0}, \dots, x_{n-1})$

f_{x_1} = the cofactor of f with respect to x_1
= $(x_0, \mathbf{1}, \dots, x_{n-1})$

Expanding the given function with respect to x_1

$$f = \cancel{x_1}^s (x_0 + x_2) + \bar{x}_1 (x_0 x_2)$$

inputs

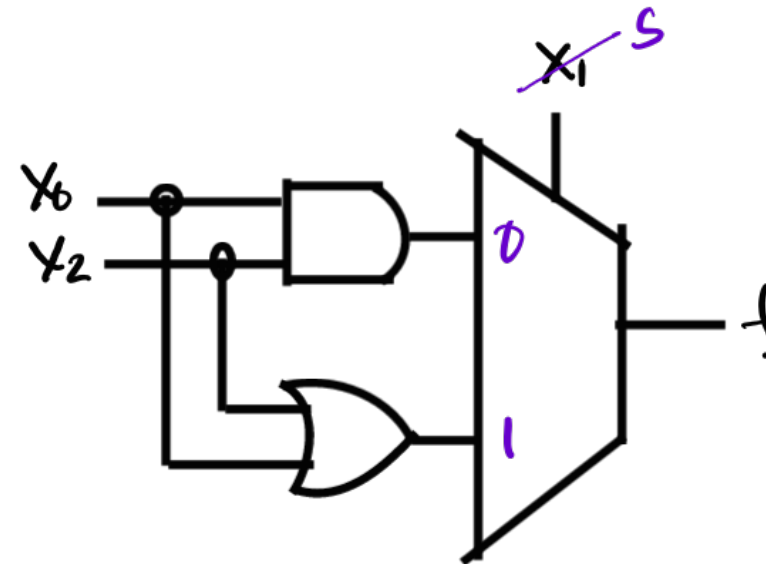

EXERCISE

Implement the logic function described by the truth table using Shannon's decomposition method.

D_2	D_1	D_0	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Minterm

$$\bar{D}_2 D_1 D_0$$

$$D_2 \bar{D}_1 D_0$$

$$D_2 D_1 \bar{D}_0$$

$$D_2 D_1 D_0$$

Solution

$$f = \bar{D}_2 D_1 D_0 + D_2 \bar{D}_1 D_0 + D_2 D_1 \bar{D}_0 + D_2 D_1 D_0$$

$$f = \bar{D}_2 D_1 D_0 + D_2 \bar{D}_1 D_0 + D_2 D_1$$

Decompose w/ D_2

$$f = D_2 (\bar{D}_1 D_0 + D_1) + \bar{D}_2 (D_1 D_0)$$

$\bar{A}B + A = A + B$

$$f = D_2 (D_0 + D_1) + \bar{D}_2 (D_1 D_0)$$

ans

EXERCISE

Implement the logic function described by the truth table using Shannon's decomposition method.

D_2 ^s	D_1	D_0	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Minterm

$$\bar{D}_2 D_1 D_0$$

$$D_2 \bar{D}_1 D_0$$


$$D_2 D_1 \bar{D}_0$$

$$D_2 D_1 D_0$$

Solution

$$f = \cancel{D_2}^b (D_0 + D_1) + \bar{D}_2 (D_1 D_0)$$

ans

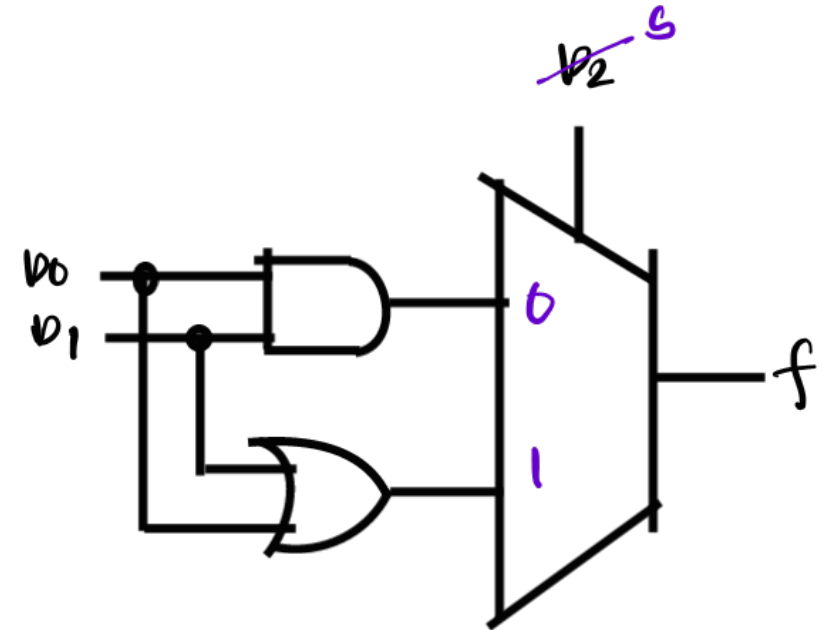

EXERCISE

Implement the logic function described by the truth table using Shannon's decomposition method.

D_2 <i>SI</i>	D_1 <i>SO</i>	D_0 <i>input</i>	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Solution

$$f = D_2(D_0 + D_1) + \bar{D}_2(D_1 D_0)$$

Decompose w/ D_1

$$f = D_2 D_1 (1) + \bar{D}_2 D_1 (D_0) + D_2 \bar{D}_1 (D_0) + \bar{D}_2 \bar{D}_1 (0)$$

$$f = \underset{11}{D_2 D_1} + \underset{01}{\bar{D}_2 D_1 (D_0)} + \underset{10}{D_2 \bar{D}_1 (D_0)} \quad \text{Ans}$$



EXERCISE


Implement the logic function described by the truth table using Shannon's decomposition method.

$\cancel{D_2}^{S_1}$	$\cancel{D_1}^{S_0}$	$\cancel{D_0}$ input	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Solution

$$f = \cancel{D_2}^{S_1} \cancel{D_1}^{S_0} + \bar{\cancel{D_2}}^{S_1} \cancel{D_1}^{S_0} (\cancel{D_0}) + \cancel{D_2}^{S_1} \bar{\cancel{D_1}}^{S_0} (\cancel{D_0})$$

1 1 0 1 1 0 ans

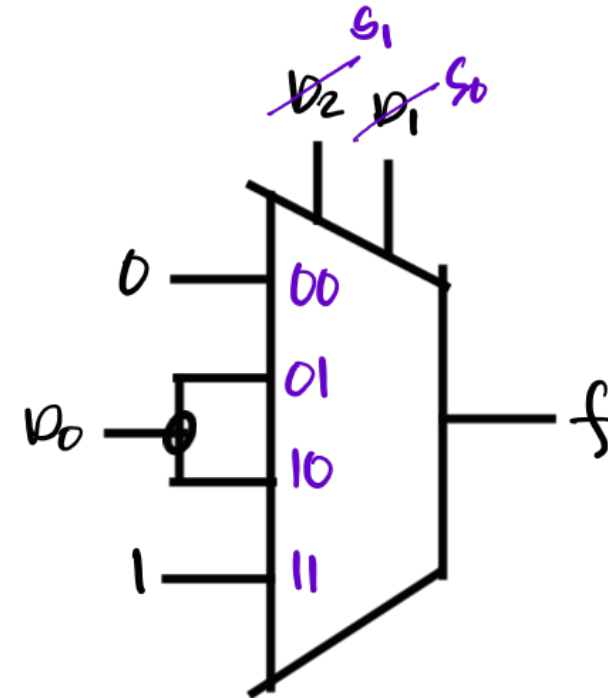

EXERCISE

Implement the three-input XOR described by the truth table using a Shannon's decomposition method.

$\cancel{D_2}^{S1}$	$\cancel{D_1}^{S0}$	$\cancel{D_0}^{input}$	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Minterm

$$\bar{D}_2 \bar{D}_1 D_0$$

$$\bar{D}_2 D_1 \bar{D}_0$$

$$D_2 \bar{D}_1 \bar{D}_0$$

$$D_2 D_1 D_0$$

Solution

Decompose w/ D_2

$$f = \bar{D}_2 (\bar{D}_1 D_0 + D_1 \bar{D}_0) + D_2 (\bar{D}_1 \bar{D}_0 + D_1 D_0)$$

Decompose w/ D_1

$$f = \bar{D}_2 \bar{D}_1 (D_0) + D_2 \bar{D}_1 (\bar{D}_0) + \bar{D}_2 D_1 (\bar{D}_0) + D_2 D_1 (D_0)$$

$$f = \bar{D}_2 \bar{D}_1 (D_0) + D_2 \bar{D}_1 (\bar{D}_0) + \bar{D}_2 D_1 (\bar{D}_0) + D_2 D_1 (D_0)$$

ans



EXERCISE

Implement the three-input XOR described by the truth table using a Shannon's decomposition method.

D_2 S_1	D_1 S_0	D_0 input	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Minterm

$$\bar{D}_2 \bar{D}_1 D_0$$

$$\bar{D}_2 D_1 \bar{D}_0$$


$$D_2 \bar{D}_1 \bar{D}_0$$

$$D_2 D_1 D_0$$

Solution

$$f = \bar{D}_2 \bar{D}_1 (D_0) + D_2 \bar{D}_1 (\bar{D}_0) + \bar{D}_2 D_1 (\bar{D}_0) + D_2 D_1 (D_0)$$

0 0
1 0
0 1
1 1
ans

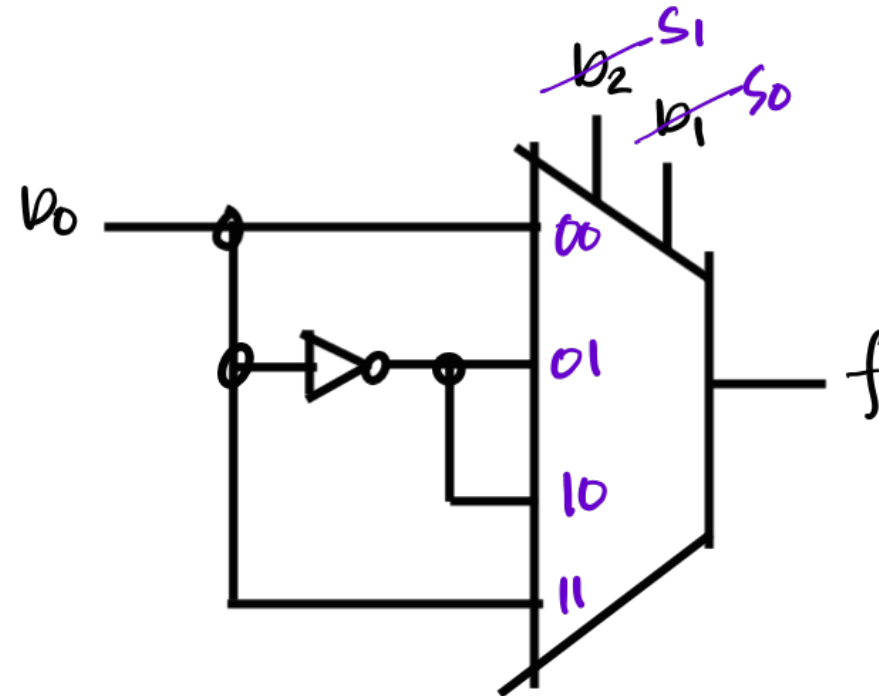

EXERCISE

Design a full-adder circuit using Shannon's decomposition method and simulate it in Multisim using the 74151 multiplexer.

A ^{S₁}	B ^{S₀}	C_{in} ^{input}	C _{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Minterm

$\bar{A}\bar{B}C_{in}$

$A\bar{B}C_{in}$

$A\bar{B}\bar{C}_{in}$

$A\bar{B}C_{in}$

Solution

Mux for C_{out}

$$C_{out} = \bar{A}(\bar{B}C_{in}) + A(\bar{B}C_{in} + B\bar{C}_{in} + BC_{in})$$

$$C_{out} = \bar{A}(\bar{B}C_{in}) + A(\bar{B} + \bar{B}C_{in})$$

$$X + \bar{X}Y = X + Y$$

$$C_{out} = \bar{A}(\bar{B}C_{in}) + A(\bar{B} + C_{in})$$

$$C_{out} = \bar{A}\bar{B}(0) + A\bar{B}(C_{in}) + \bar{A}B(C_{in}) + AB(1)$$

$$C_{out} = A\bar{B}(C_{in}) + \bar{A}B(C_{in}) + AB$$

Ans



EXERCISE

Design a full-adder circuit using Shannon's decomposition method and simulate it in Multisim using the 74151 multiplexer.

A S_1	B S_0	C_{in} input	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Minterm

$\bar{A} \bar{B} C_{in}$


$A \bar{B} C_{in}$

$A \bar{B} \bar{C}_{in}$

$A B C_{in}$

Solution
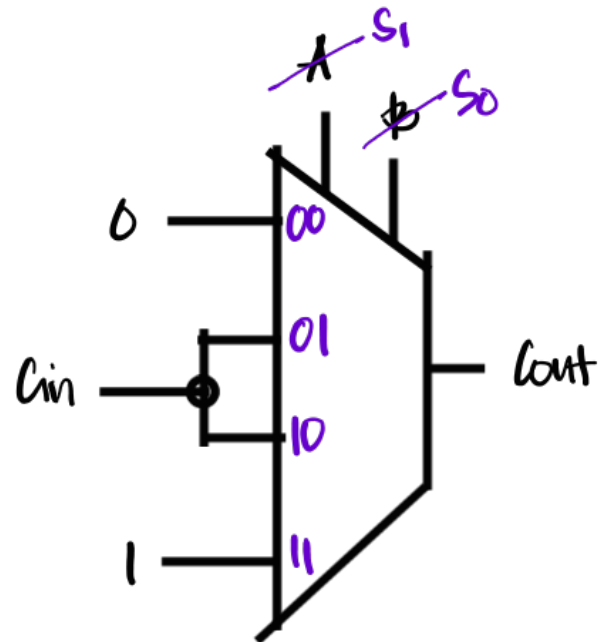
$$C_{out} = A \bar{B} (C_{in}) + \bar{A} B (C_{in}) + A B$$



EXERCISE

Design a full-adder circuit using Shannon's decomposition method and simulate it in Multisim using the 74151 multiplexer.

A S_1	B S_0	C_{in} $input$	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Minterm

$\bar{A}\bar{B}C_{in}$

$\bar{A}B\bar{C}_{in}$

$A\bar{B}\bar{C}_{in}$

ABC_{in}

Solution

Mux for Sum

$$Sum = \bar{A}(\bar{B}C_{in} + B\bar{C}_{in}) + A(\bar{B}\bar{C}_{in} + B C_{in})$$

$$Sum = \bar{A}\bar{B}(C_{in}) + A\bar{B}(\bar{C}_{in}) + \bar{A}B(\bar{C}_{in}) + AB(C_{in})$$

ans



EXERCISE

Design a full-adder circuit using Shannon's decomposition method and simulate it in Multisim using the 74151 multiplexer.

A S_1	B S_0	C_{in} input	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Minterm

$\bar{A}\bar{B}C_{in}$

$\bar{A}B\bar{C}_{in}$


$A\bar{B}\bar{C}_{in}$

ABC_{in}

Solution

$$Sum = \bar{A}\bar{B}(C_{in}) + \bar{A}B(\bar{C}_{in}) + \bar{A}B(\bar{C}_{in}) + AB(C_{in})$$

00 10
01 11 ans

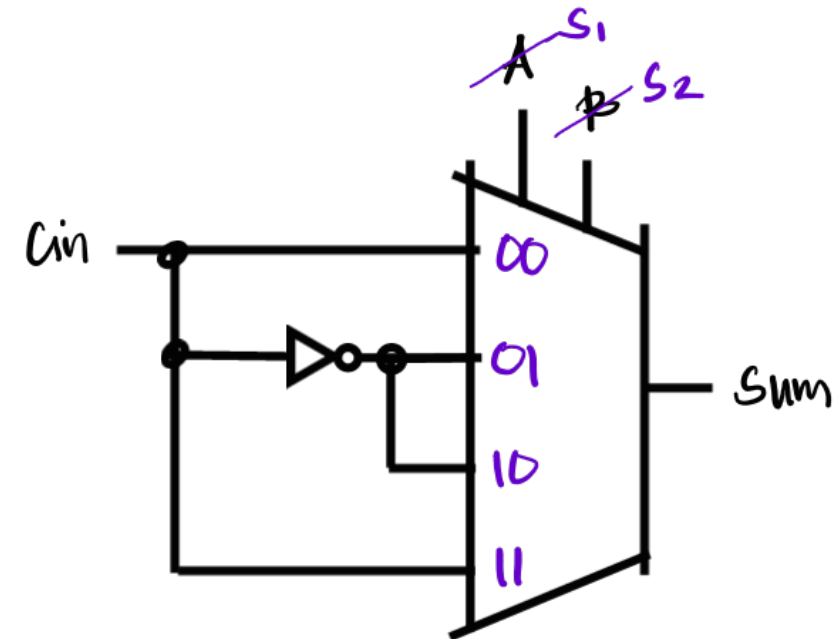

LABORATORY

