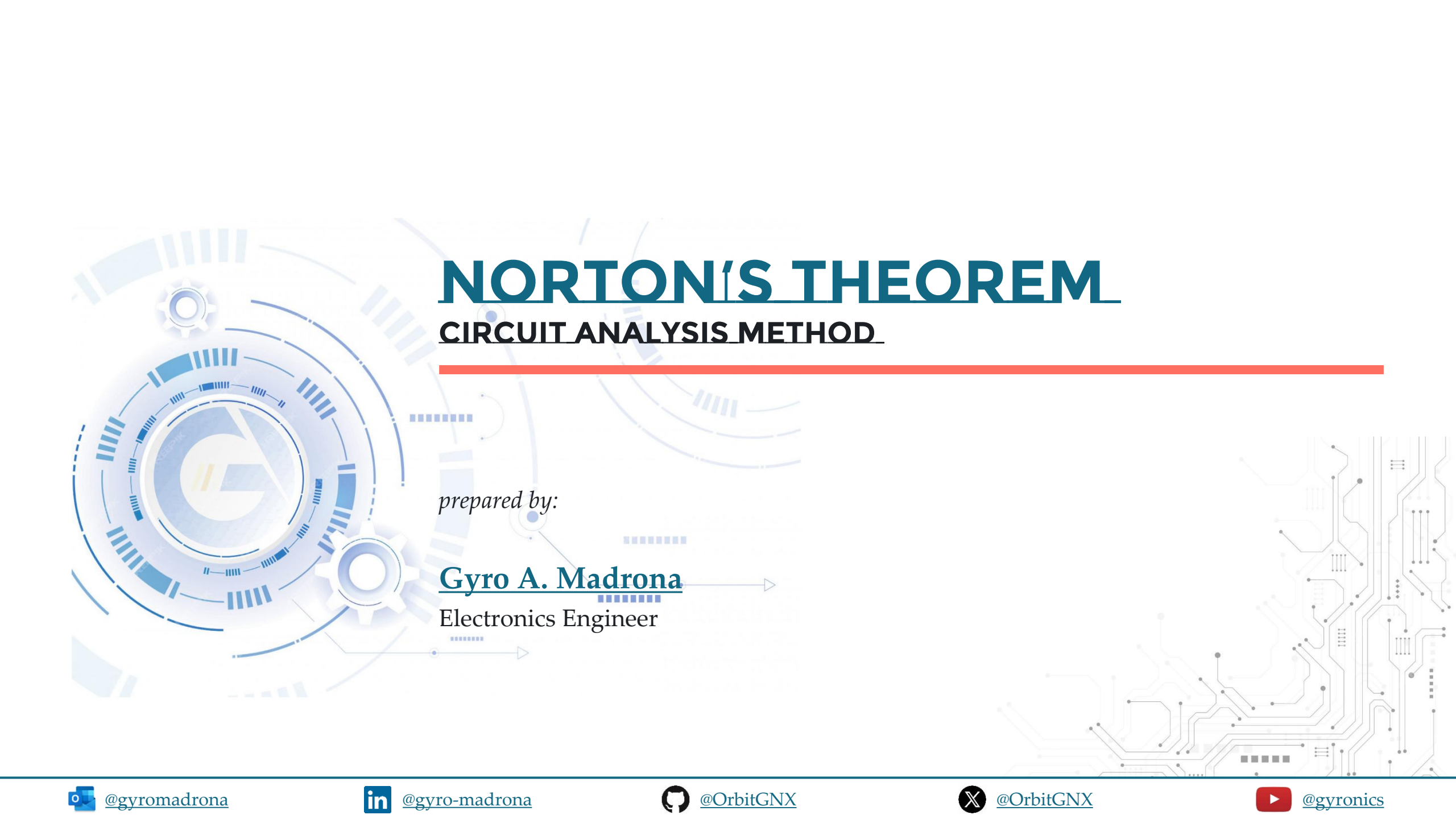




NORTON'S THEOREM

CIRCUIT ANALYSIS METHOD

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Norton's Theorem




NORTON'S THEOREM



NORTON'S THEOREM


Arbitrary Network

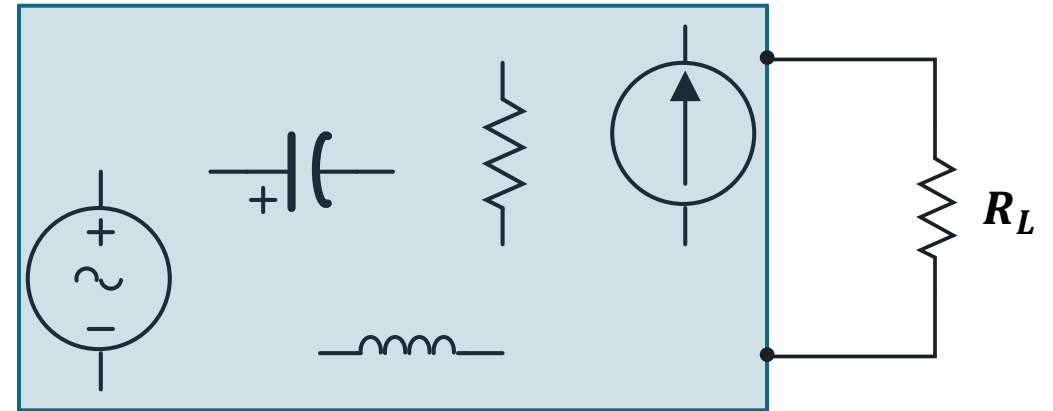It is possible to simplify any linear circuit, irrespective of how complex it is, to an equivalent circuit with a single current source, i_N and a parallel resistance, R_N .




NORTON'S THEOREM

Norton's Equivalent Circuit

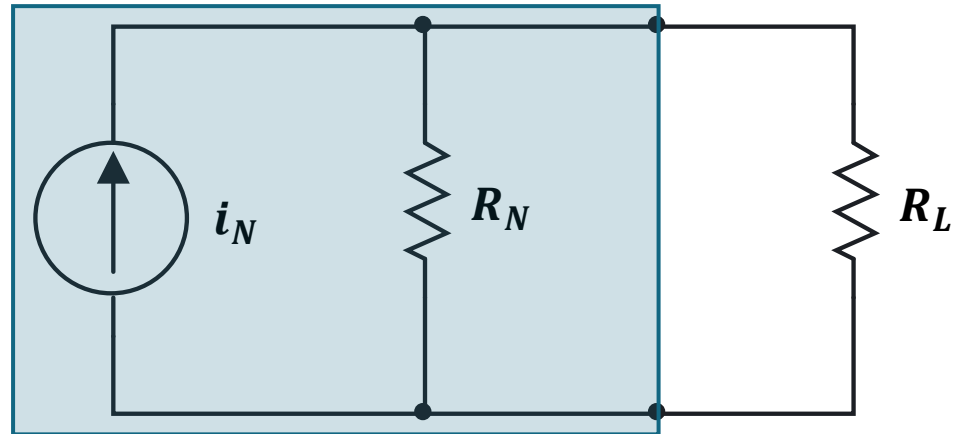


Arbitrary Network

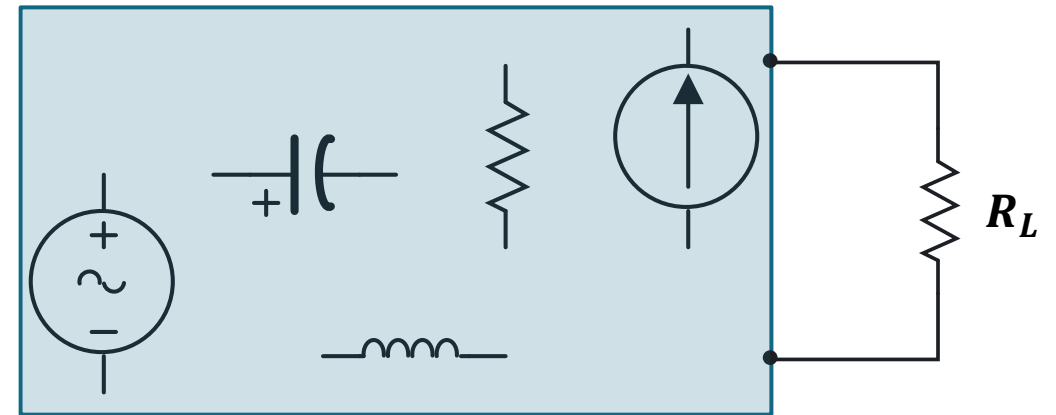


STEPS TO APPLY NORTON'S THEOREM

1. Identify the load.

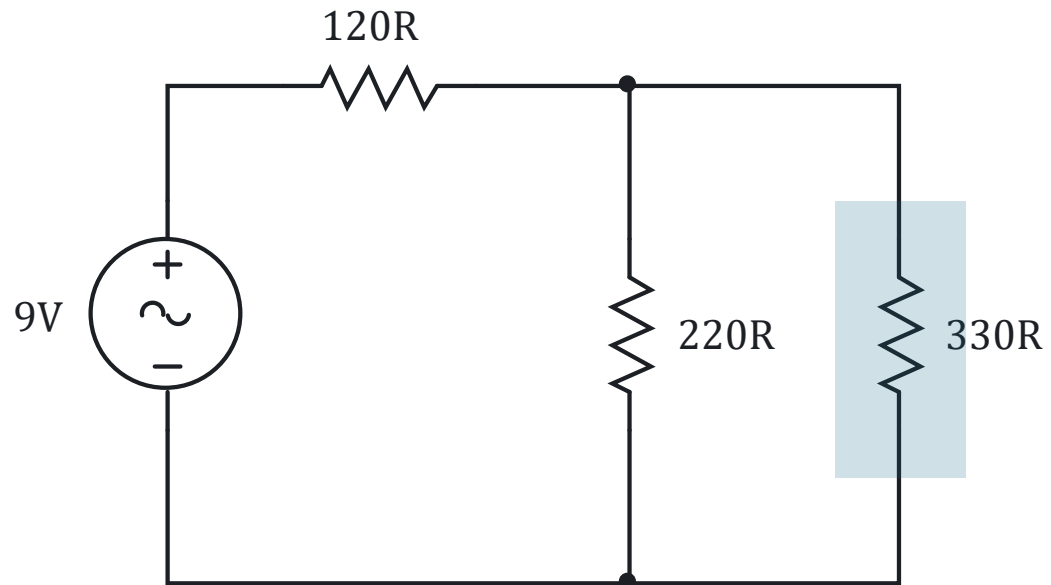

STEPS TO APPLY NORTON'S THEOREM

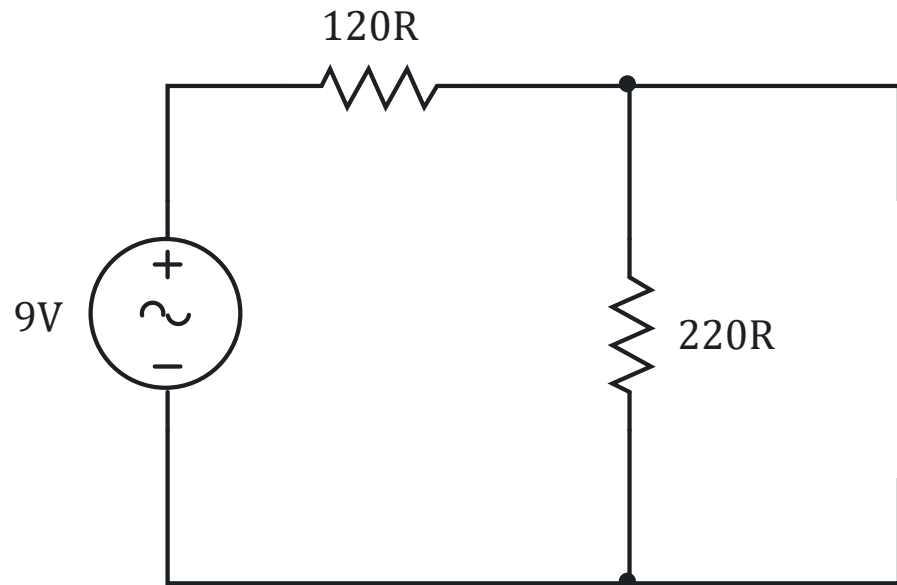
1. Identify the load.
2. Remove the load.




STEPS TO APPLY NORTON'S THEOREM

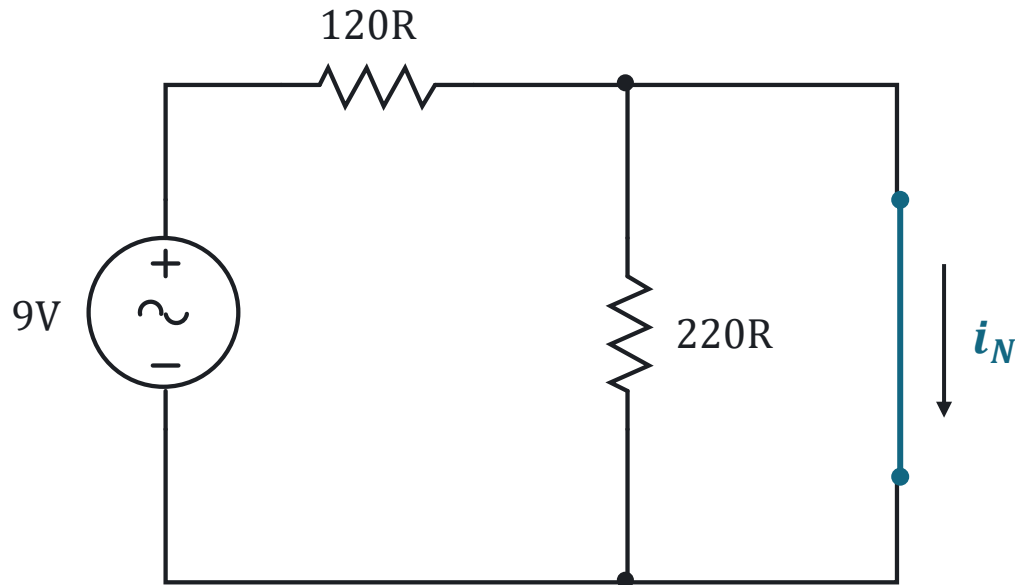1. Identify the load.
2. Remove the load.
3. Determine the Norton current, i_N :

Calculate the short-circuit current flowing through the shorted terminals where the load was connected.



STEPS TO APPLY NORTON'S THEOREM

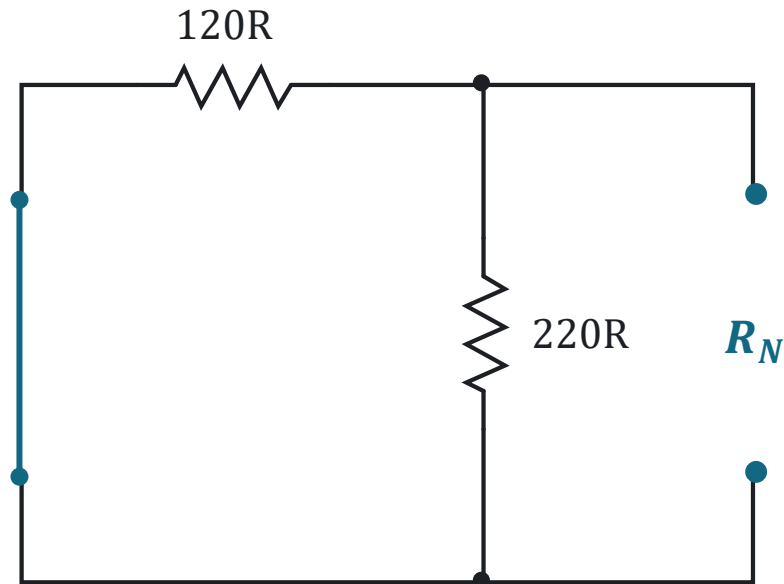

1. Identify the load.
2. Remove the load.
3. Determine the Norton current, i_N :

Calculate the short-circuit current flowing through the shorted terminals where the load was connected.


4. Determine the Norton resistance, R_N :

Set all independent sources to zero and calculate the equivalent resistance looking into the terminals where the load was connected.



STEPS TO APPLY NORTON'S THEOREM

Norton Equivalent Circuit

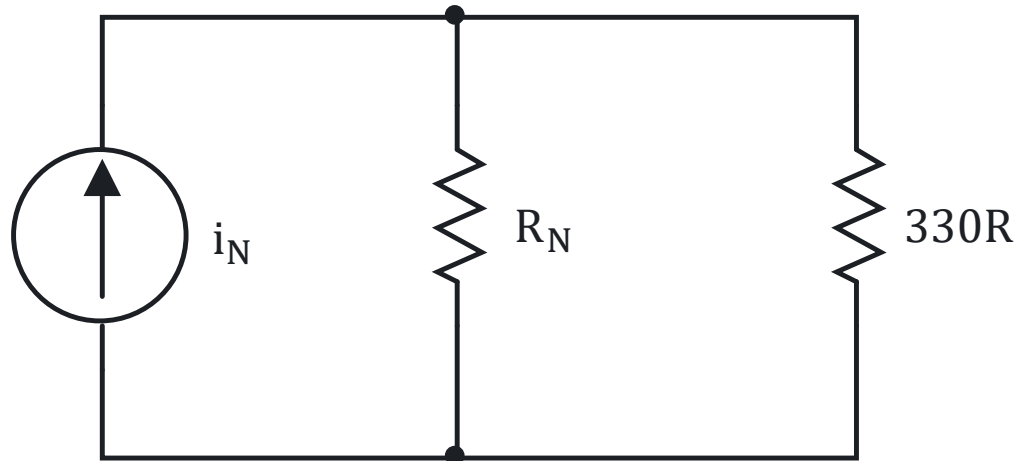

1. Identify the load.

2. Remove the load.

3. Determine the Norton current, i_N :

Calculate the short-circuit current flowing through the shorted terminals where the load was connected.

4. Determine the Norton resistance, R_N :

Set all independent sources to zero and calculate the equivalent resistance looking into the terminals where the load was connected.


5. Replace the original circuit with Norton equivalent and reconnect the load.



EXERCISE

Determine the load current, load voltage, and load power of the given circuit.

Solution

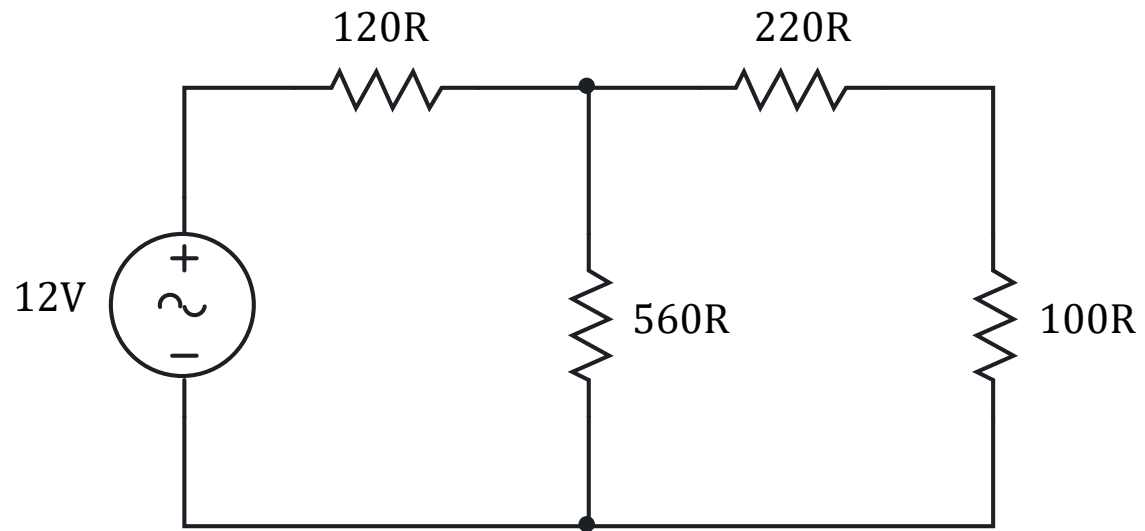

LABORATORY

