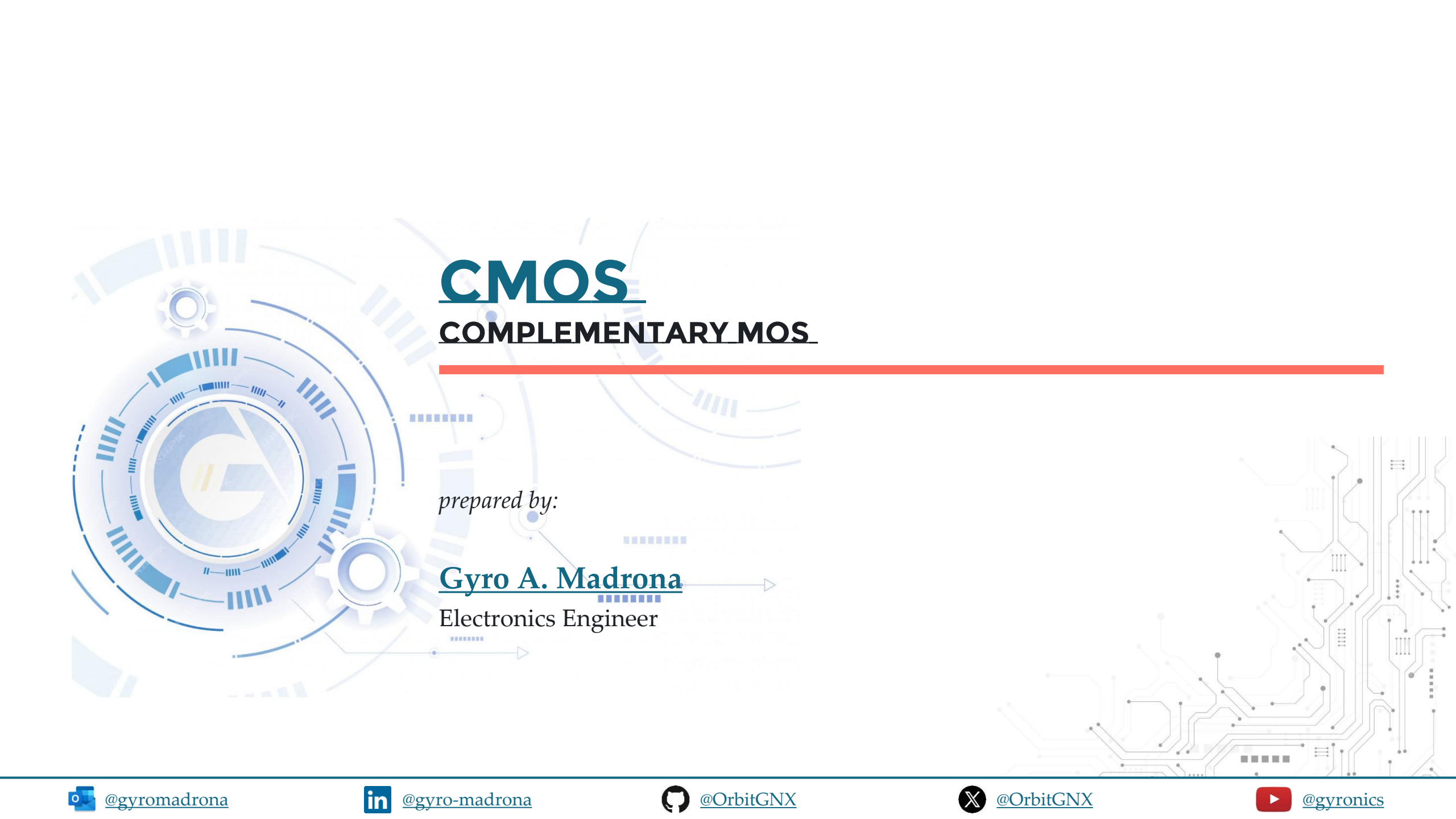




CMOS

COMPLEMENTARY MOS

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Complementary Metal-Oxide Semiconductor





CMOS

CMOS

(Complementary Metal-Oxide Semiconductor) is a technology used in integrated circuit (IC) design that combines n-channel and p-channel MOSFETs in a complementary arrangement.

CMOS Inverter

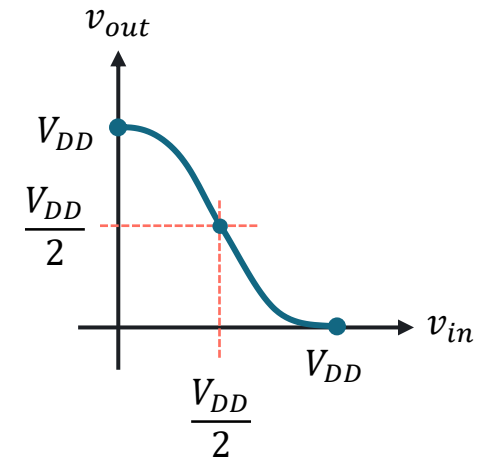
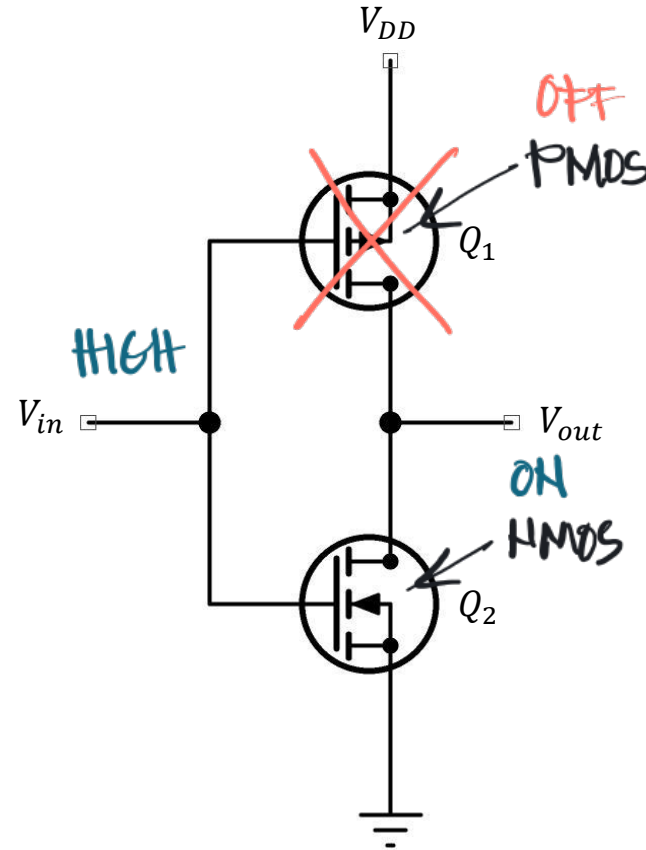


CMOS

CMOS

(Complementary Metal-Oxide Semiconductor) is a technology used in integrated circuit (IC) design that combines n-channel and p-channel MOSFETs in a complementary arrangement.



CMOS Inverter

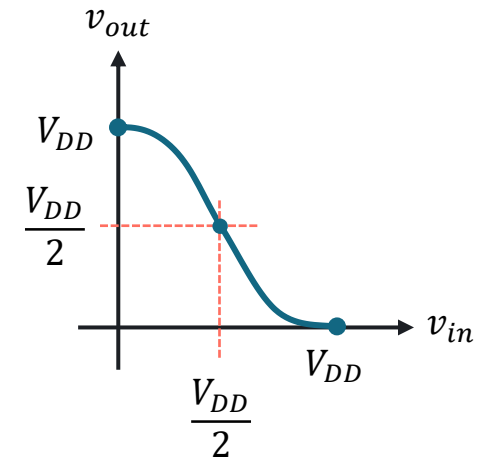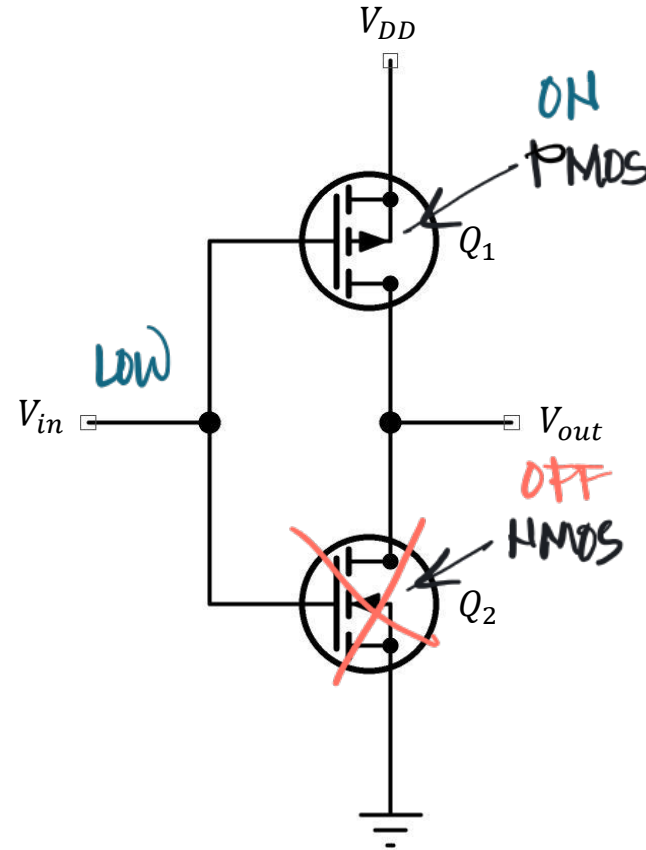

EXERCISE

The MOSFETs have $R_{DS(on)} = 100\Omega$ and $R_{DS(off)} = 1M\Omega$. What does the output waveform look like?



Solution

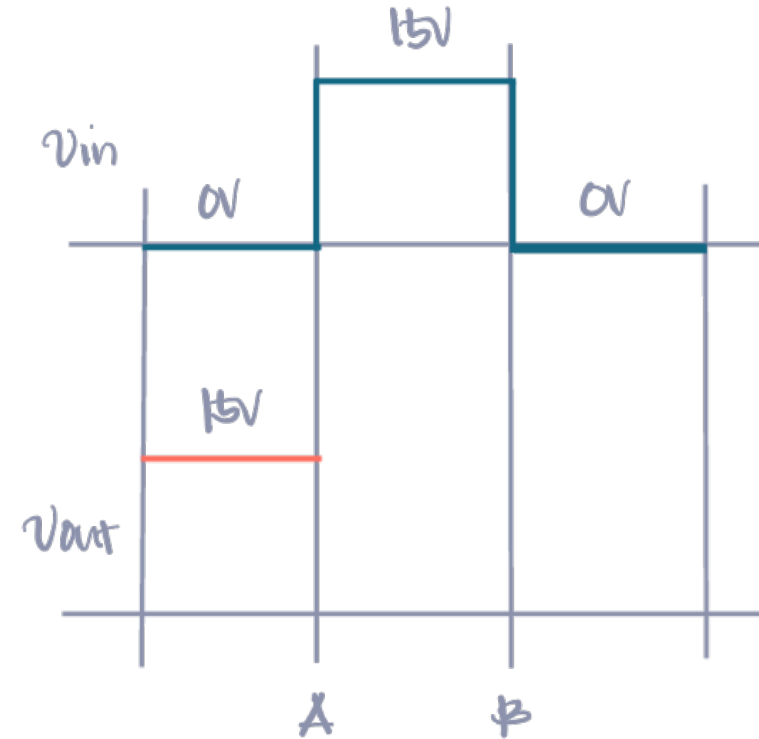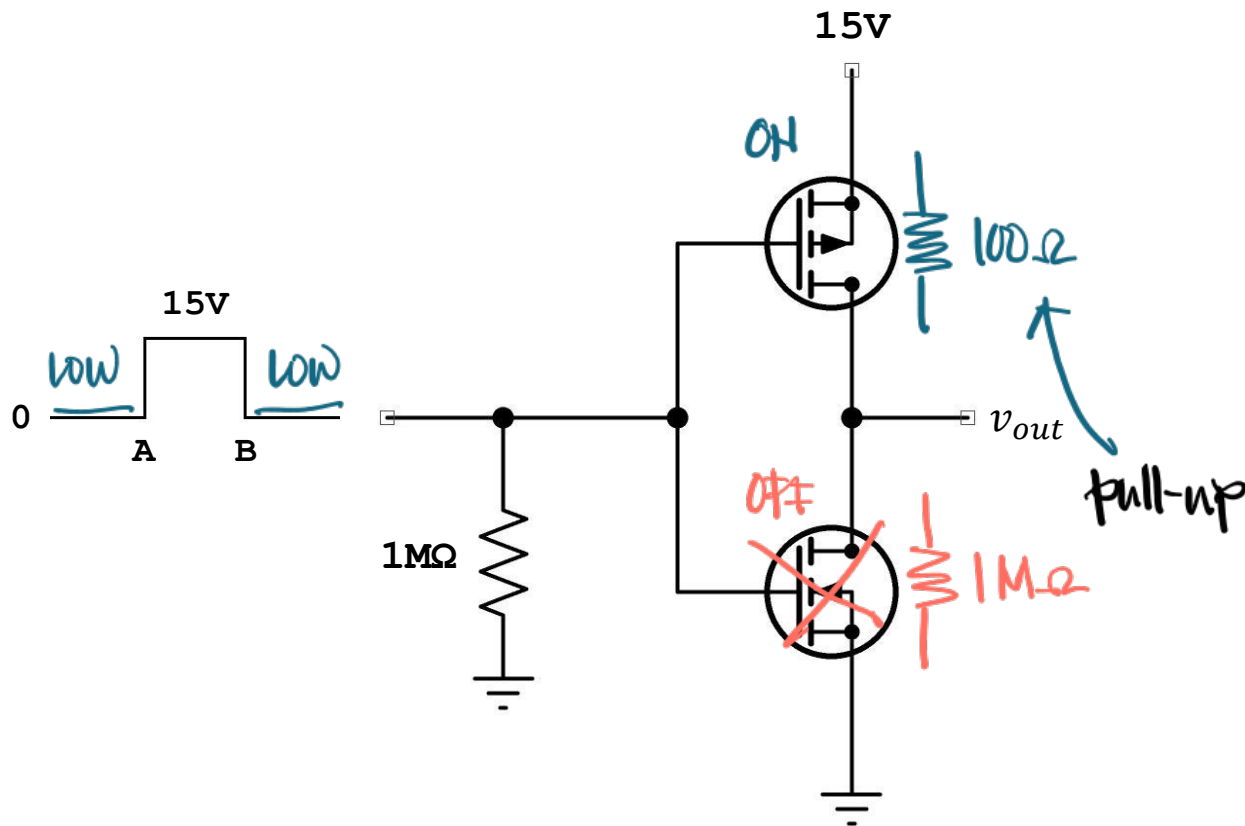

EXERCISE

The MOSFETs have $R_{DS(on)} = 100\Omega$ and $R_{DS(off)} = 1M\Omega$. What does the output waveform look like?

Solution

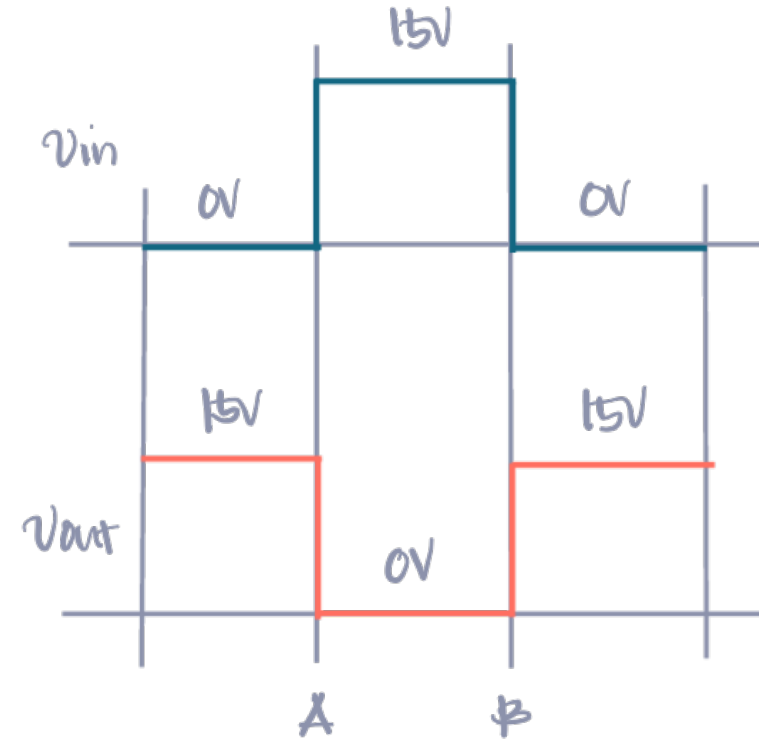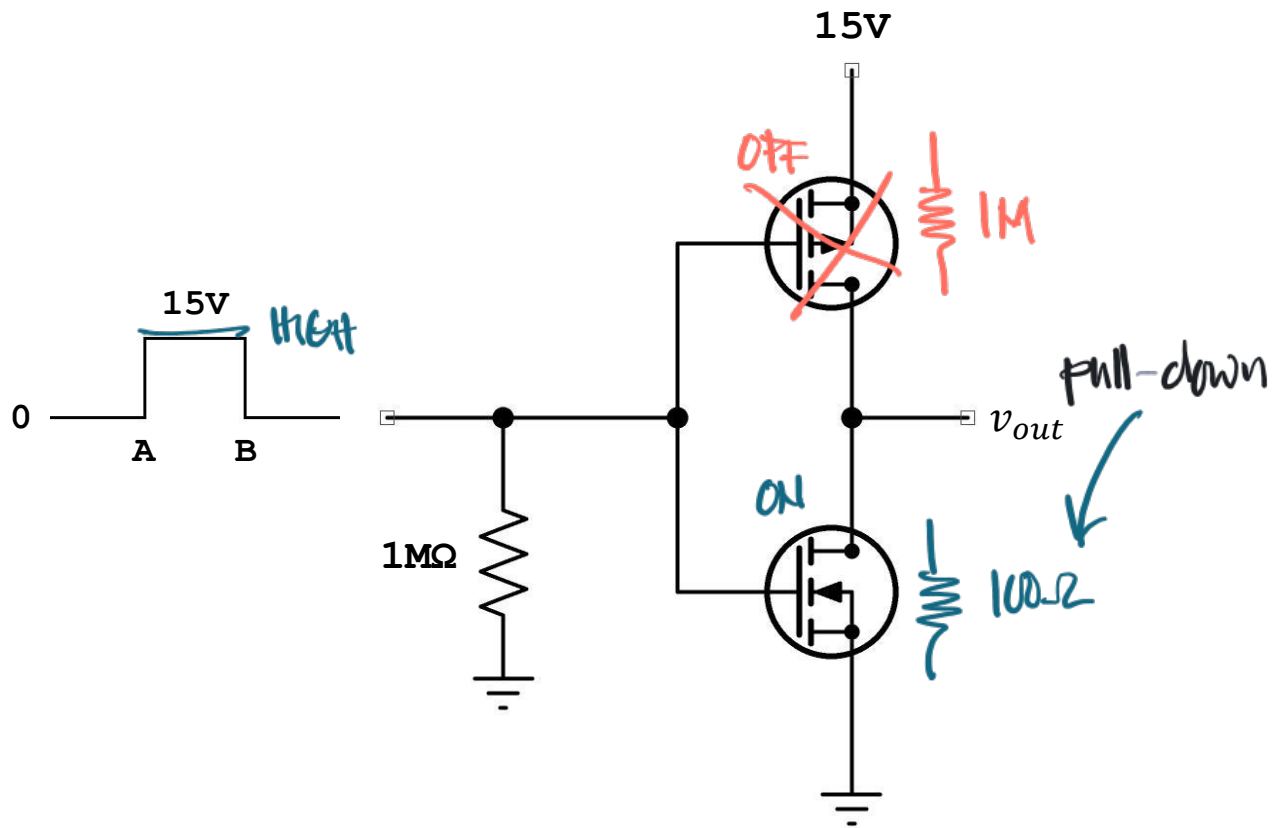

LABORATORY

