



REGISTERS

SEQUENTIAL LOGIC CIRCUITS

prepared by:

Gyro A. Madrona
Electronics Engineer

TOPIC OUTLINE

Registers

- Shift Register
- Parallel-Access Shift Register




REGISTERS



REGISTER

Flip-flop stores one bit of information.

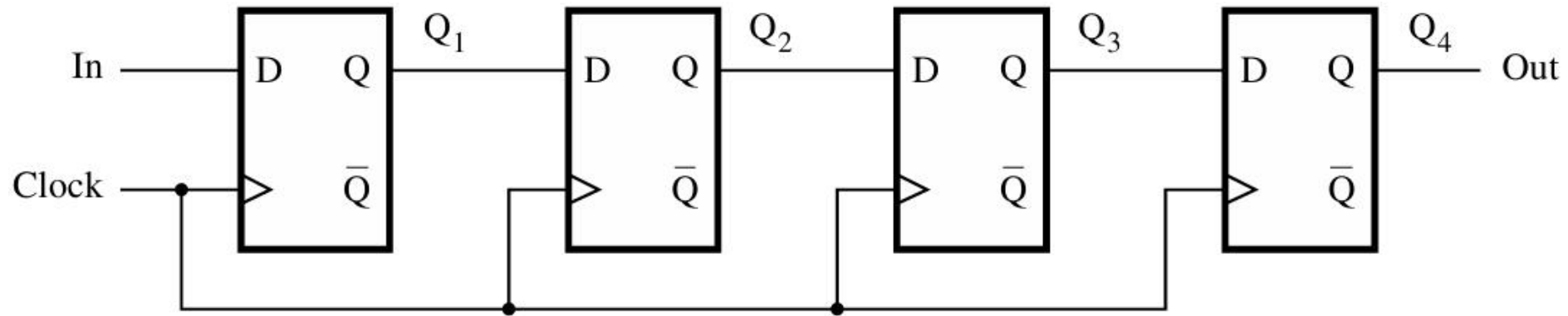Register store **n bits** of information.



4-bit register = 4 flip-flops

A simple shift-register


The term register is merely a convenience for referring to n-bit structures **consisting of flip-flops**.



SHIFT REGISTER

A register that provides the ability to shift its contents is called a shift register.

sample sequence: 0 0 0 1 1 1 0 1

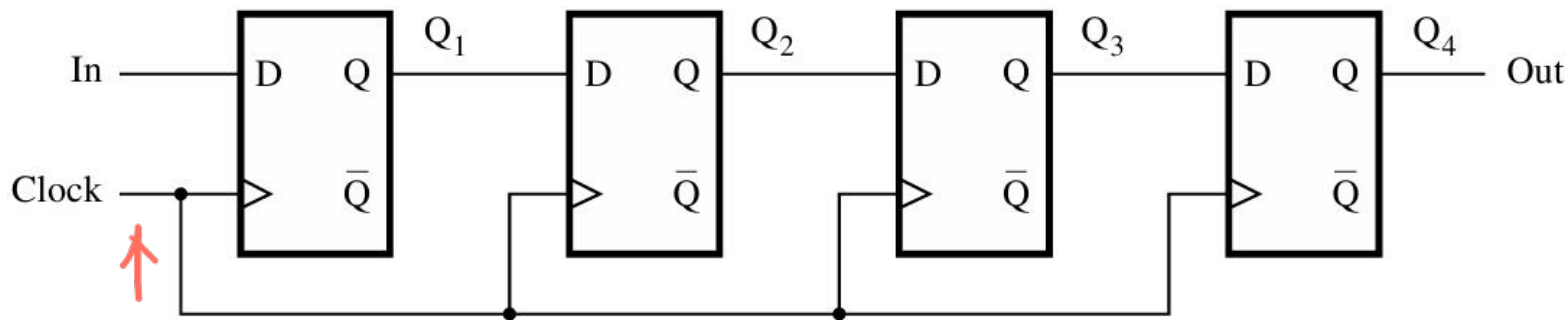

A simple shift-register

Shifted 1-bit every ↑

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t ₀	1	0	0	0	0
t ₁	0	1	0	0	0
t ₂	1	0	1	0	0
t ₃	1	1	0	1	0
t ₄	1	1	1	0	1
t ₅	0	1	1	1	0
t ₆	0	0	1	1	1
t ₇	0	0	0	1	1




PARALLEL-ACCESS SHIFT REGISTER

The control signal **Shift/Load** is used to select the mode of operation.

0 – operates as a shift register

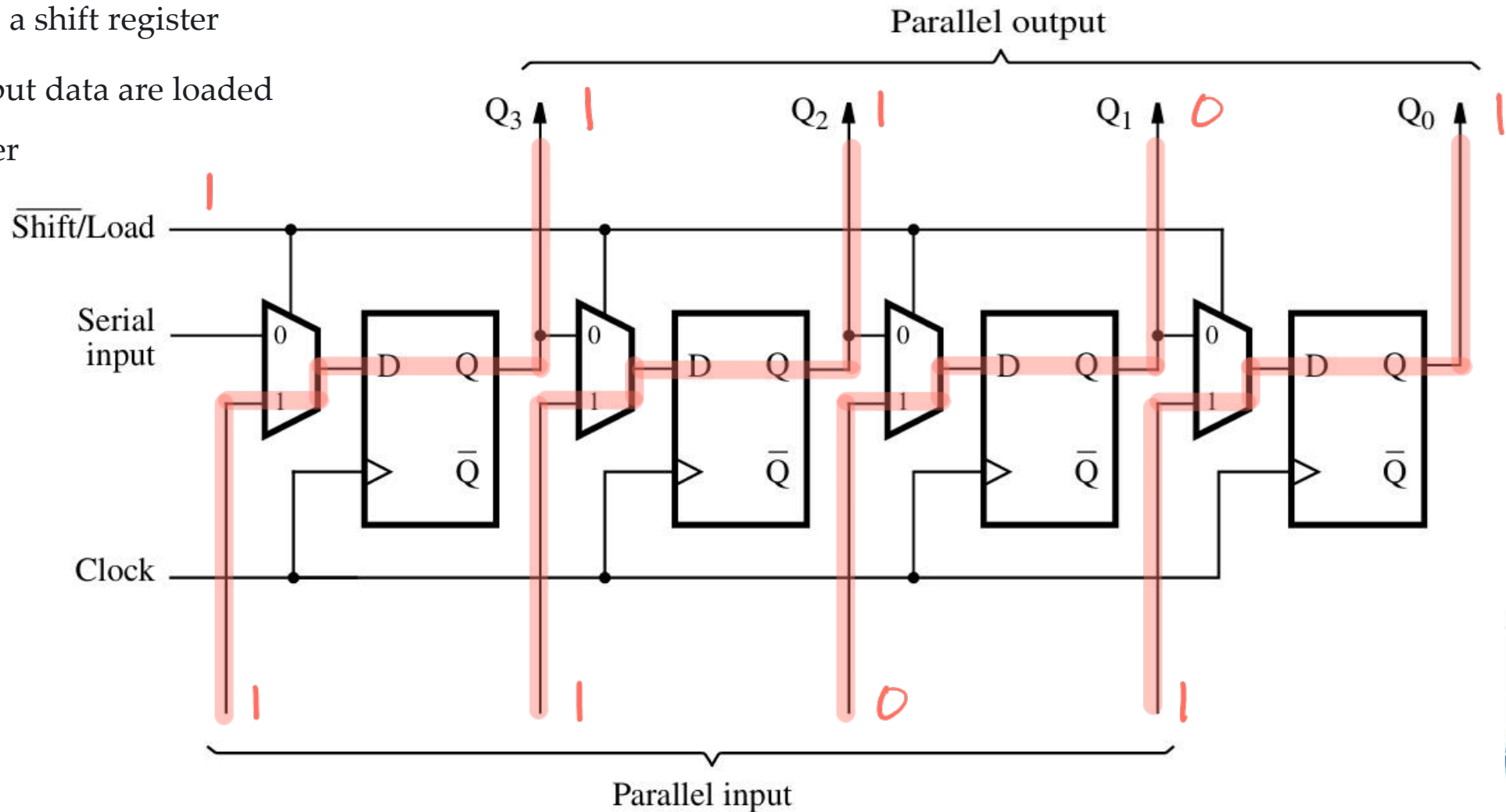1 – parallel input data are loaded into the register




PARALLEL-ACCESS SHIFT REGISTER

The control signal **Shift/Load** is used to select the mode of operation.

0 – operates as a shift register

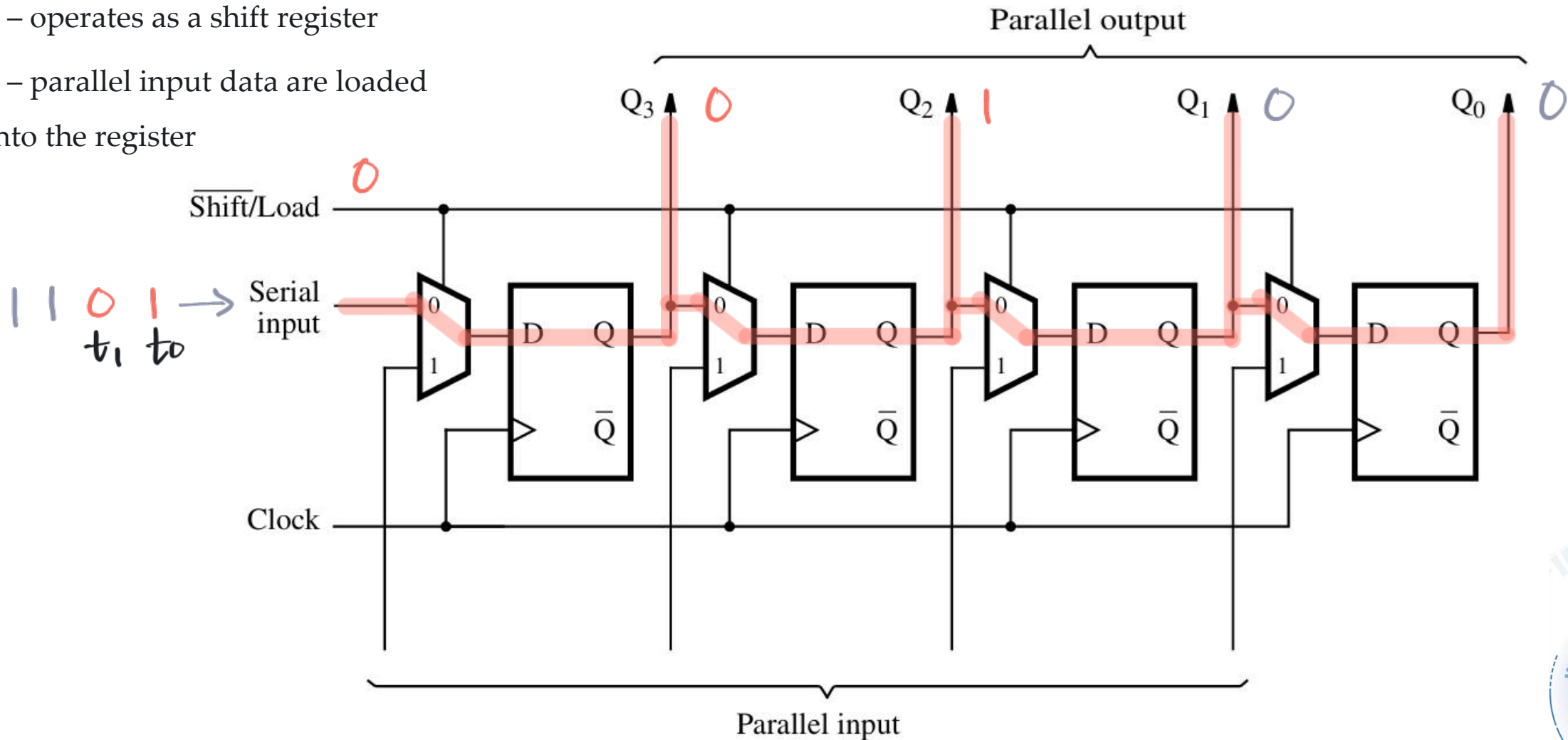1 – parallel input data are loaded into the register



LABORATORY

